

CSE 31


Computer Organization

Lecture 22 – CPU Design (2)

Announcement

- ▶ Lab #10
 - Due in 1 week
- ▶ Project #2
 - Start working on it during lab this week
 - Due Monday (4/29)
- ▶ HW #7 in CatCourses
 - Due Monday (5/6) at 11:59pm
- ▶ Reading assignment
 - Chapter 5.7-5.11 of zyBooks
 - Make sure to do the Participation Activities
 - Due Friday (5/3) at 11:59pm
- ▶ Course evaluation online by 5/9


Five Components of a Computer

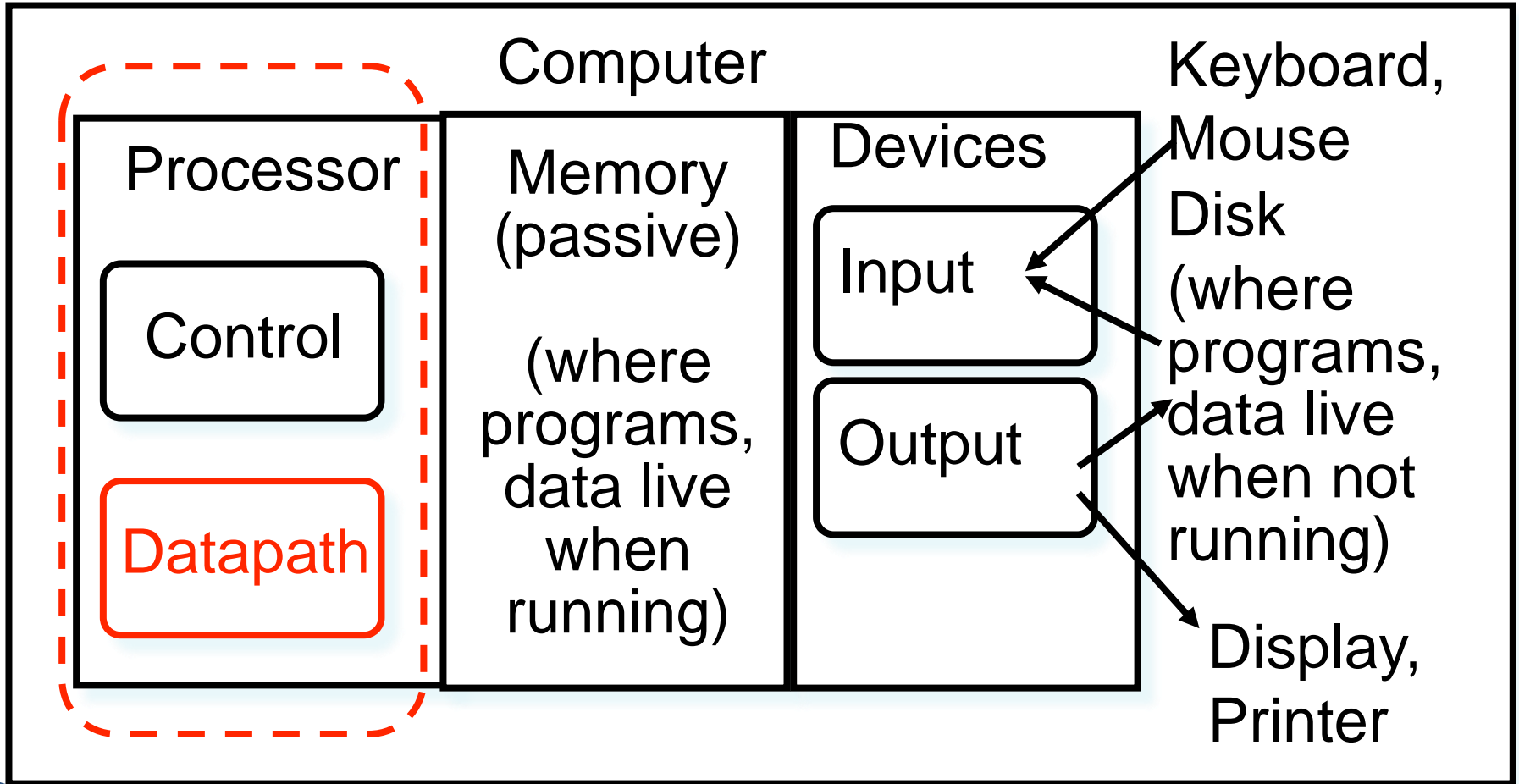

Review

- ▶ CPU design involves Datapath, Control
 - Datapath in MIPS involves 5 CPU stages
 1. Instruction Fetch
 2. Instruction Decode & Register Read
 3. ALU (Execute)
 4. Memory
 5. Register Write


Generic Diagram of Datapath

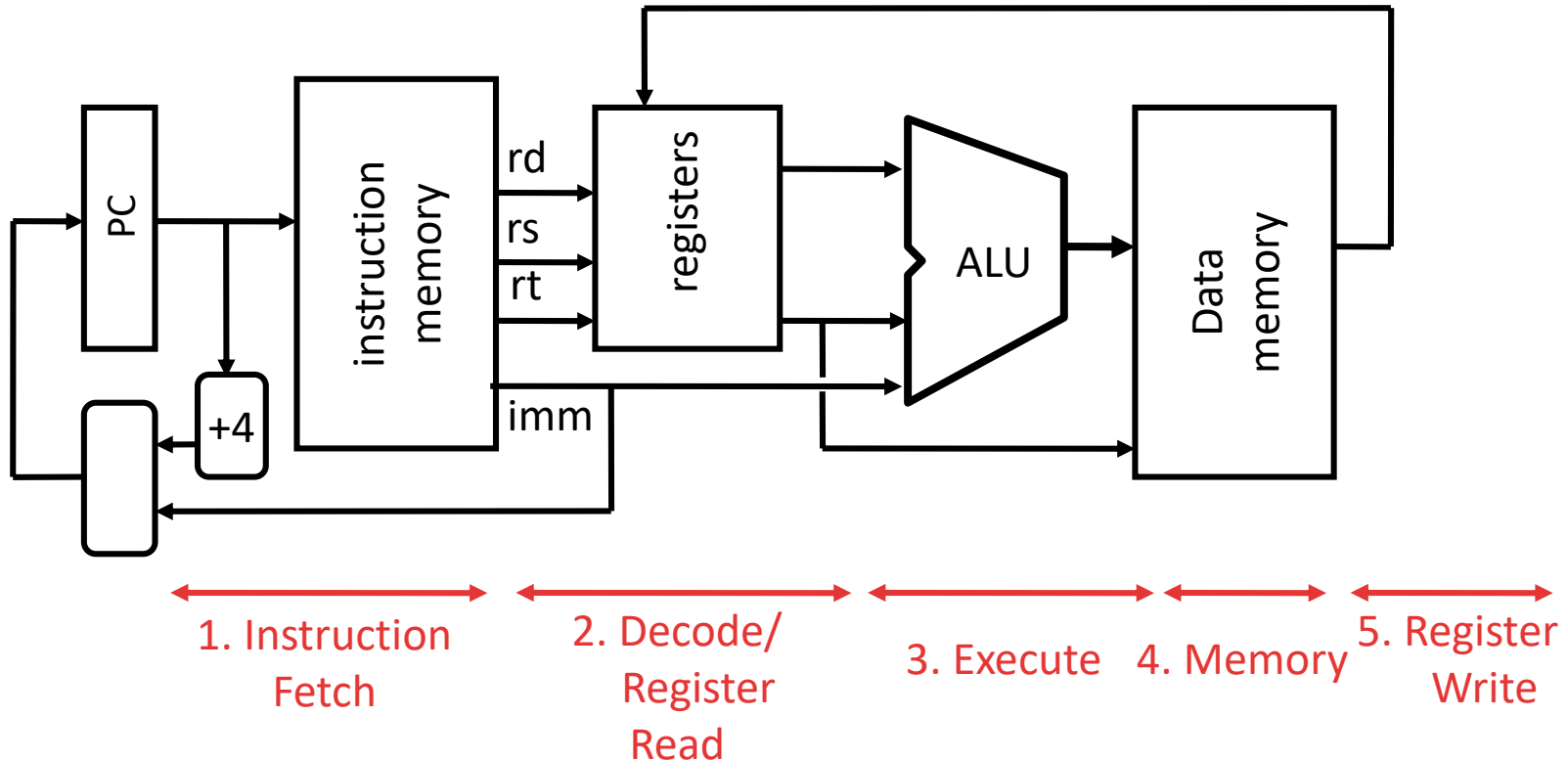

Datapath Walkthroughs (1/3)

- ▶ `add $r3,$r1,$r2 # r3 = r1+r2`
 - Stage 1: fetch this instruction, inc. PC
 - Stage 2: decode to find it's an `add`, then read registers `$r1` and `$r2`
 - Stage 3: add the two values retrieved in Stage 2
 - Stage 4: idle (nothing to write to memory)
 - Stage 5: write result of Stage 3 into register `$r3`

Example: add Instruction

 


Datapath Walkthroughs (2/3)

▶ `slti $r3, $r1, 17`

- Stage 1: fetch this instruction, inc. PC
- Stage 2: decode to find it's an `slti`, then read register `$r1`
- Stage 3: compare value retrieved in Stage 2 with the integer 17
- Stage 4: idle
- Stage 5: write the result of Stage 3 in register `$r3`


Example: `slti` Instruction

 

Datapath Walkthroughs (3/3)

- ▶ `sw $r3, 17($r1)`
 - Stage 1: fetch this instruction, inc. PC
 - Stage 2: decode to find it's a `sw`, then read registers `$r1` and `$r3`
 - Stage 3: add 17 to value in register `$r1` (retrieved in Stage 2)
 - Stage 4: write value in register `$r3` (retrieved in Stage 2) into memory address computed in Stage 3
 - Stage 5: idle (nothing to write into a register)

Example: *sw* Instruction

 


Why Five Stages? (1/2)

- ▶ Could we have a different number of stages?
 - Yes, and other architectures do
- ▶ So why does MIPS have five if instructions tend to idle for at least one stage?
 - The five stages are the union of all the operations needed by all the instructions.
 - There is one instruction that uses all five stages: the **load**

Why Five Stages? (2/2)


- ▶ `lw $r3, 17($r1)`
 - Stage 1: fetch this instruction, inc. PC
 - Stage 2: decode to find it's a `lw`, then read register `$r1`
 - Stage 3: add `17` to value in register `$r1` (retrieved in Stage 2)
 - Stage 4: read value from memory address compute in Stage 3
 - Stage 5: write value found in Stage 4 into register `$r3`

Example: 1w Instruction

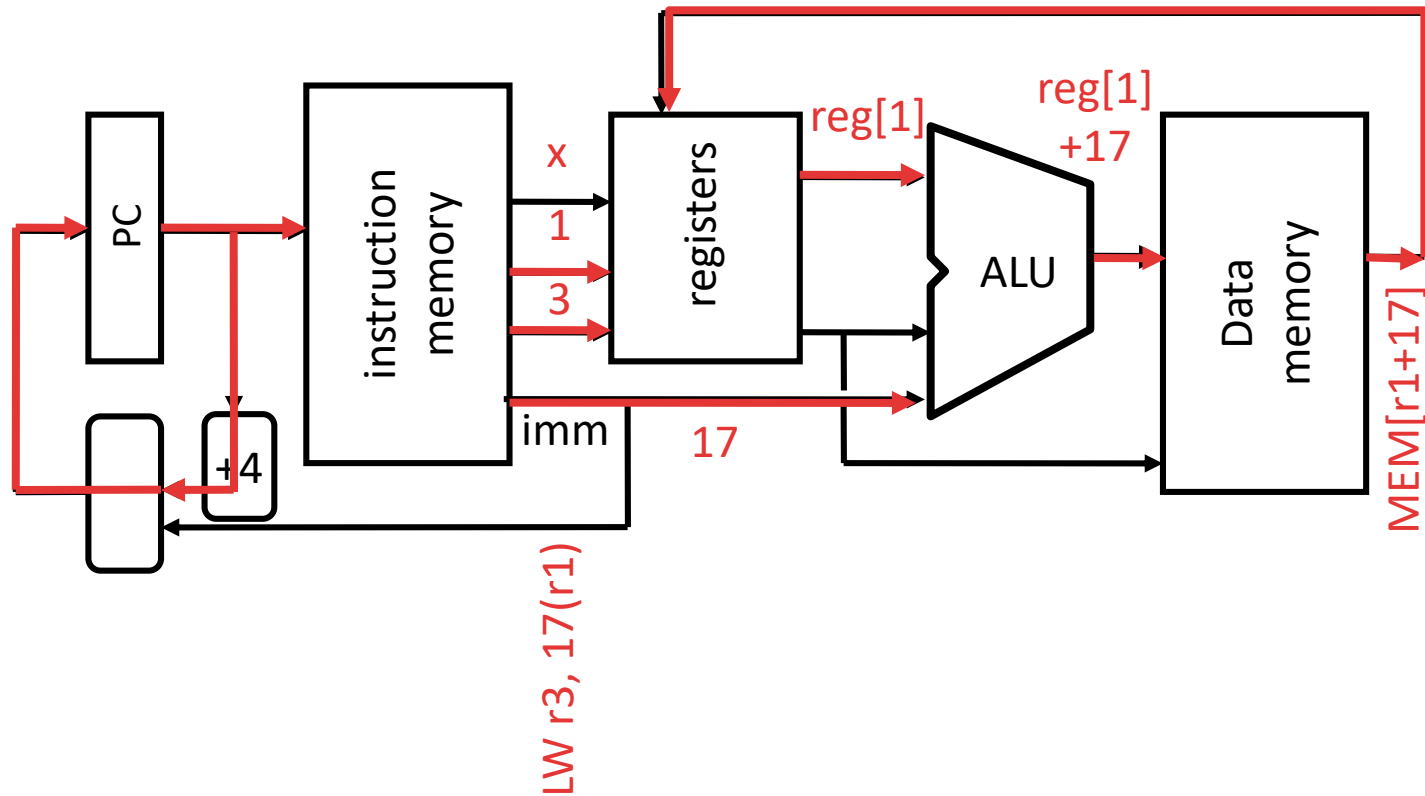


Datapath Summary

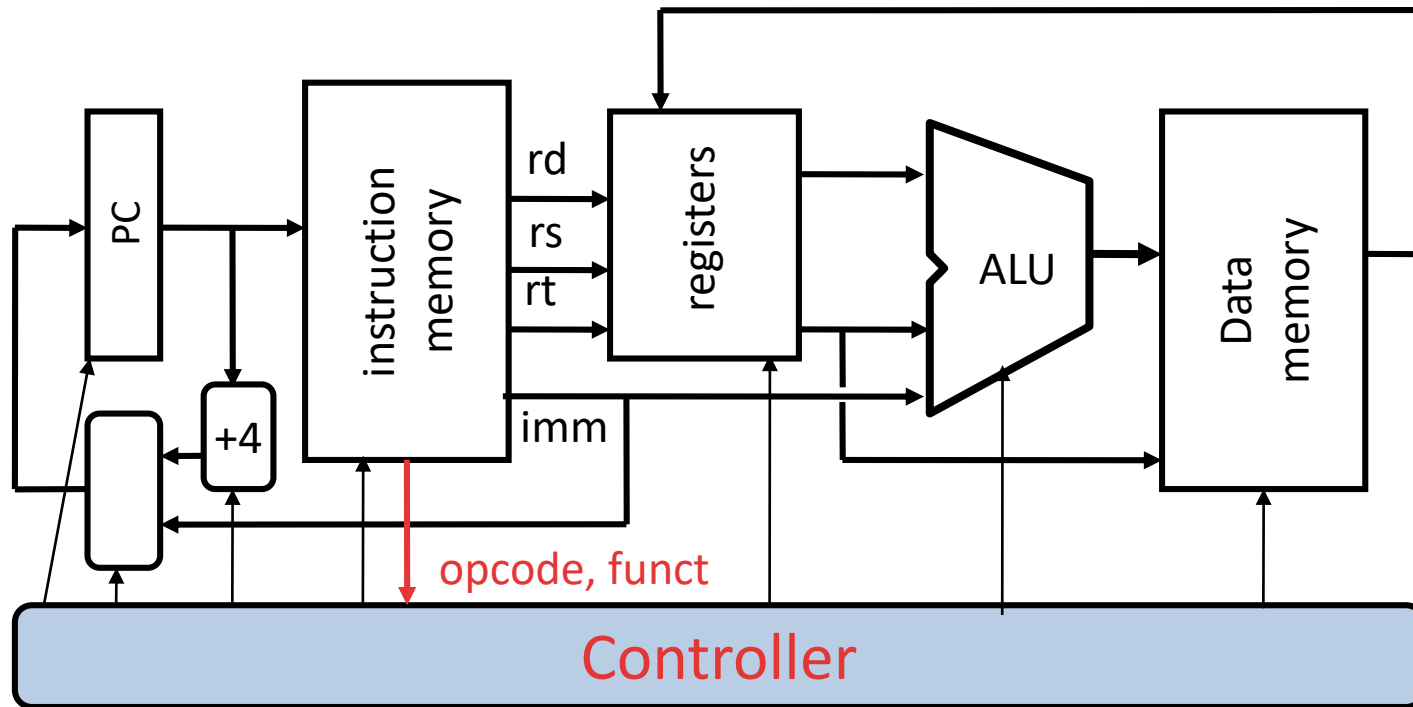- Datapath based on data transfers required to perform instructions
- Controller causes the right transfers to happen




CPU clocking (1/2)

 - For each instruction, how do we control the flow of information through the datapath?
- **Single Cycle CPU:** All stages of an instruction completed within one long clock cycle
 - Clock cycle sufficiently long to allow each instruction to complete all stages without interruption within one cycle



CPU clocking (2/2)

 - **Multiple-cycle CPU:** only one stage of instruction per clock cycle
- Clock is made as long as the slowest stage



- Several significant advantages over single cycle execution:
Unused stages in a particular instruction can be skipped OR
instructions can be pipelined (overlapped)
- Will talk about this in CSE 140!

What Hardware Is Needed? (1/2)

- ▶ PC: a register which keeps track of memory addr of the next instruction
- ▶ General Purpose Registers
 - used in Stages 2 (Read) and 5 (Write)
 - MIPS has 32 of these
- ▶ Memory
 - used in Stages 1 (Fetch) and 4 (R/W)
 - cache system makes these two stages as fast as the others, on average

What Hardware Is Needed? (2/2)

▶ ALU

- used in Stage 3
- something that performs all necessary functions: arithmetic, logicals, etc.
- we'll design details later


▶ Miscellaneous Registers

- In implementations with only one stage per clock cycle, registers are inserted between stages to hold intermediate data and control signals as they travel from stage to stage.
- Note: Register is a general purpose term meaning something that stores bits. Not all registers are in the "register file".

Quiz

- A. If the destination reg is the same as the source reg, we **could compute the incorrect value!**
- B. We're going to be able to read 2 registers and write a 3rd in **1 cycle**
- C. Datapath is hard, **Control is easy**


Generic Steps of Datapath

 


How do we handle the different register usage between r-type and i-type instructions?

Data Multiplexor (mux)


(2-to-1, n-bits)

 

4-to-1 Multiplexor?

 


A zoomed in version of RegFile and ALU

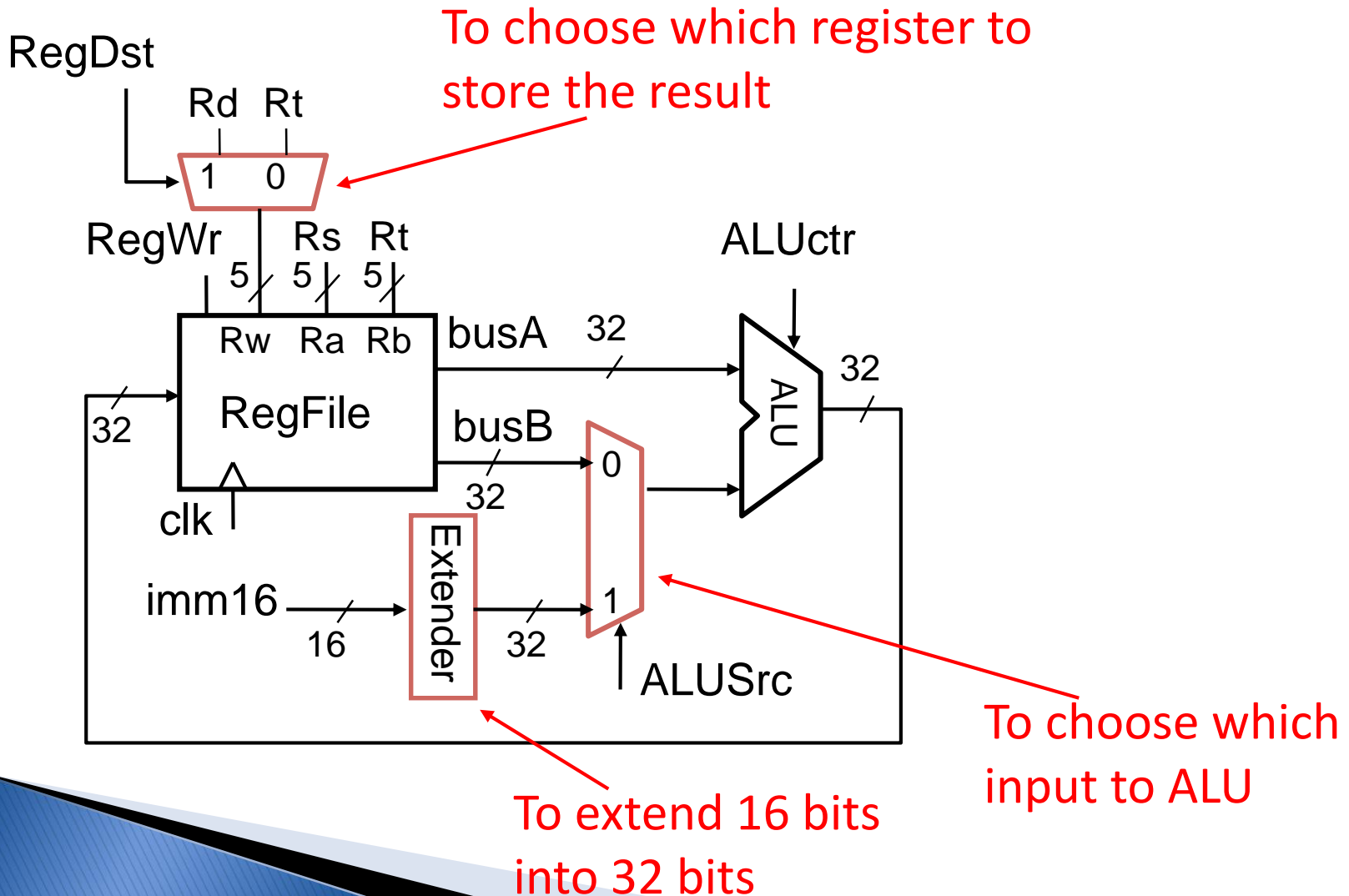


Operations with Immediate

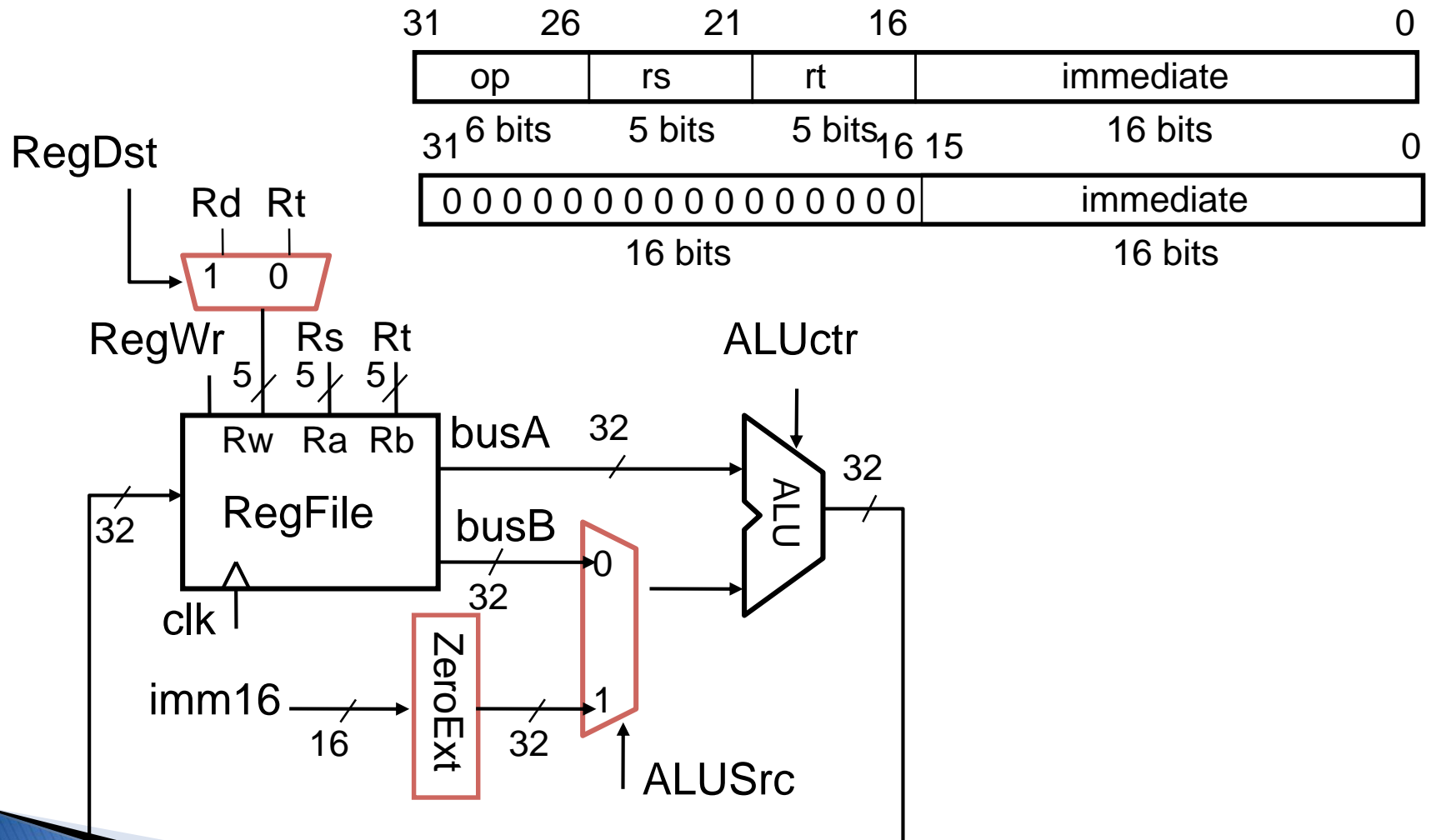- ▶ $R[rt] = R[rs] \text{ op ZeroExt}[imm16]$



Operations with Immediate

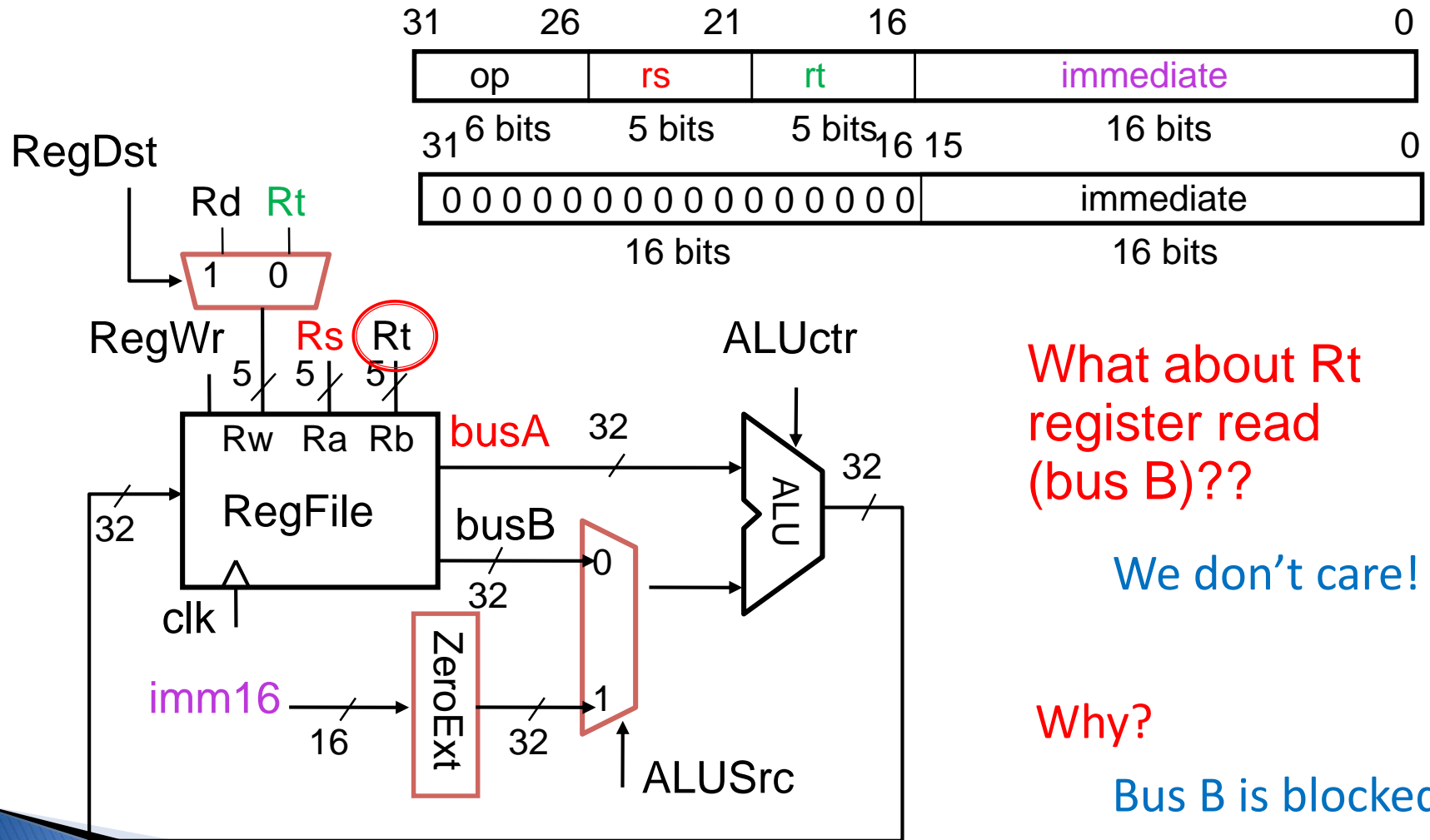- ▶ $R[\text{rt}] = R[\text{rs}] \text{ op ZeroExt}[\text{imm16}]$



What about Rt
register read
(bus B)??


We don't care!

Why?

Bus B is blocked

Load Memory

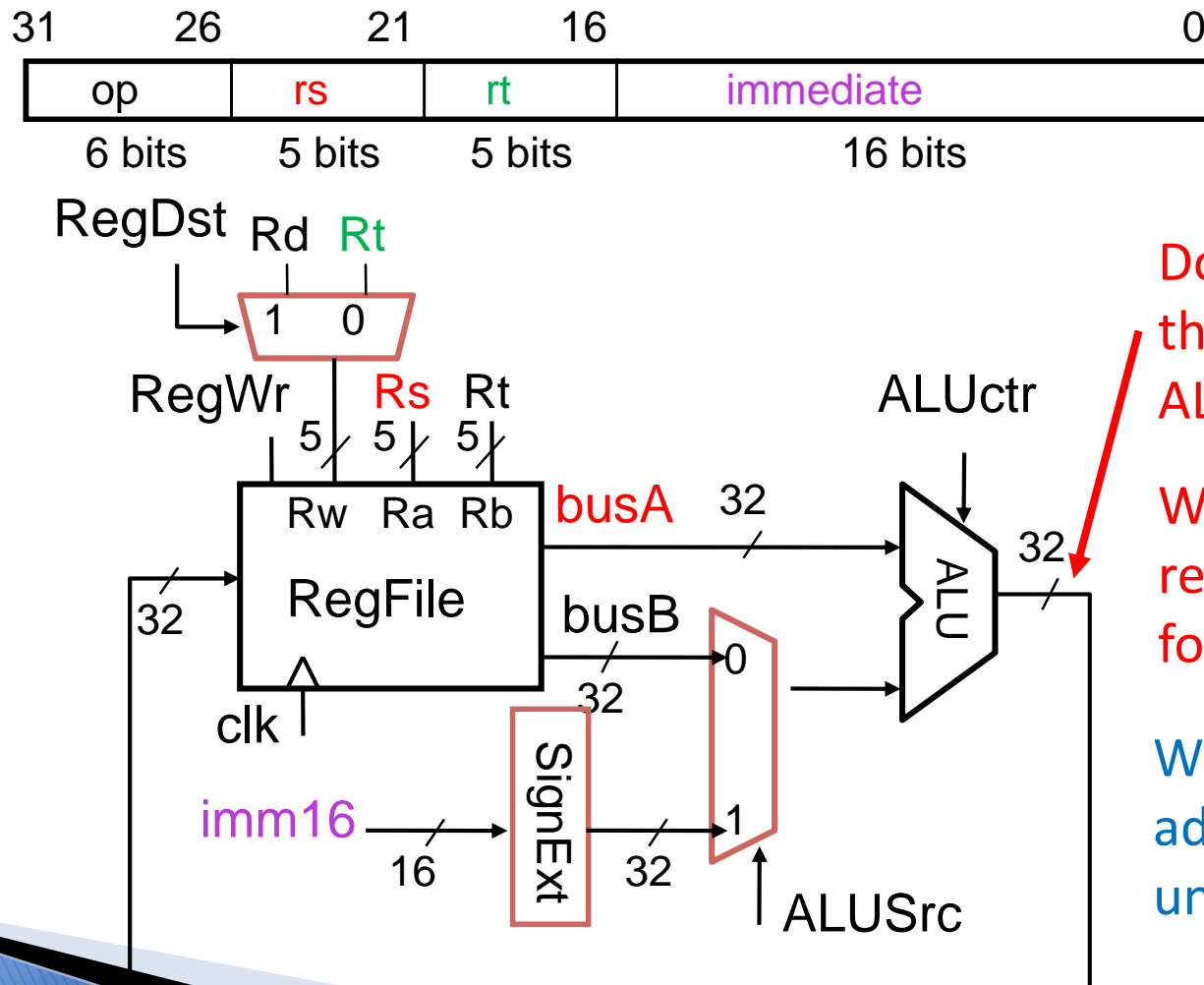- ▶ $R[\underline{rt}] = \text{Mem}[R[\text{rs}] + \text{SignExt}[\text{imm16}]]$
- ▶ Example: `lw rt, rs, imm16`



Do we store
the result of
ALU?


What is the
result of ALU
for?

We need to
add a memory
unit!

Load Memory

► $R[\underline{rt}] = \text{Mem}[R[rs] + \text{SignExt}[\text{imm16}]]$


► Example: `lw rt, rs, imm16`

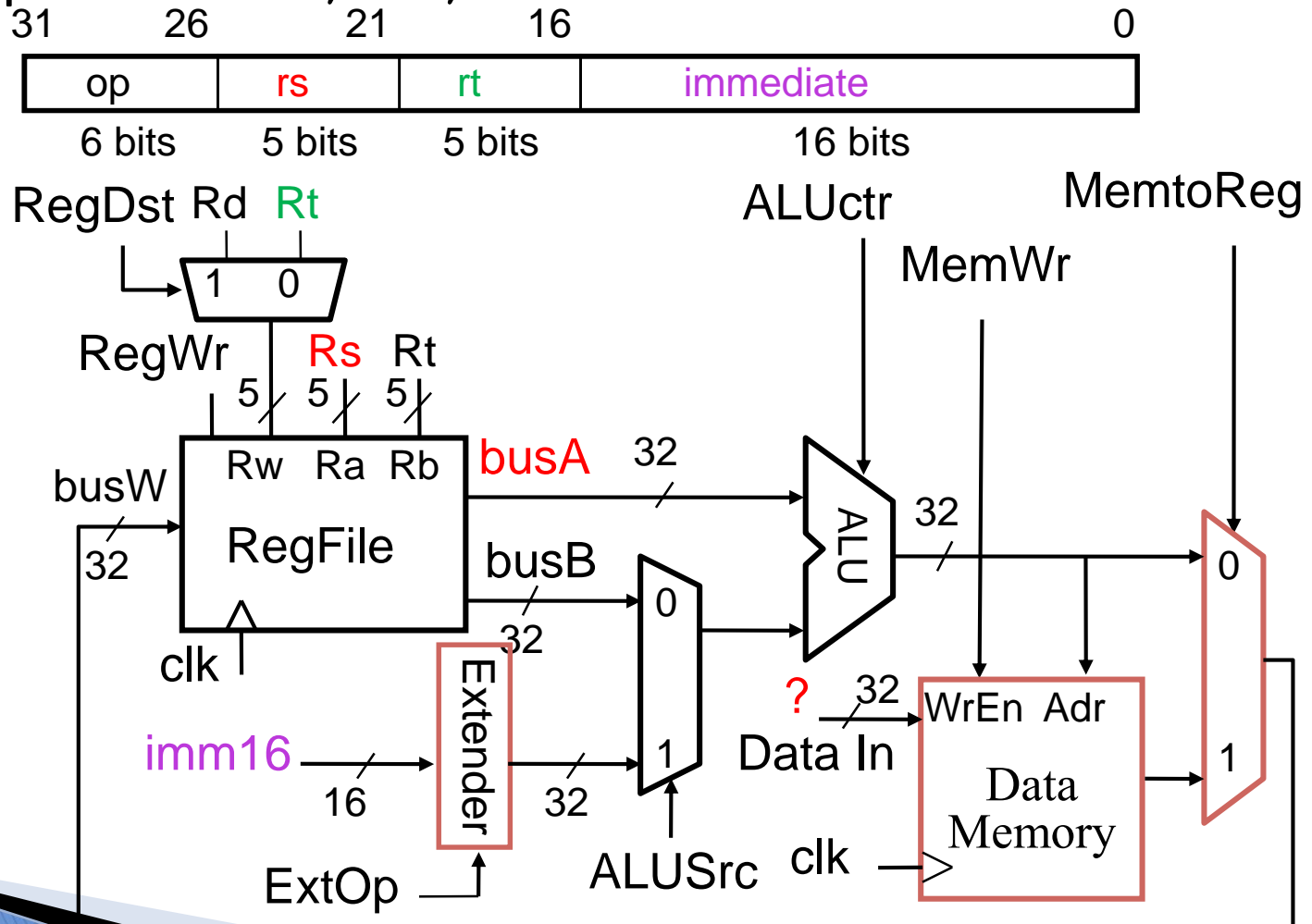

Store Memory

- ▶ $\text{Mem}[\text{R}[\text{rs}] + \text{SignExt}[\text{imm16}]] = \text{R}[\text{rt}]$

Ex.: `sw rt, rs, imm16`

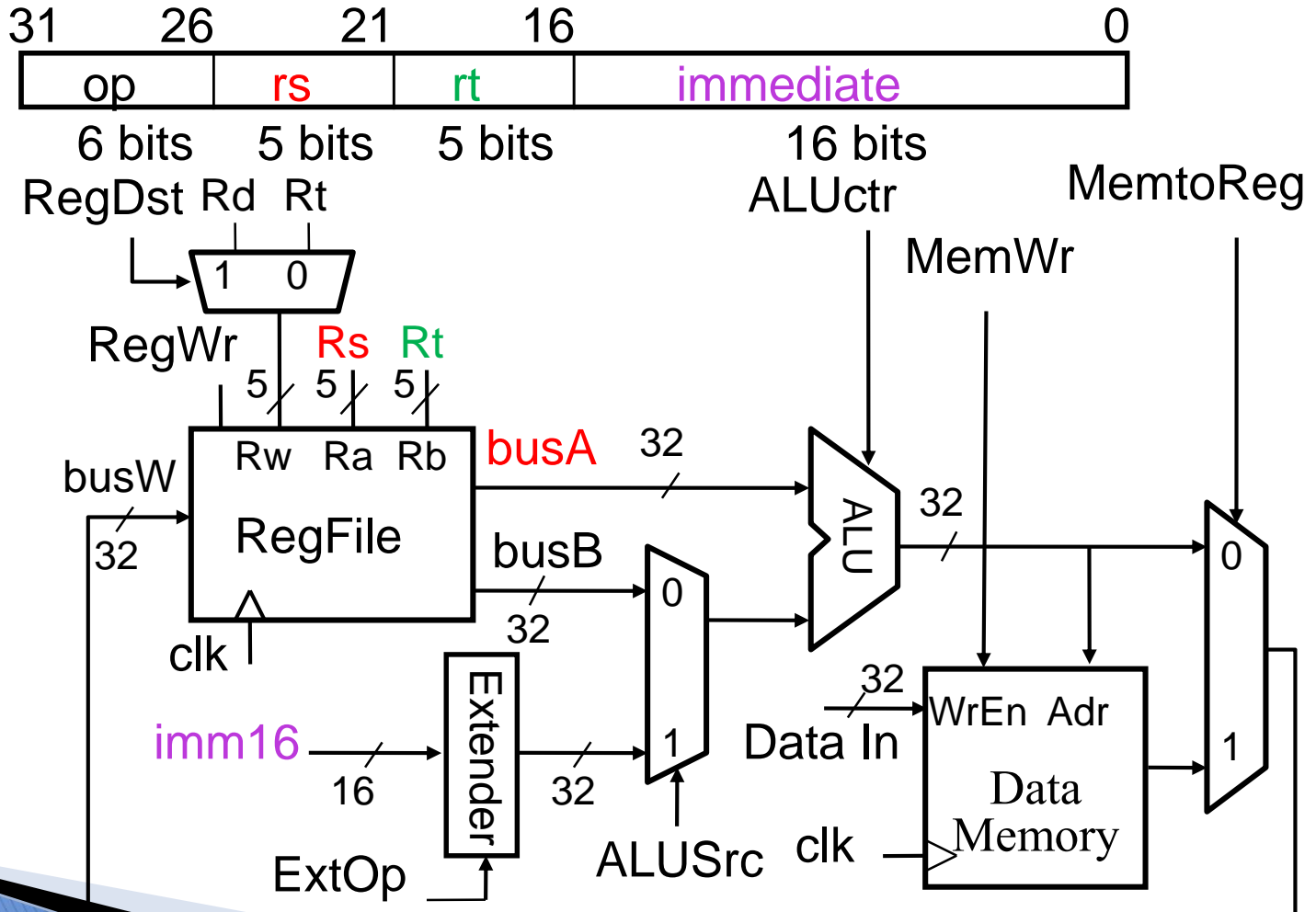

Store Memory

- ▶ $\text{Mem}[\text{R}[\text{rs}] + \text{SignExt}[\text{imm16}]] = \text{R}[\text{rt}]$

Ex.: `sw rt, rs, imm16`

