

# CSE 31

# Computer Organization

Lecture 24 – CPU Design (4)

# Announcement


- ▶ Lab #10
  - Due this week
- ▶ HW #7 in CatCourses
  - Due Monday (5/6) at 11:59pm
- ▶ HW #8 in zyBooks (Through CatCourses)
  - Due Saturday (5/11) at 11:59pm
- ▶ Course evaluation online by 5/9

# Announcement

- ▶ zyBooks assignment Re-dos
  - Re-submit at most 5 reading assignments **or** HW (**zyBooks only**)
  - Email to me (not your TAs)
    - Include your name, assignment numbers
    - (Monday) 5/13 at 11:59pm, no extension
  - Fill out online evaluation by 5/9, Thursday (70% of class)
- ▶ Final Exam
  - 5/11 (Saturday), 11:30 – 2:30pm
  - Cover all
  - Practice exam in CatCourses
  - Closed book
  - 2 sheet of note (8.5" x 11")
  - MIPS reference sheet will be provided
  - Review: 5/10 (Friday) 2-4pm, COB2 140

# TT $\Rightarrow$ Gates (e.g., majority circ.)

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

# Canonical forms (1/2)

	$abc$	$y$
$\bar{a} \cdot \bar{b} \cdot \bar{c}$	000	1
$\bar{a} \cdot \bar{b} \cdot c$	001	1
	010	0
	011	0
$a \cdot \bar{b} \cdot \bar{c}$	100	1
	101	0
$a \cdot b \cdot \bar{c}$	110	1
	111	0




$$y = \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + a\bar{b}\bar{c} + ab\bar{c}$$

Sum-of-products  
Sum-of-minterms  
(ORs of ANDs)
 
## Canonical forms (2/2)

$$\begin{aligned}y &= \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + a\bar{b}\bar{c} + ab\bar{c} \\&= \bar{a}\bar{b}(\bar{c} + c) + a\bar{c}(\bar{b} + b) && \text{distribution} \\&= \bar{a}\bar{b}(1) + a\bar{c}(1) && \text{complementarity} \\&= \bar{a}\bar{b} + a\bar{c} && \text{identity}\end{aligned}$$



# Canonical forms example


A	B	C	O
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

$$= \bar{a}\bar{b}c + \bar{a}bc + ab\bar{c}$$

$$= \bar{a}c(\bar{b} + b) + ab\bar{c}$$


$$= \bar{a}c + ab\bar{c}$$

# Single Cycle Datapath

 




# Abstract View of the Implementation

 
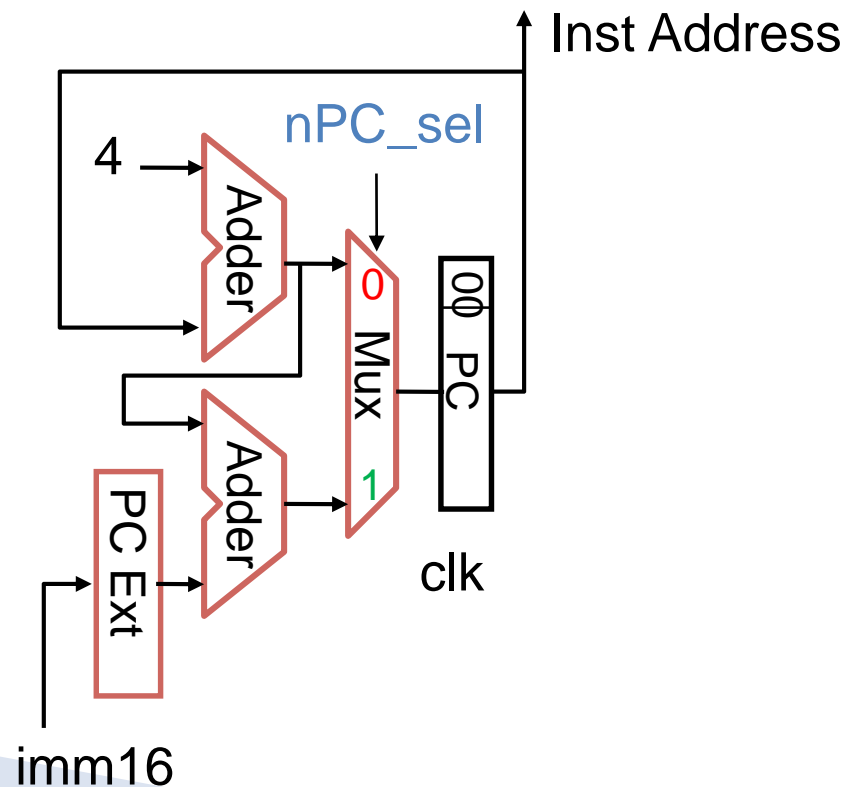
# Meaning of the Control Signals


- ▶ **nPC\_sel**: “+4”:  $0 \Rightarrow PC \leftarrow PC + 4$   
“br”:  $1 \Rightarrow PC \leftarrow PC + 4 + \{\text{SignExt}(\text{Imm16}), 00\}$   
“n”=next

- ▶ Later in lecture: higher-level connection between mux and branch condition



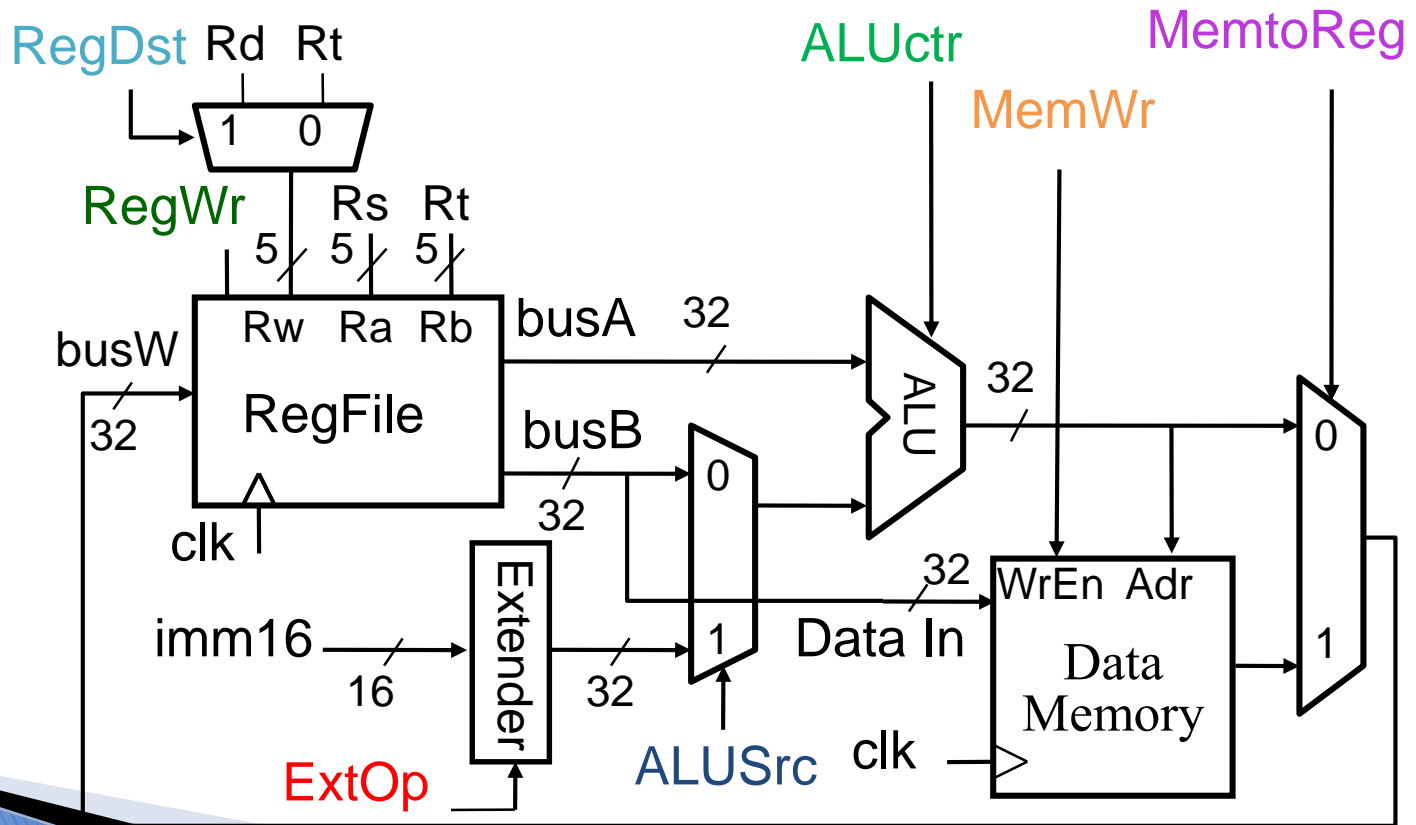
# Meaning of the Control Signals

- ▶ **ExtOp**: “zero”, “sign”
- ▶ **ALUsrc**: 0  $\Rightarrow$  regB; 1  $\Rightarrow$  immedi
- ▶ **ALUctr**: “ADD”, “SUB”, “OR”
- **MemWr**: 1  $\Rightarrow$  write memory
- **MemtoReg**: 0  $\Rightarrow$  ALU; 1  $\Rightarrow$  Mem
- **RegDst**: 0  $\Rightarrow$  “rt”; 1  $\Rightarrow$  “rd”
- **RegWr**: 1  $\Rightarrow$  write register



# The Add Instruction

 

add rd, rs, rt


- MEM[PC]                      Fetch the instruction from memory
- $R[rd] = R[rs] + R[rt]$       The actual operation
- $PC = PC + 4$  Calculate the next instruction's address

# Instruction Fetch Unit start of Add


- Fetch the instruction from Instruction memory:

Instruction = MEM[PC]


- same for all instructions

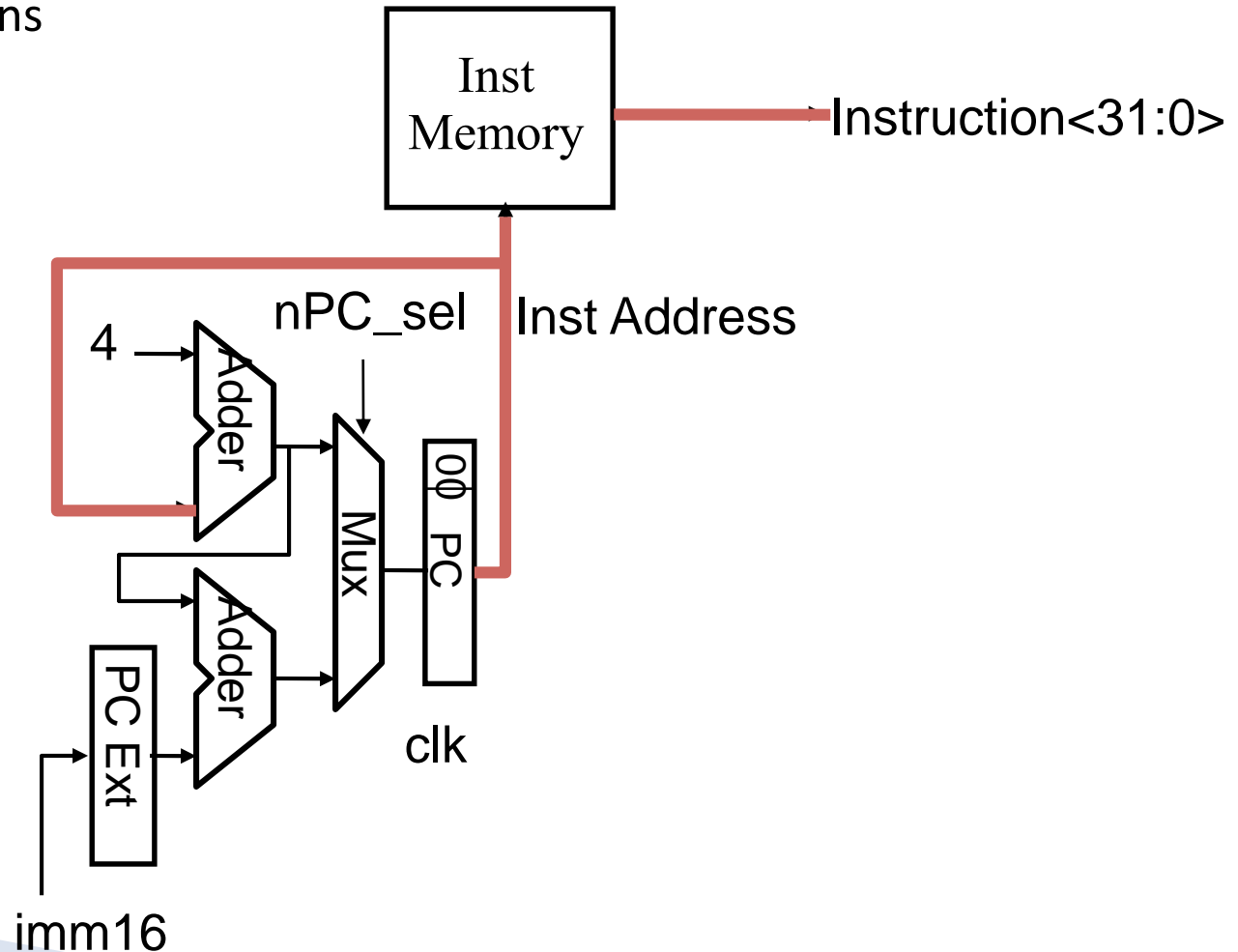

# The Single Cycle Datapath during Add

 


$$R[rd] = R[rs] + R[rt]$$

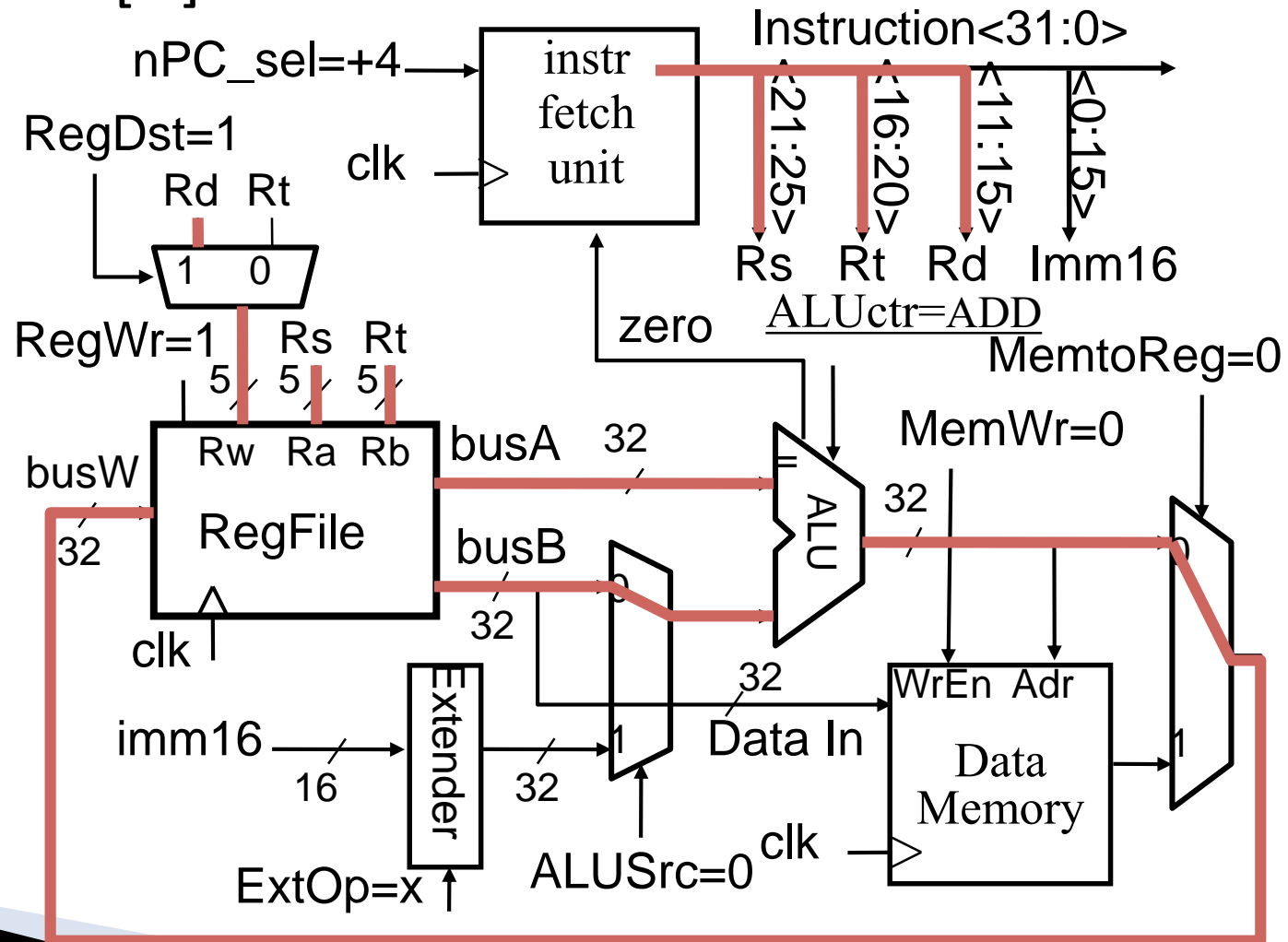

 
# Instruction Fetch Unit end of Add


- ▶  $PC = PC + 4$ 
  - This is the same for all instructions except: Branch and Jump



# Single Cycle Datapath for Ori

 


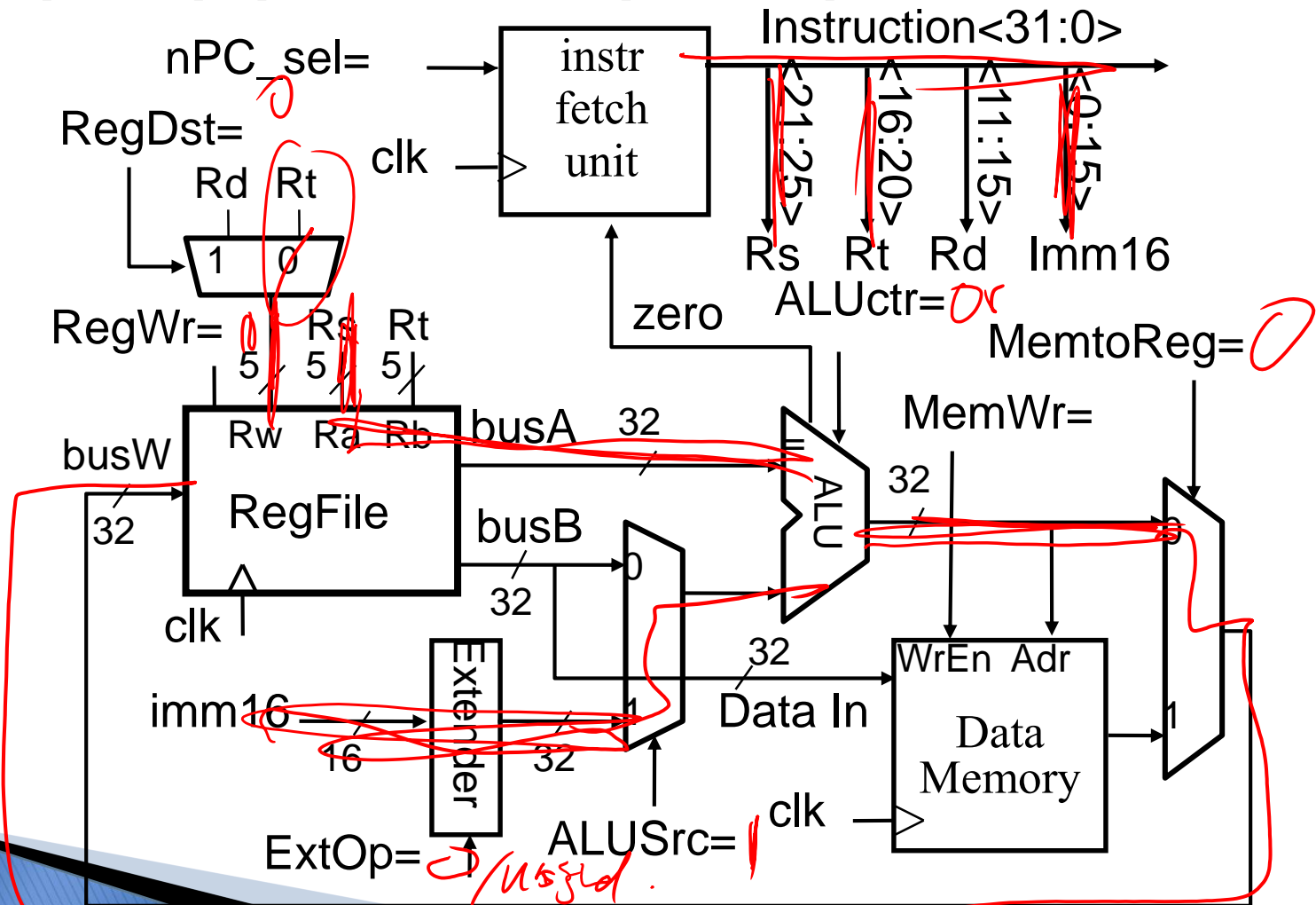►  $R[rt] = R[rs] \text{ OR } \text{ZeroExt}[\text{Imm16}]$







# Single Cycle Datapath for Ori

 

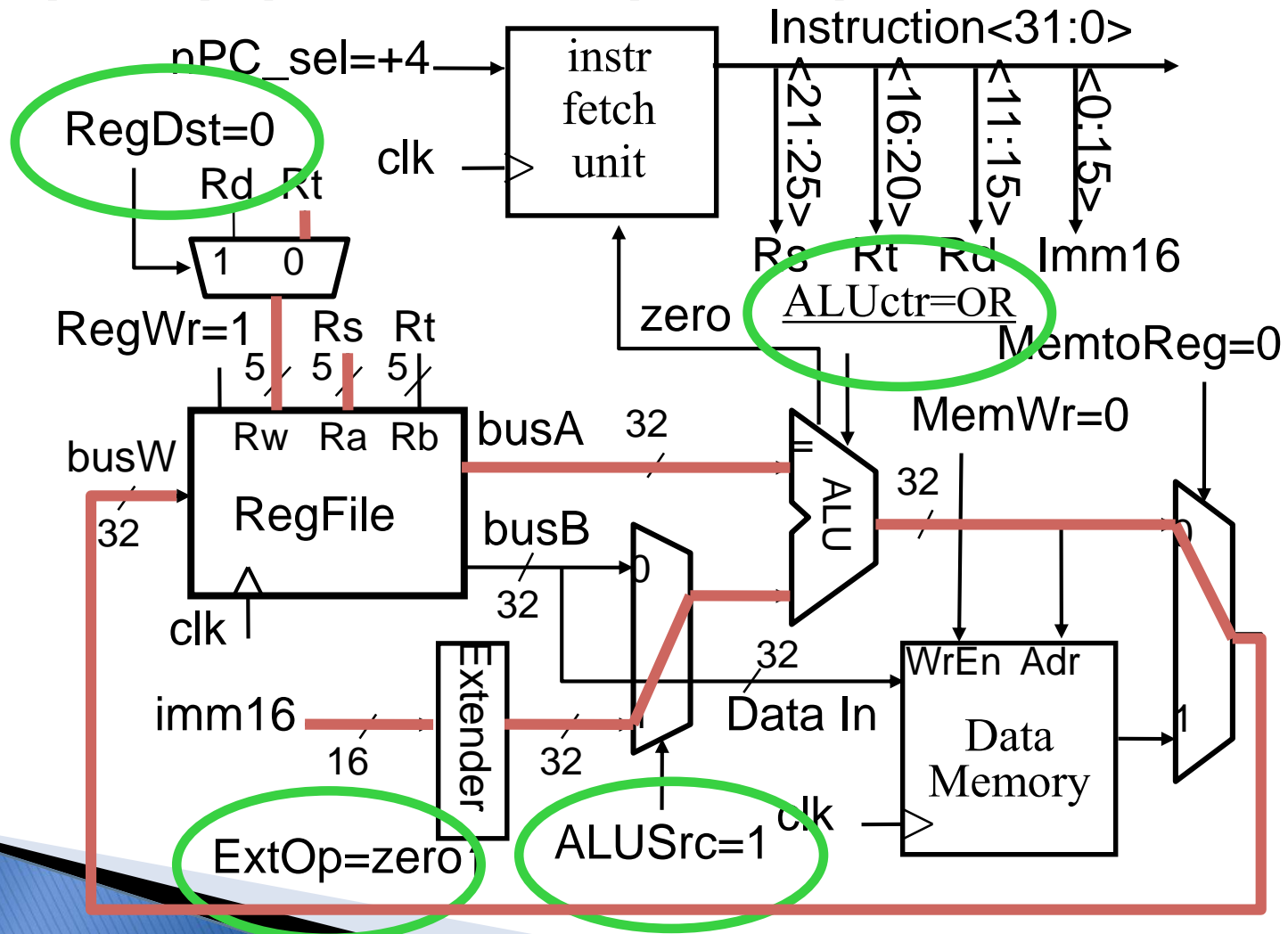
- ▶  $R[rt] = R[rs] \text{ OR } \text{ZeroExt}[\text{Imm16}]$




# Single Cycle Datapath for LW

 

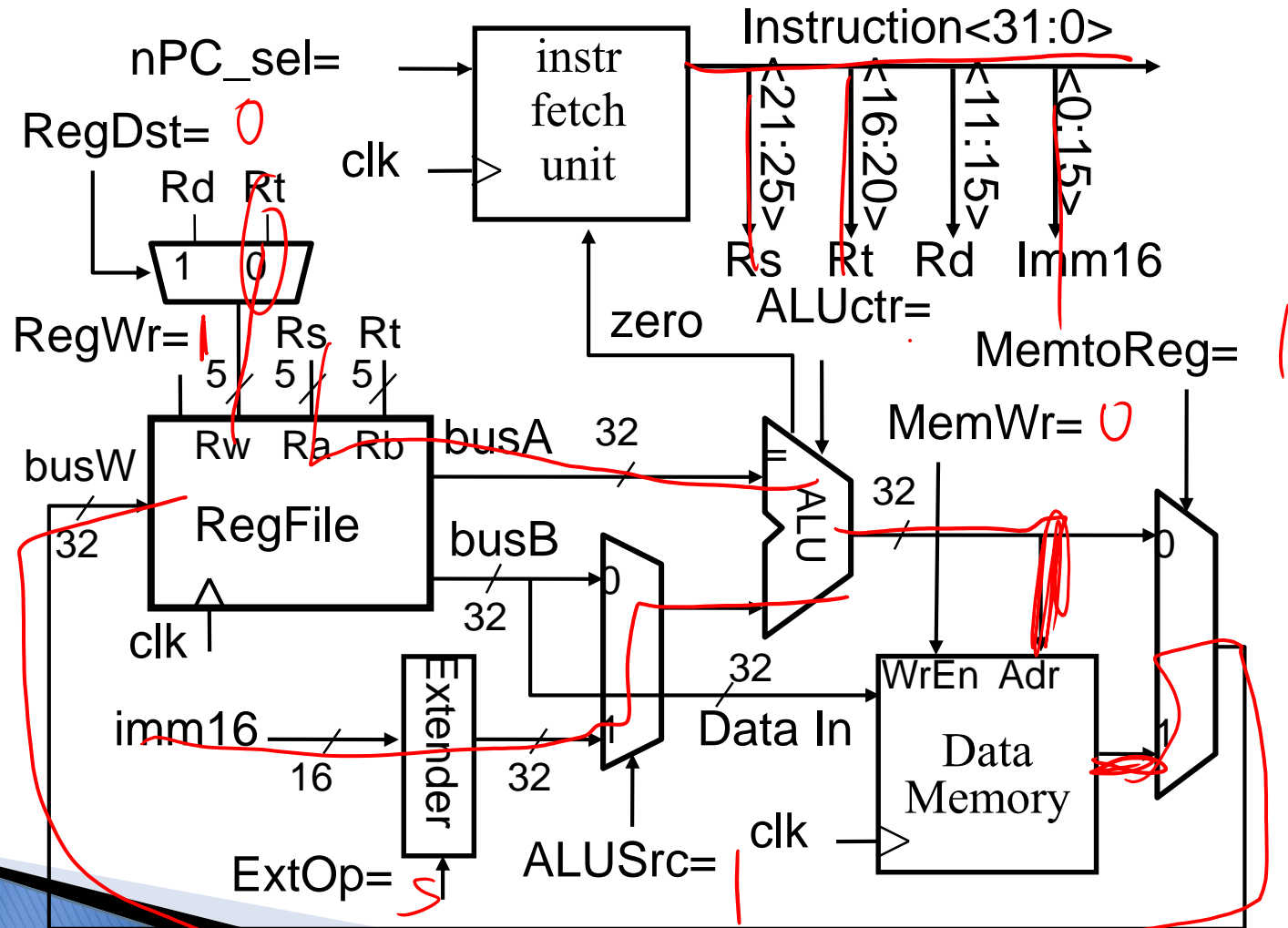
- ▶  $R[rt] = \text{Data Memory} \{R[rs] + \text{SignExt}[\text{imm16}]\}$




# Single Cycle Datapath for LW

 

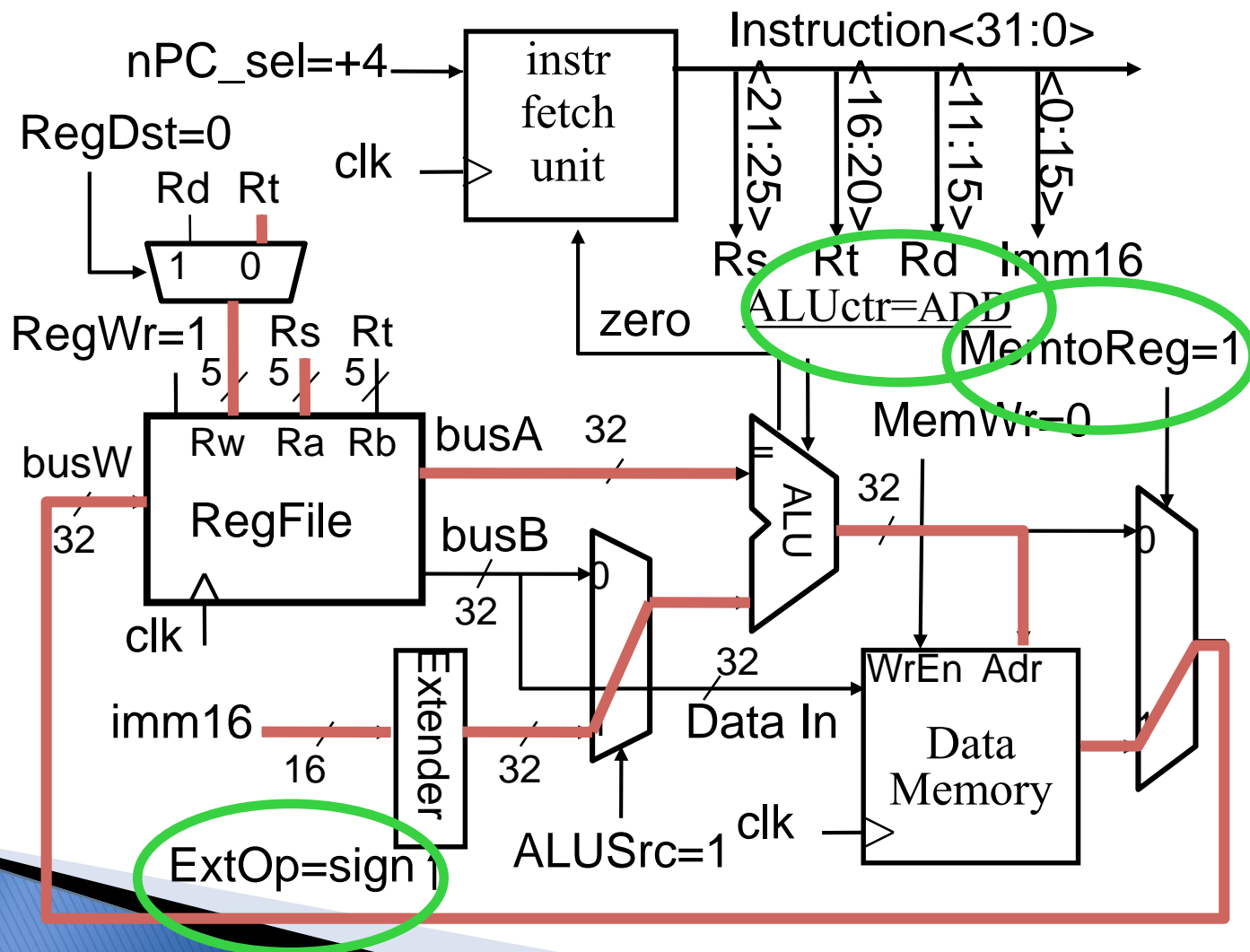
- ▶  $R[rt] = \text{Data Memory} \{R[rs] + \text{SignExt}[\text{imm16}]\}$




# Single Cycle Datapath for SW

 

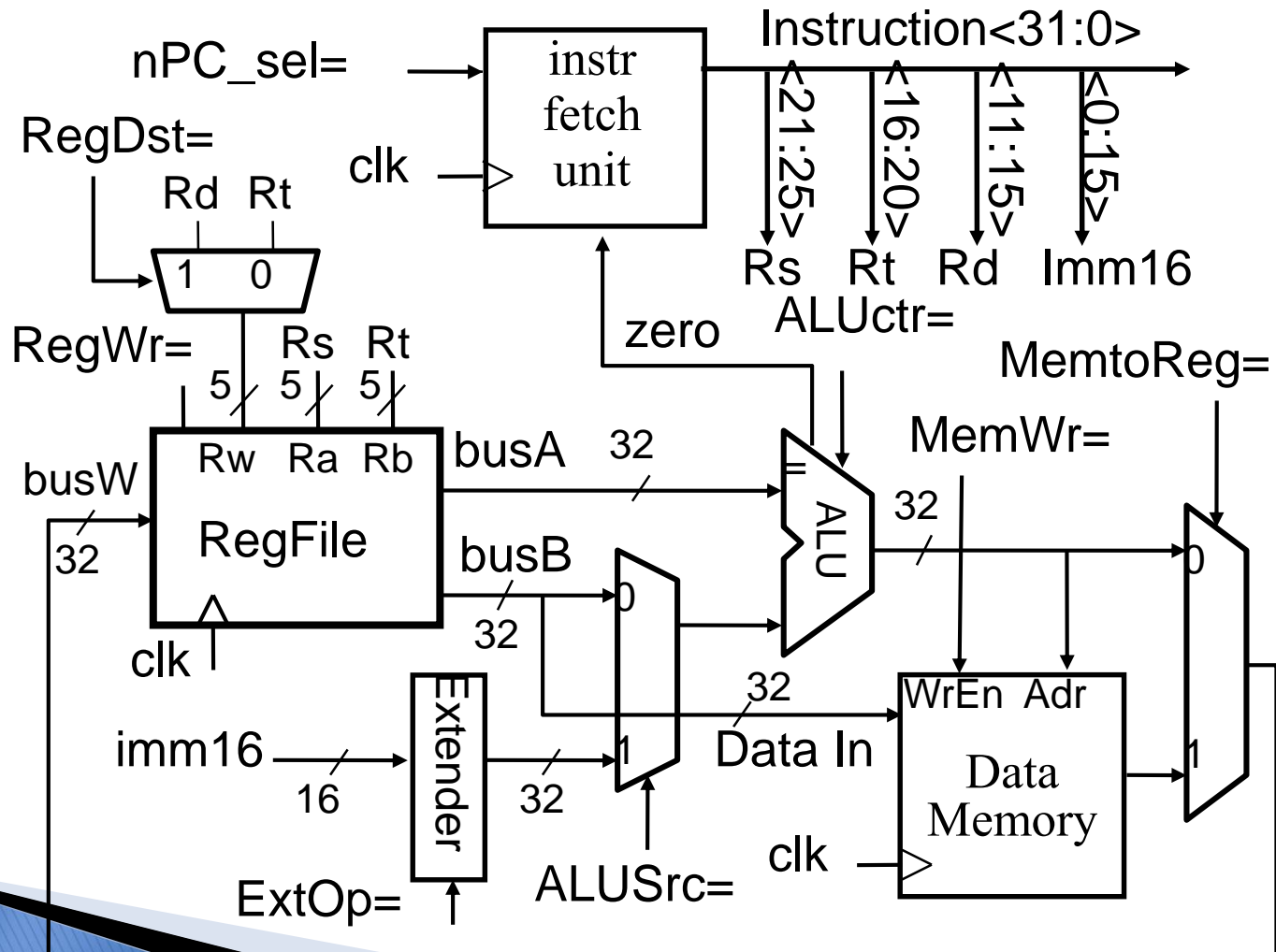
- ▶ Data Memory  $\{R[rs] + \text{SignExt}[imm16]\} = R[rt]$




# Single Cycle Datapath for SW

 

 
- ▶ Data Memory  $\{R[rs] + \text{SignExt}[imm16]\} = R[rt]$




# Single Cycle Datapath for Branch

 

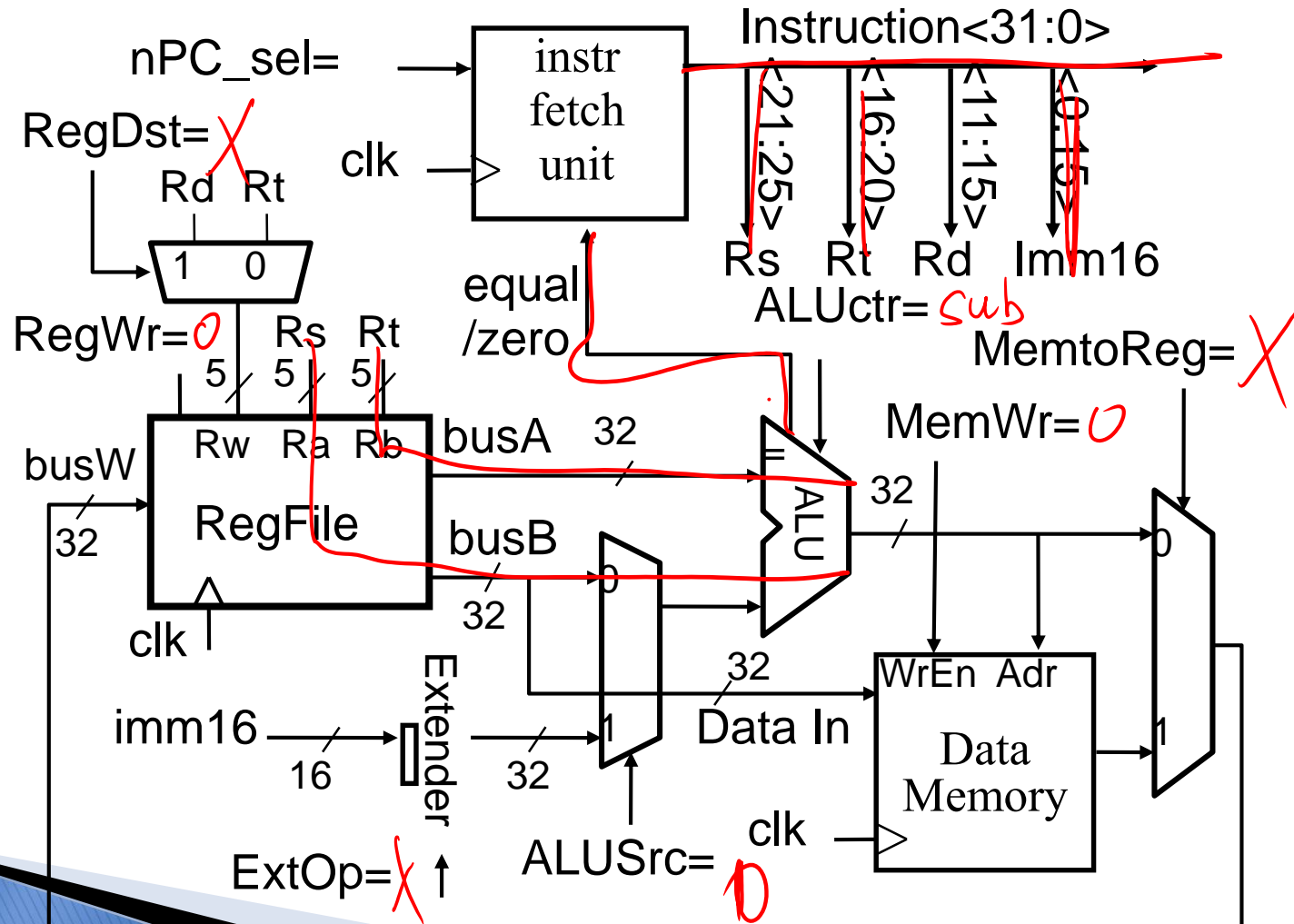
- if  $(R[rs] - R[rt] == 0)$  then Zero = 1 ; else Zero = 0




# Single Cycle Datapath for Branch

 

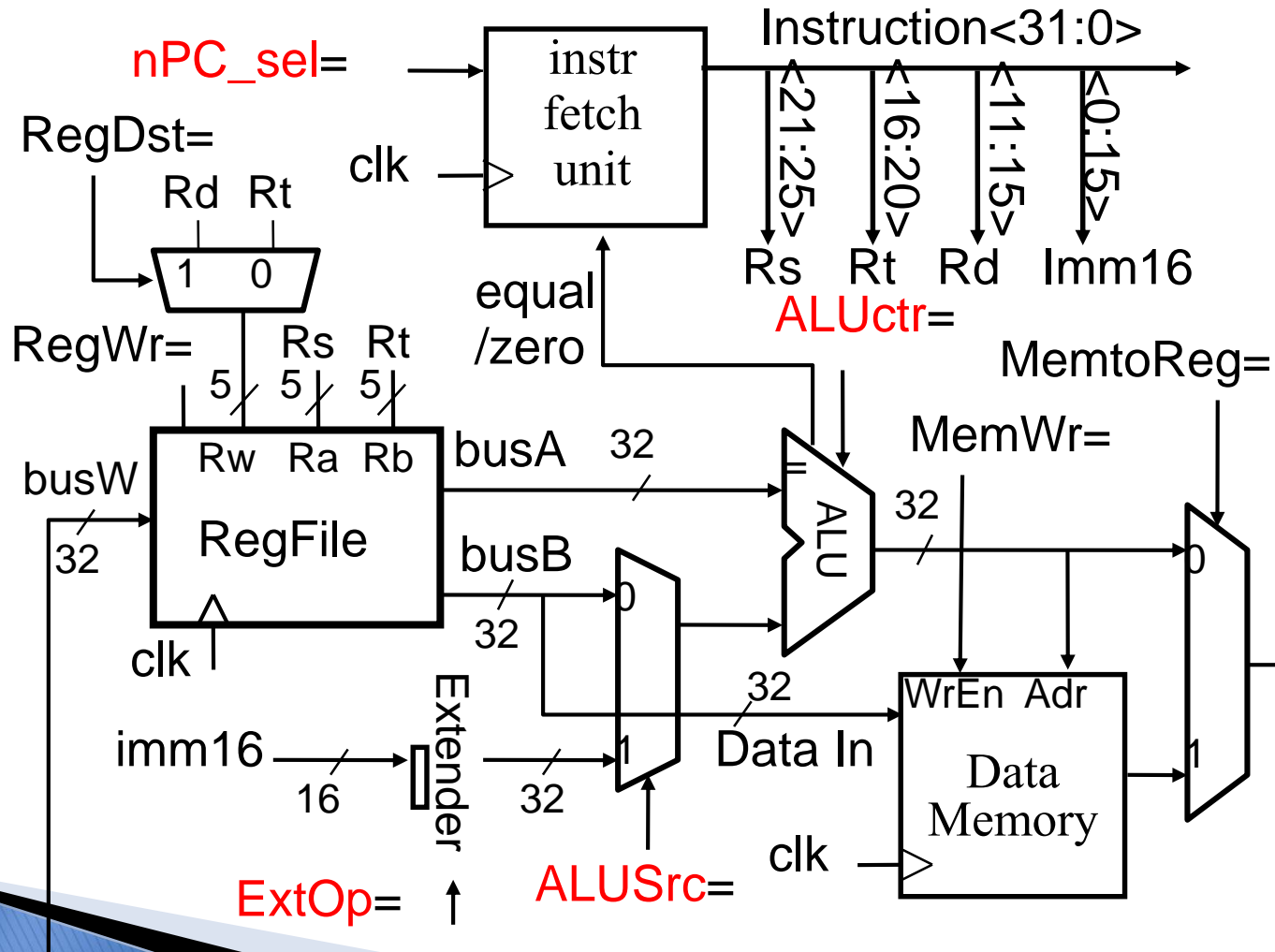
- ▶ if  $(R[rs] - R[rt] == 0)$  then Zero = 1 ; else Zero = 0



# Single Cycle Datapath for Branch

 


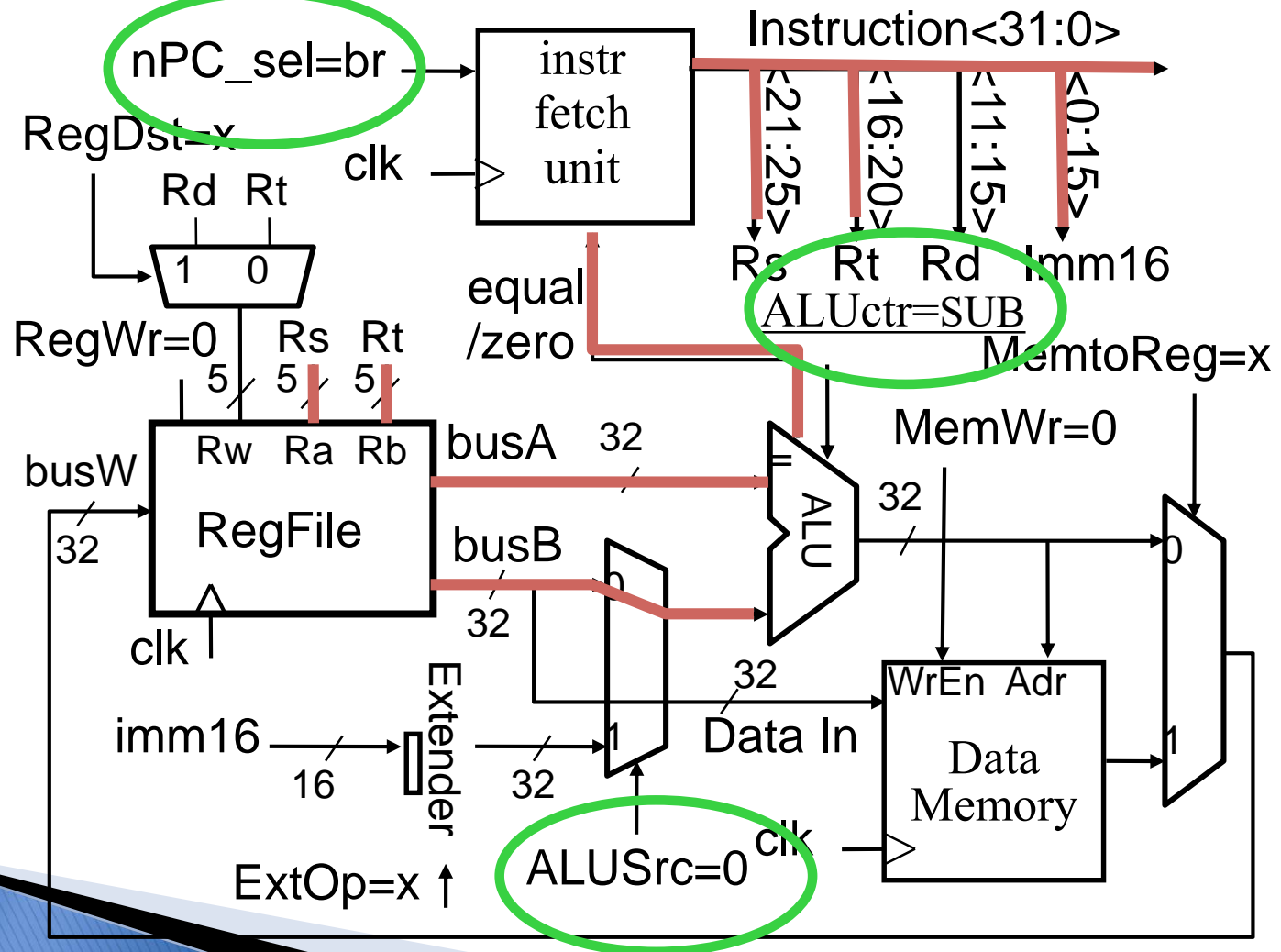- if  $(R[rs] - R[rt] == 0)$  then Zero = 1 ; else Zero = 0






# Instruction Fetch Unit end of Branch

 

 - ▶ if (Zero == 1) then  $PC = PC + 4 + \text{SignExt}[\text{imm16}] * 4$ ; else  $PC = PC + 4$



- What is encoding of nPC\_sel?
  - **Direct MUX select?**
  - **Branch inst. / not branch**
- Let's pick 2nd option


*is a branch statement*

Q: What logic gate?


nPC_sel	zero?	MUX
0	x	0
1	0	0
1	1	1




# The Single Cycle Datapath during Jump

 

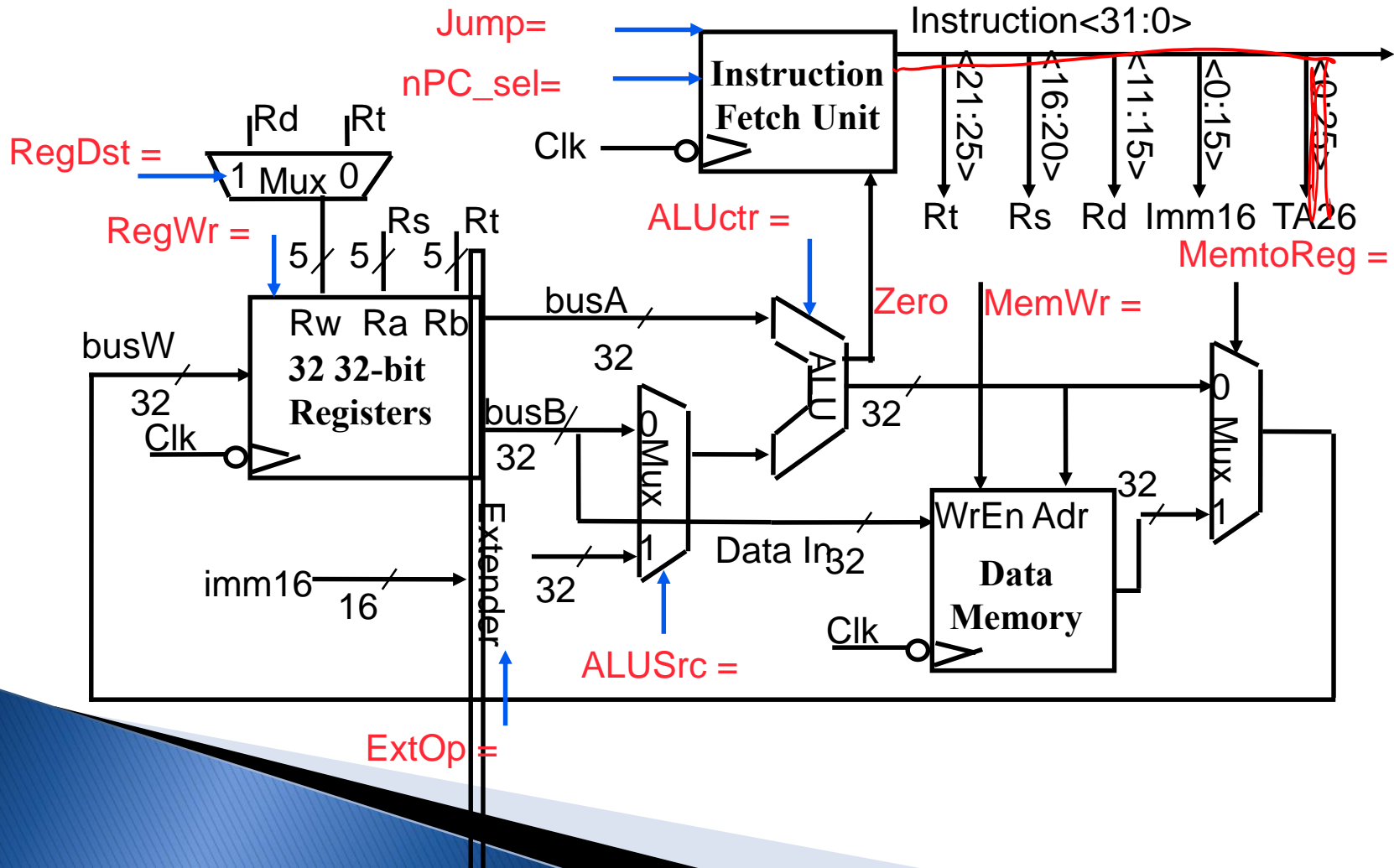
- **New PC = { PC[31..28], target address, 00 }**




# The Single Cycle Datapath during Jump

 

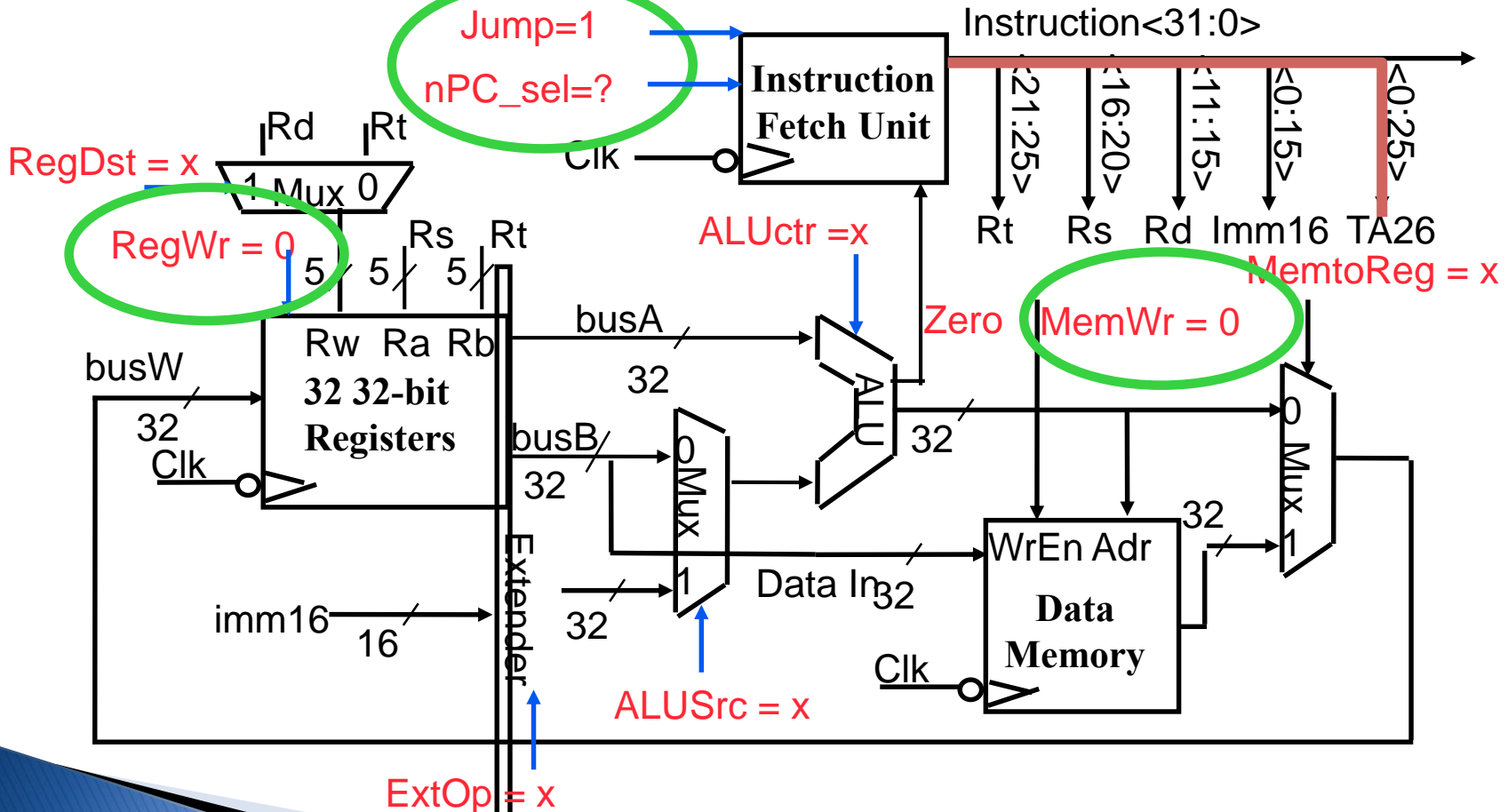
- New PC = { PC[31..28], target address, 00 }


 
# Instruction Fetch Unit at the End of Jump




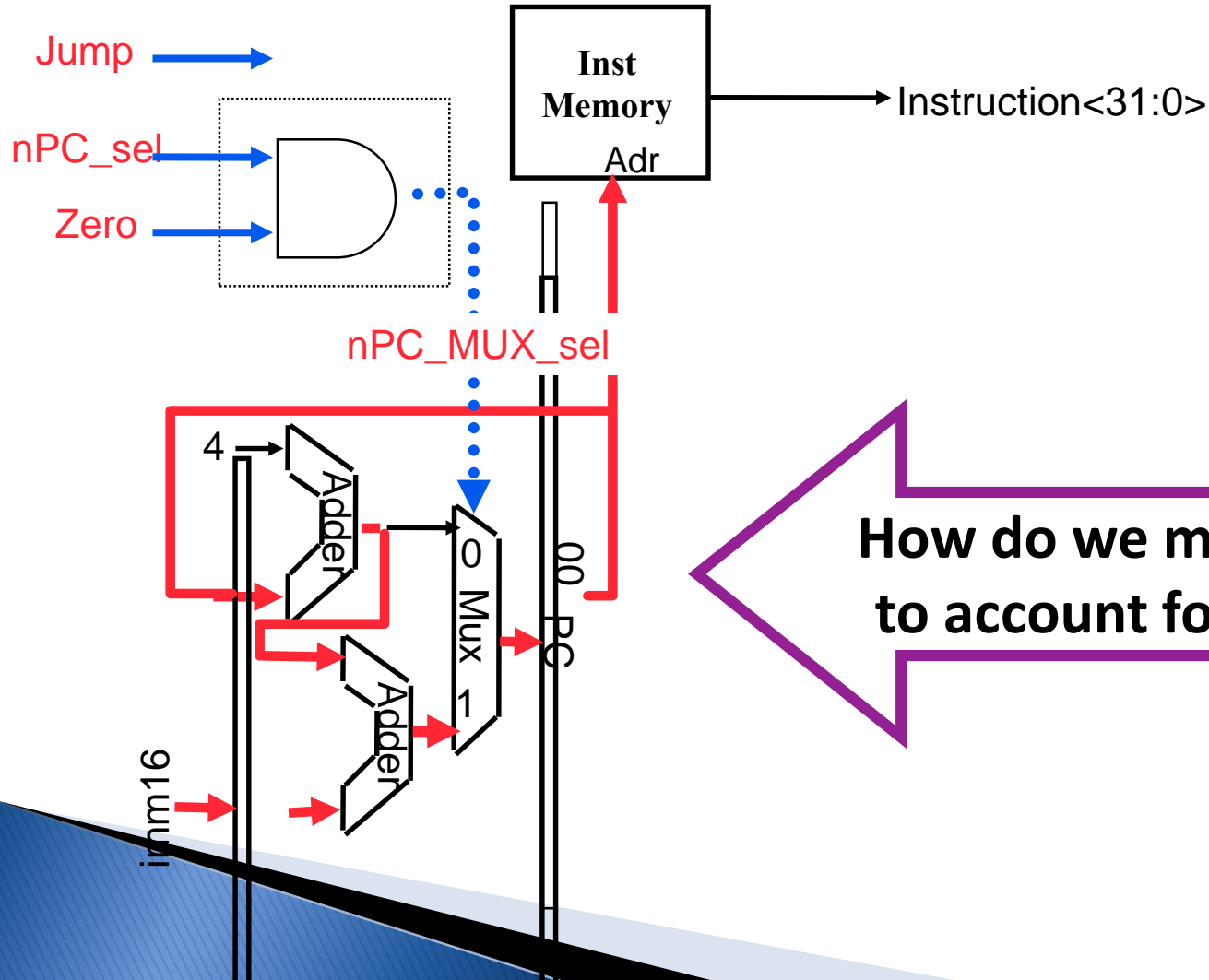- **New PC = { PC[31..28], target address, 00 }**



How do we modify this to account for jumps?
 
# Instruction Fetch Unit at the End of Jump



- **New PC = { PC[31..28], target address, 00 }**

