

# CSE 31

# Computer Organization

Lecture 23 – CPU Design (3)

# Announcement


- ▶ Lab #10
  - Due in 1 week
- ▶ HW #7 in CatCourses
  - Due Monday (5/6) at 11:59pm
- ▶ HW #8 in zyBooks (Through CatCourses)
  - Due Saturday (5/11) at 11:59pm
- ▶ Reading assignment
  - Chapter 5.7-5.11 of zyBooks
    - Make sure to do the Participation Activities
    - Due Friday (5/3) at 11:59pm
- ▶ Course evaluation online by 5/9

# Announcement

## ► Final Exam


- 5/11 (Saturday), 11:30am – 2:30pm
- Cover all
- Practice exam in CatCourses
- Closed book
- 2 sheet of note (8.5" x 11")
- MIPS reference sheet will be provided
- Review: 5/10 (Friday) 2-4pm, COB2 140

# Generic Steps of Datapath

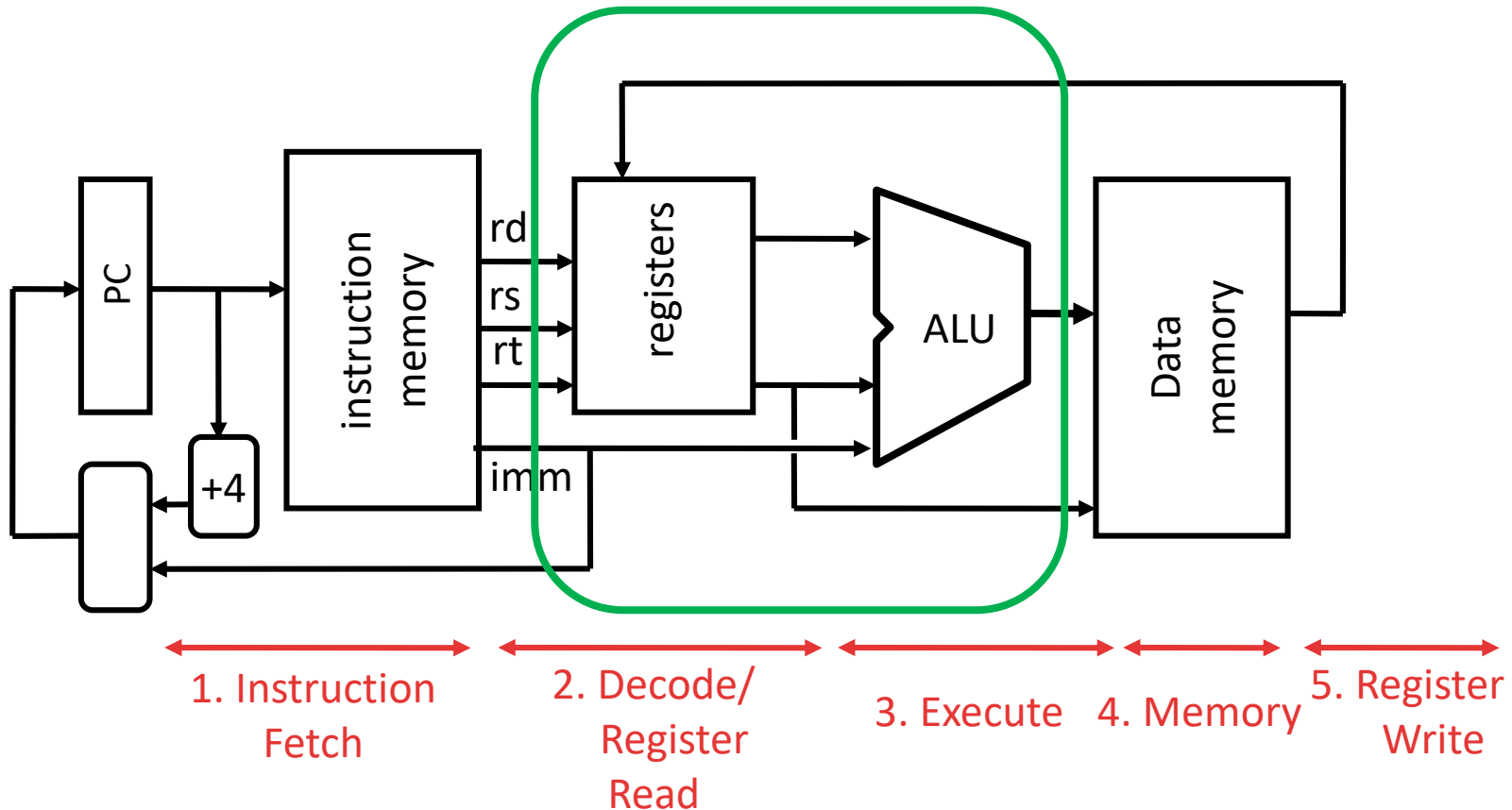

How do we handle the different register usage between r-type and i-type instructions?


# A zoomed in version of RegFile and ALU

 

# Load Memory

►  $R[\underline{rt}] = \text{Mem}[R[rs] + \text{SignExt}[\text{imm16}]]$


► Example: `lw rt, rs, imm16`

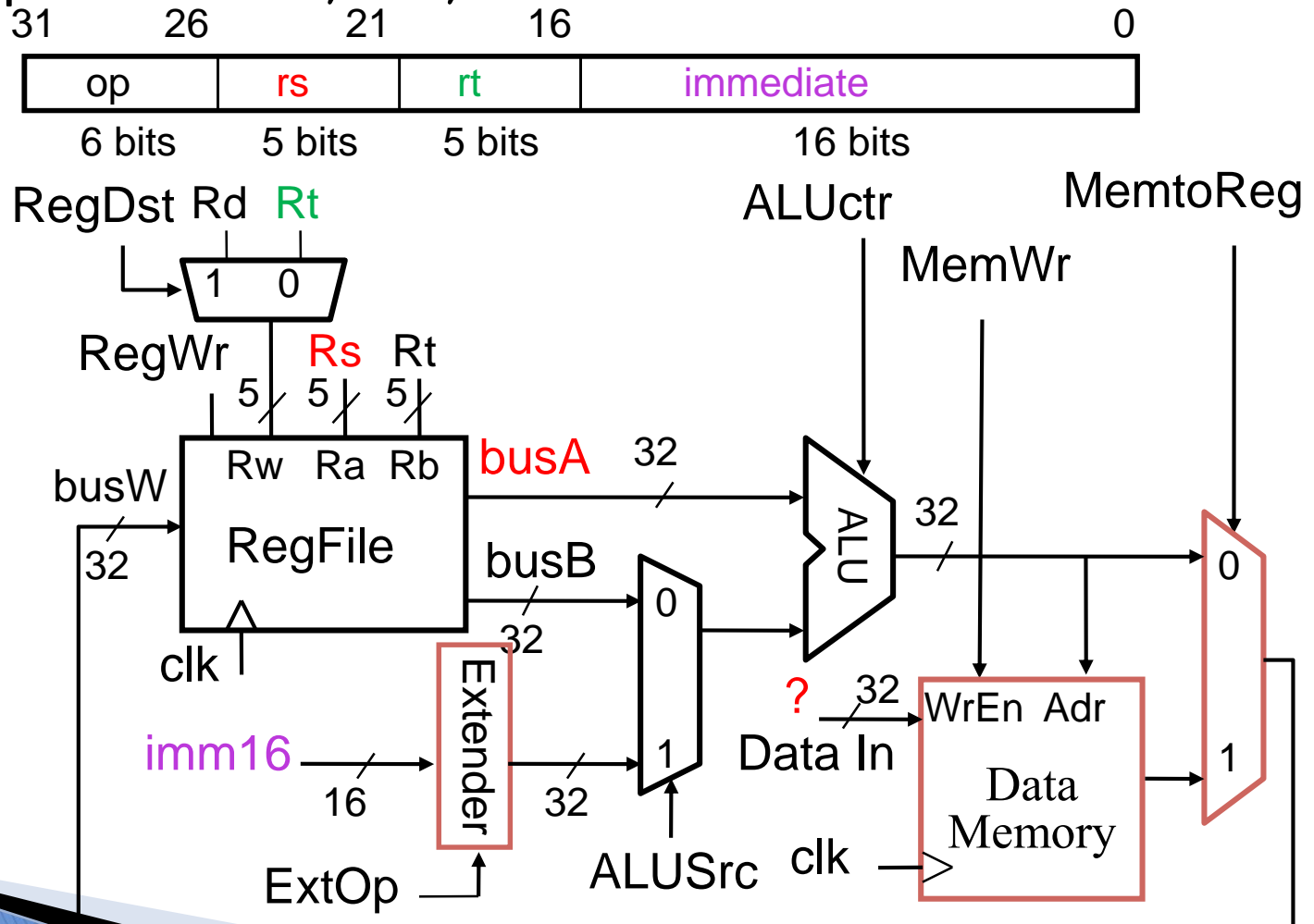

# Store Memory

- ▶  $\text{Mem}[ \text{R}[\text{rs}] + \text{SignExt}[\text{imm16}] ] = \text{R}[\text{rt}]$



Ex.: `sw rt, rs, imm16`

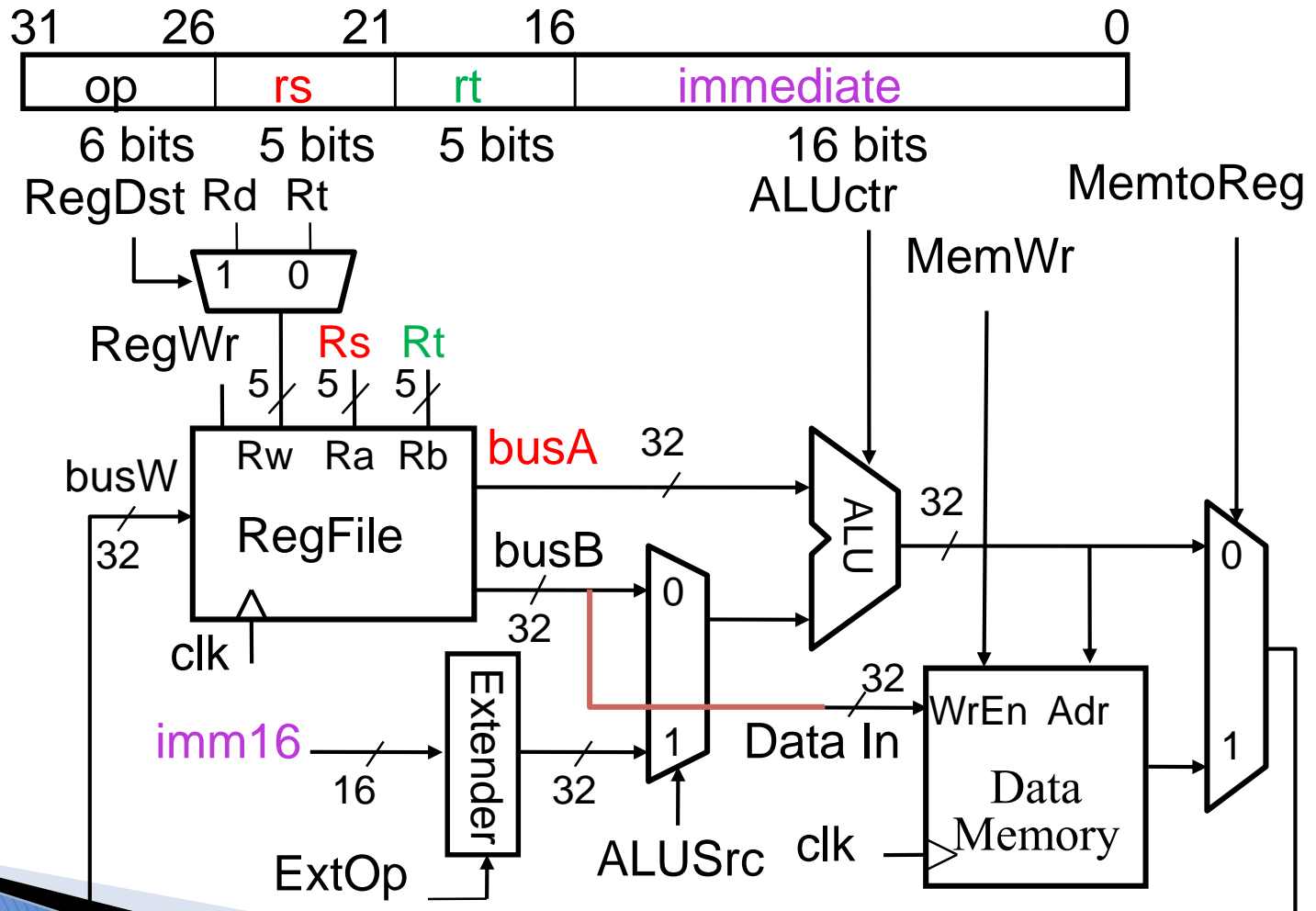

# Datapath for Branch Operations

- ▶ beq rs, rt, imm16

Datapath generates condition (equal)

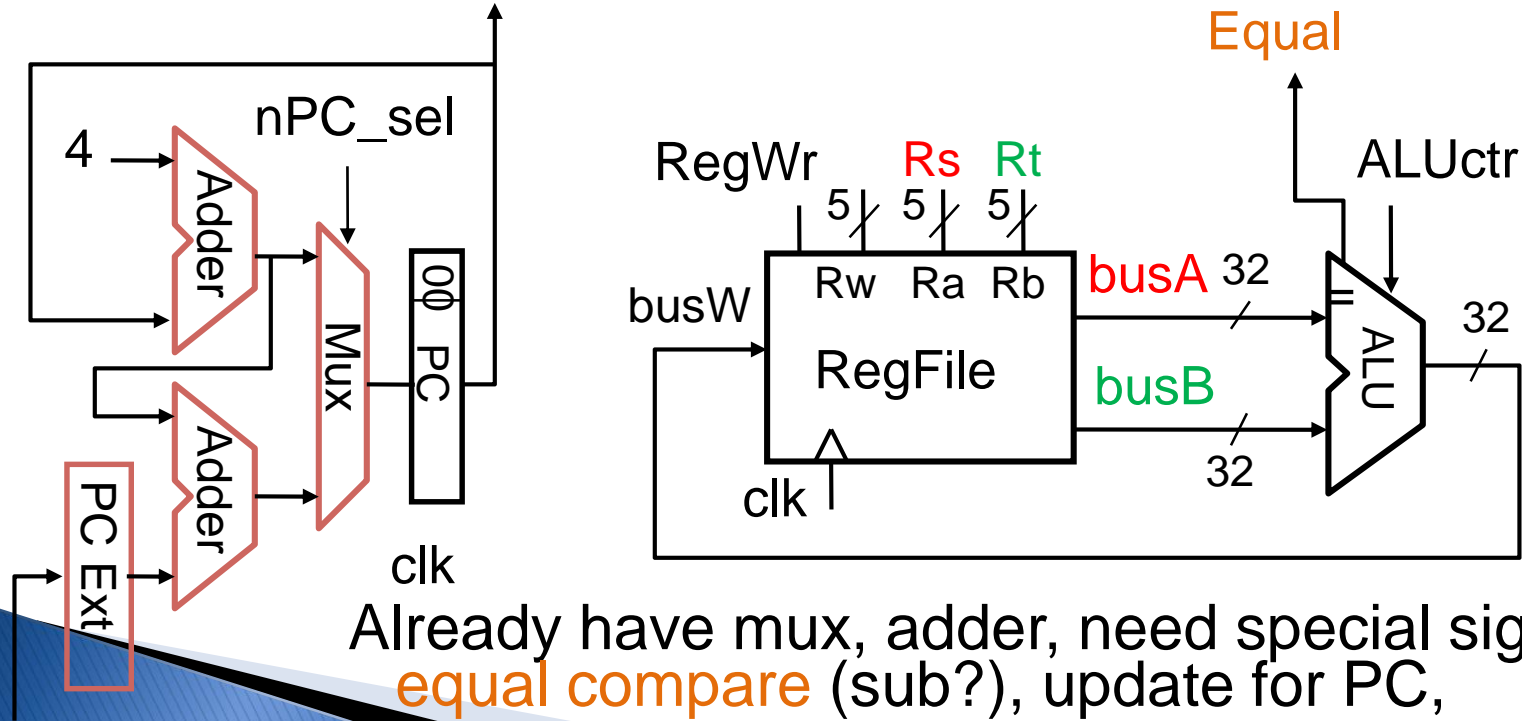 


Already have mux, adder, need special sign need  
equal compare (sub?), update for PC,


imm16



# Single Cycle Datapath

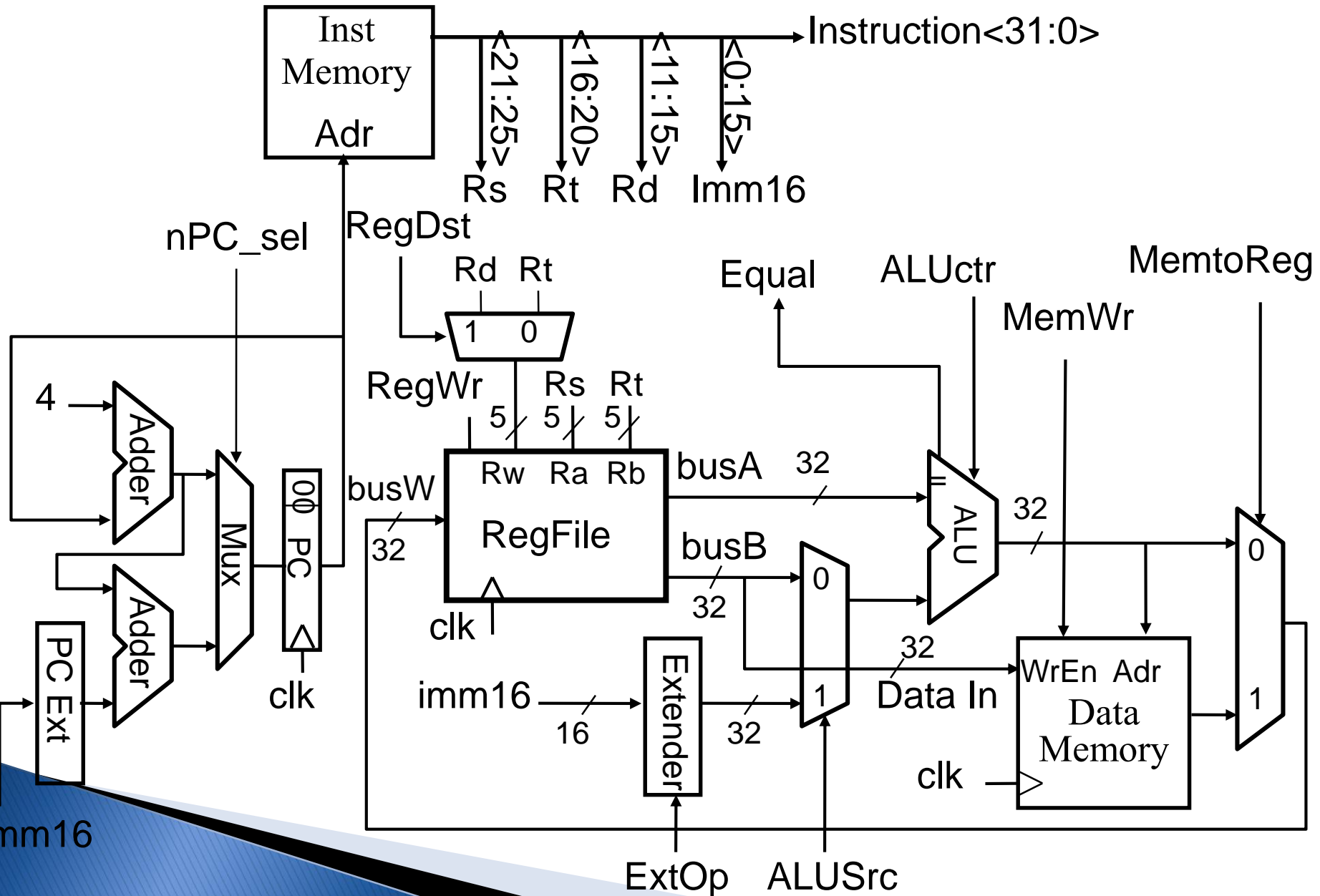


# Abstract View of the Implementation

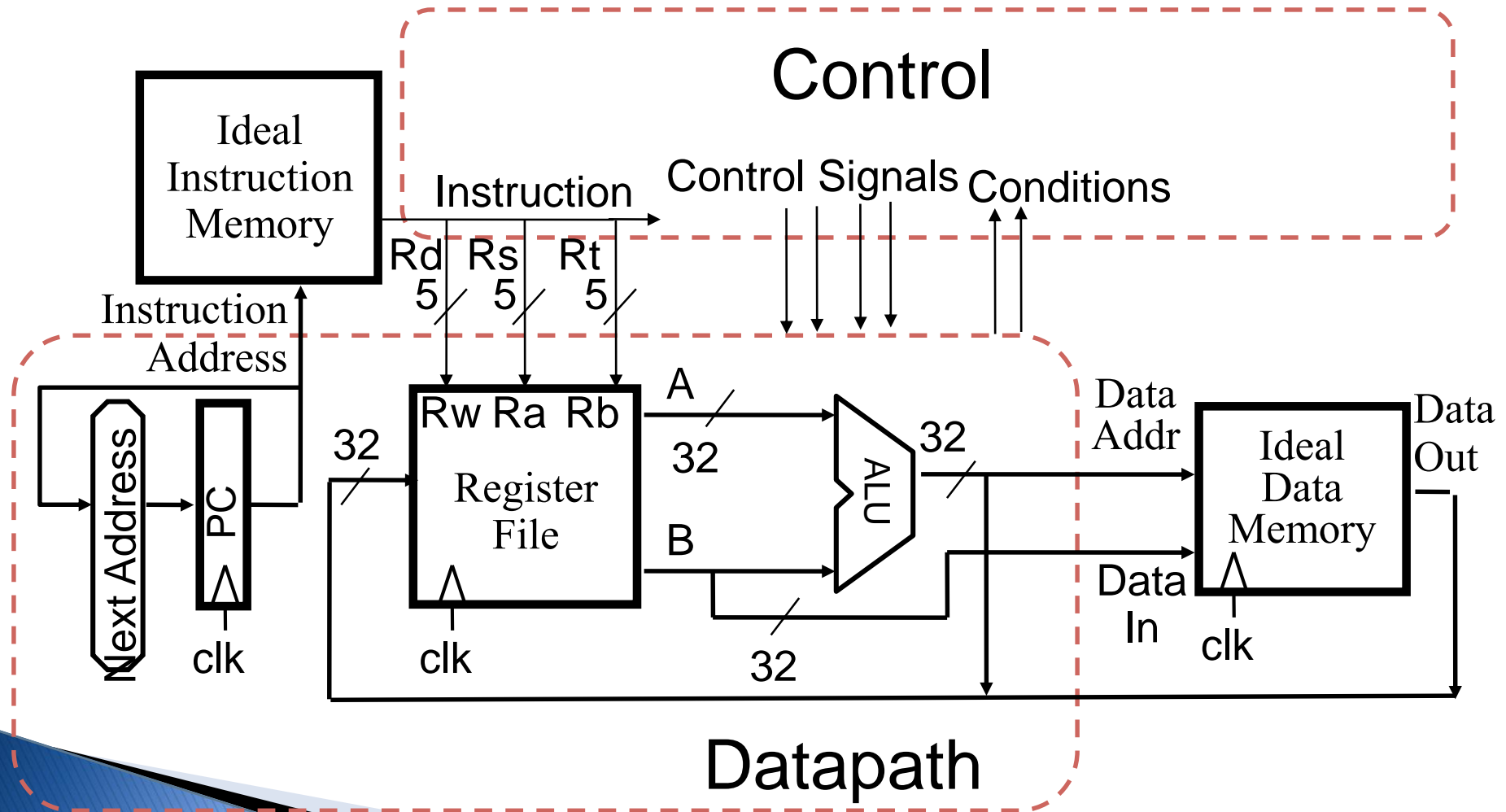
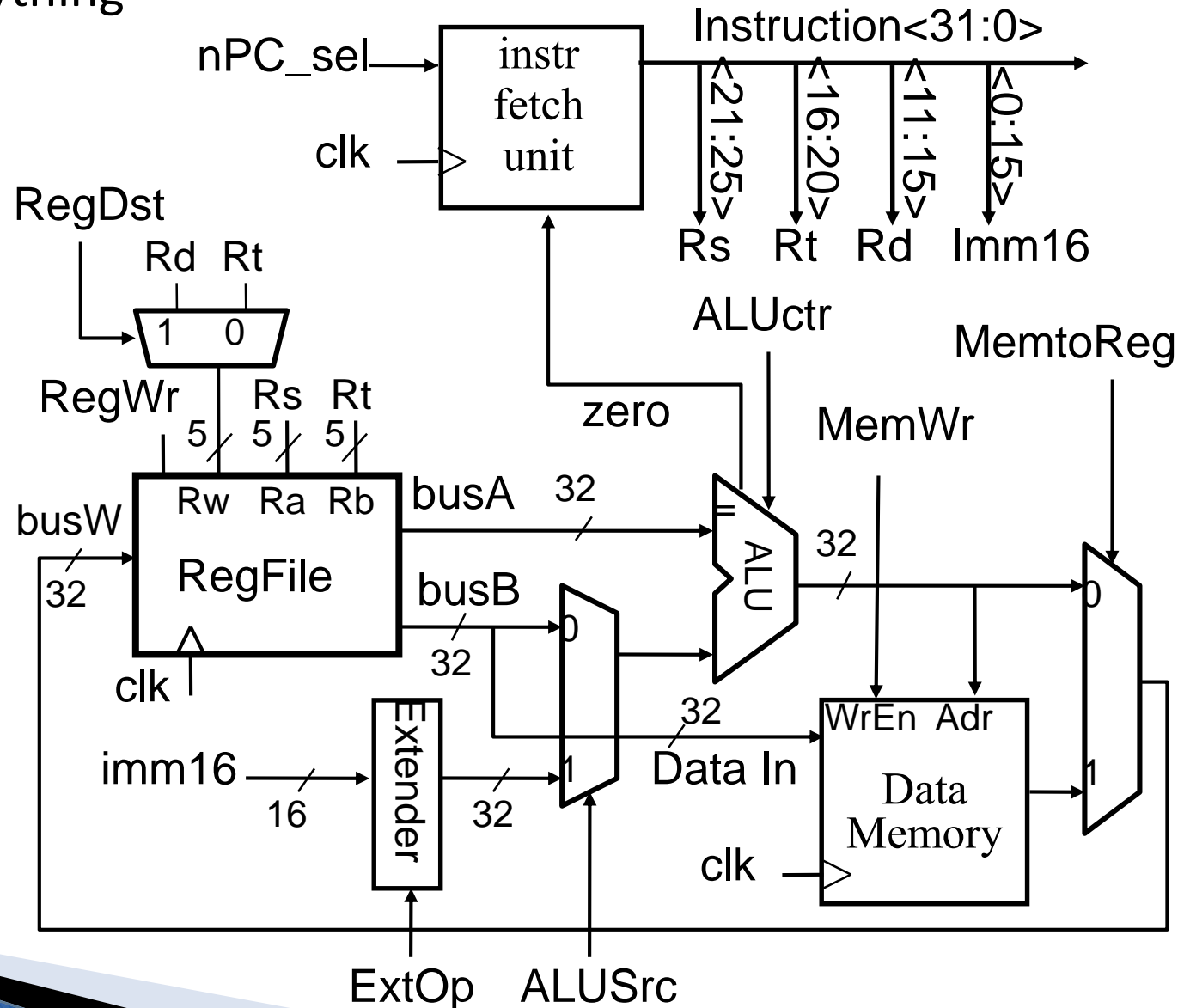
# A Single Cycle Datapath


- ▶ We have everything except control signals


 
# Meaning of the Control Signals


- ▶ `nPC_sel`: “+4”:  $0 \Rightarrow PC \leftarrow PC + 4$   
“br”:  $1 \Rightarrow PC \leftarrow PC + 4 + \{ \text{SignExt}(\text{Imm16}), 00 \}$   
“n”=next

- ▶ Later in lecture: higher-level connection between mux and branch condition



 
# Meaning of the Control Signals

- ▶ **ExtOp**: “zero”, “sign”
- ▶ **ALUsrc**: 0  $\Rightarrow$  regB; 1  $\Rightarrow$  immedi
- ▶ **ALUctr**: “ADD”, “SUB”, “OR”
- **MemWr**: 1  $\Rightarrow$  write memory
- **MemtoReg**: 0  $\Rightarrow$  ALU; 1  $\Rightarrow$  Mem
- **RegDst**: 0  $\Rightarrow$  “rt”; 1  $\Rightarrow$  “rd”
- **RegWr**: 1  $\Rightarrow$  write register



# The Add Instruction

 

add rd, rs, rt


- MEM[PC]                      Fetch the instruction from memory
- $R[rd] = R[rs] + R[rt]$       The actual operation
- $PC = PC + 4$  Calculate the next instruction's address

# Instruction Fetch Unit start of Add


- Fetch the instruction from Instruction memory:

Instruction = MEM[PC]


- same for all instructions

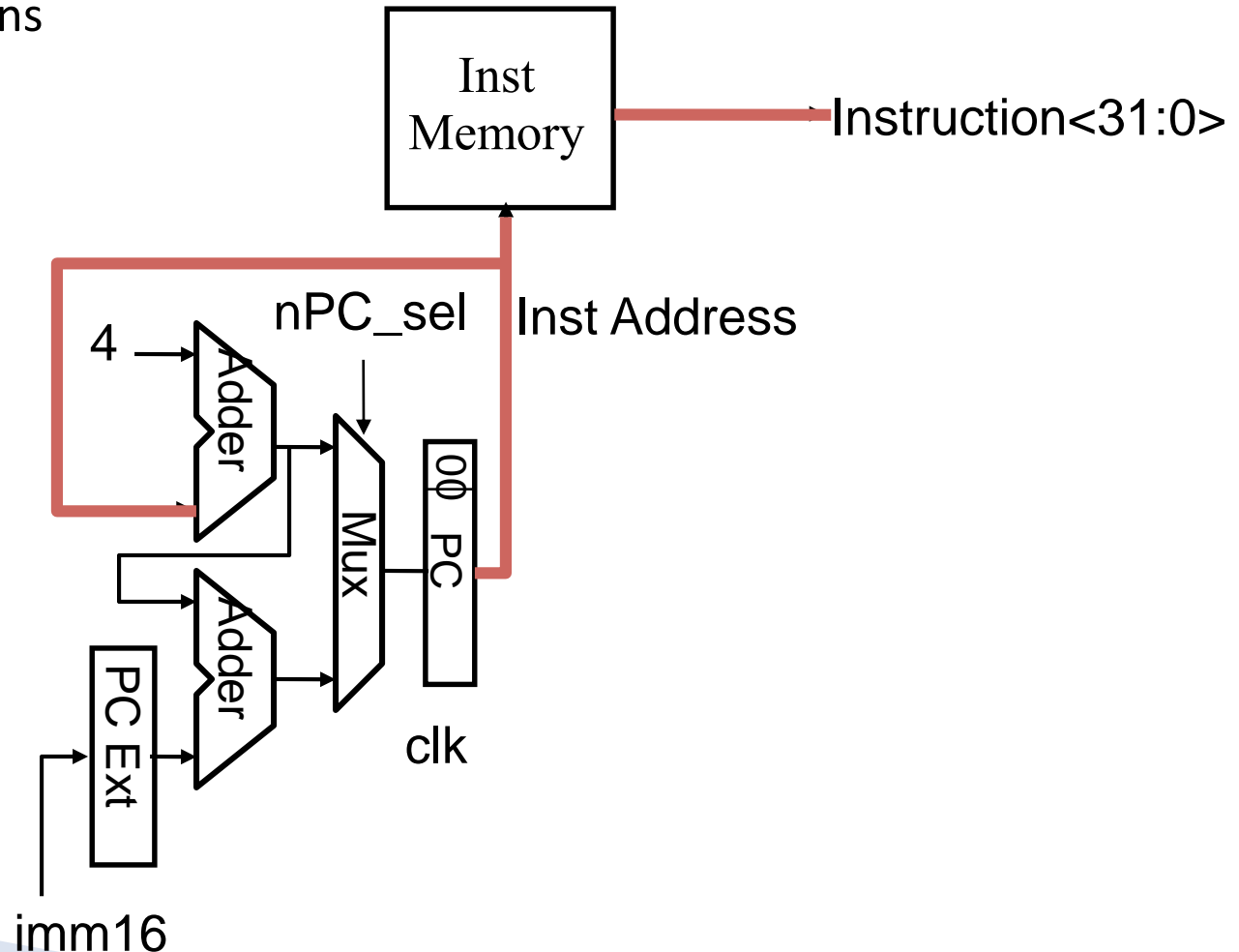

# The Single Cycle Datapath during Add

 


$$R[rd] = R[rs] + R[rt]$$

 



 
# Instruction Fetch Unit end of Add


- ▶  $PC = PC + 4$ 
  - This is the same for all instructions except: Branch and Jump




# Single Cycle Datapath for Ori

 

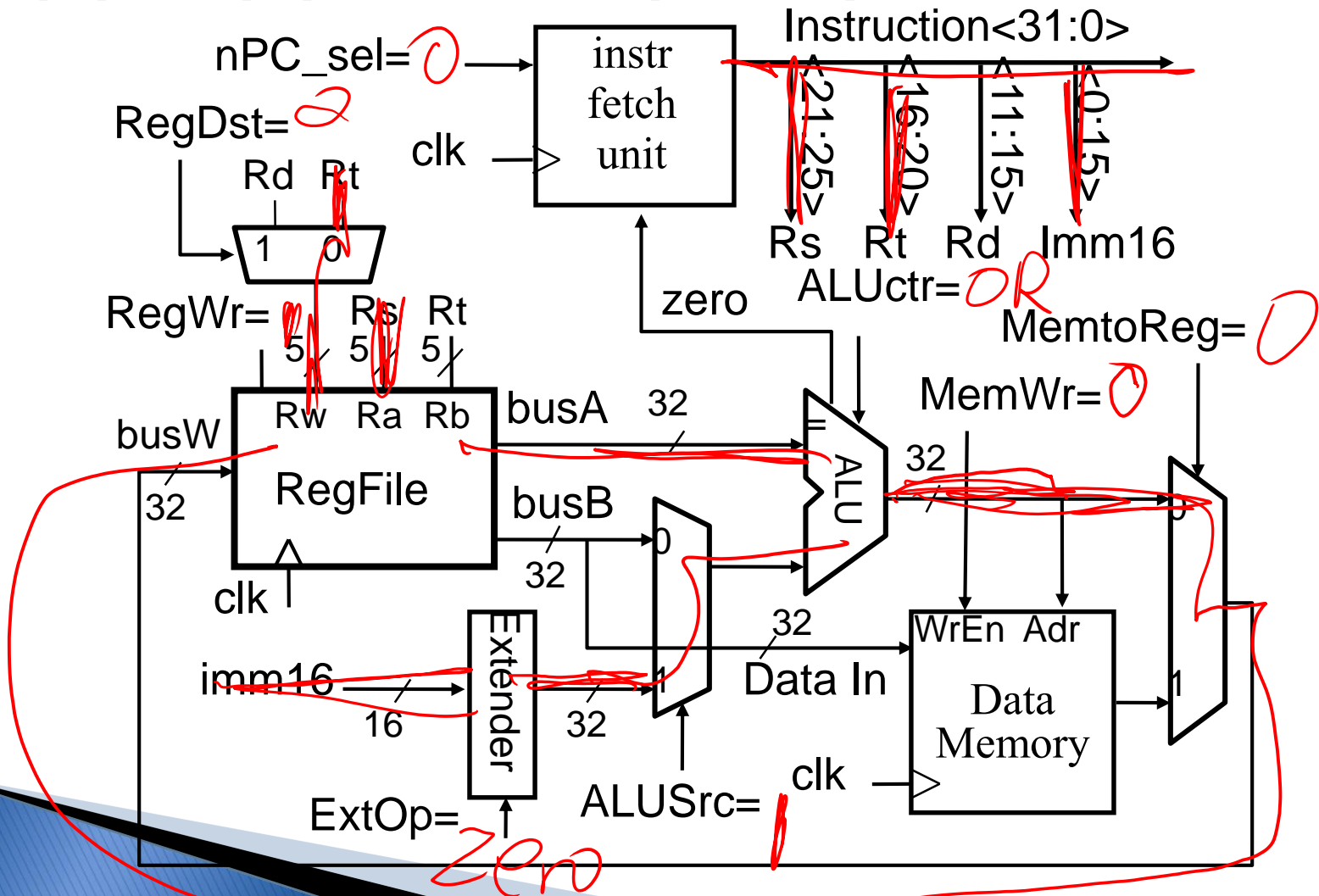
►  $R[rt] = R[rs] \text{ OR } \text{ZeroExt}[\text{Imm16}]$




# Single Cycle Datapath for Ori

 

 
►  $R[rt] = R[rs] \text{ OR } \text{ZeroExt}[\text{Imm16}]$




# Single Cycle Datapath for LW

 

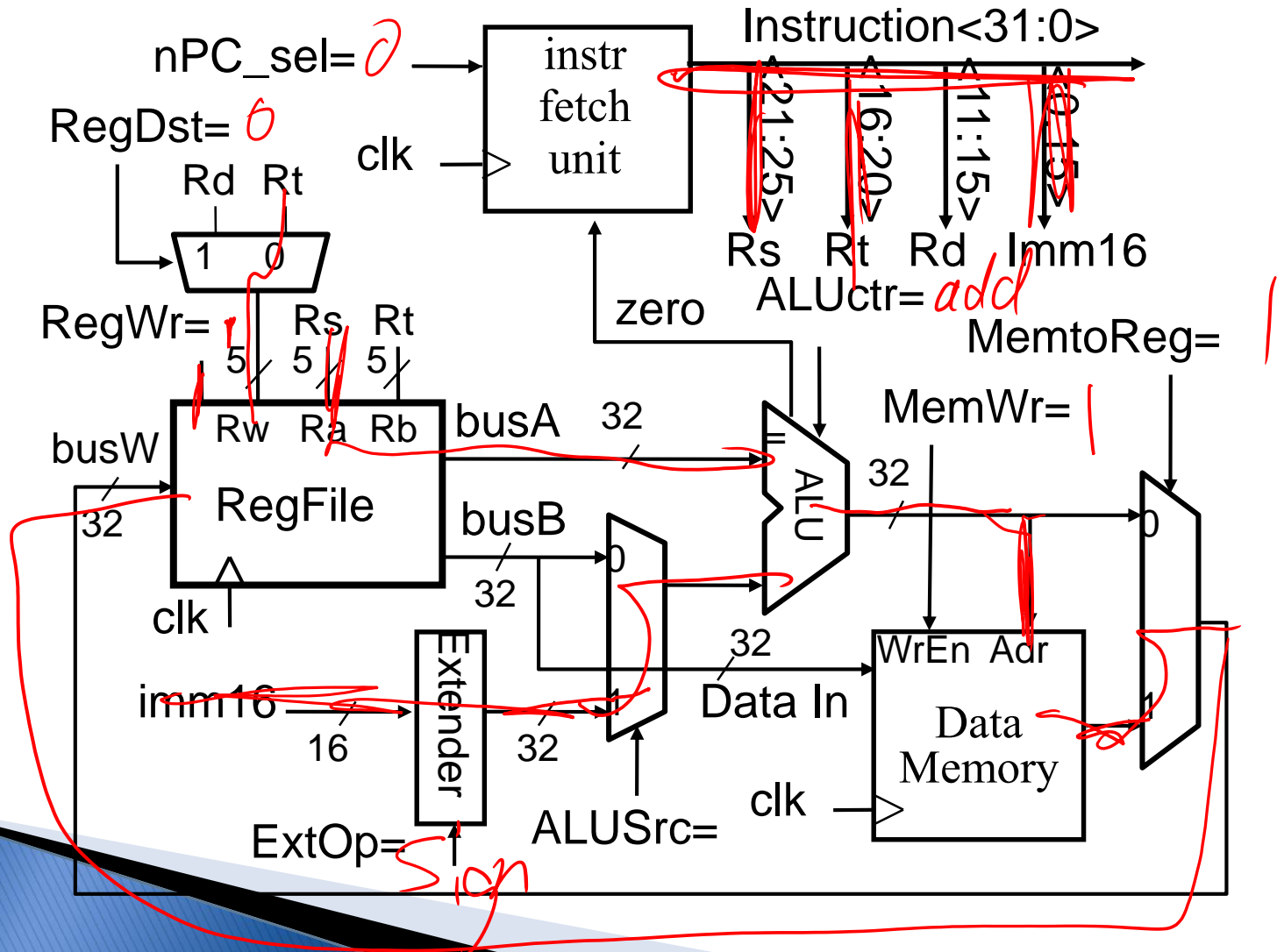
- ▶  $R[rt] = \text{Data Memory} \{R[rs] + \text{SignExt}[\text{imm16}]\}$




# Single Cycle Datapath for LW

 

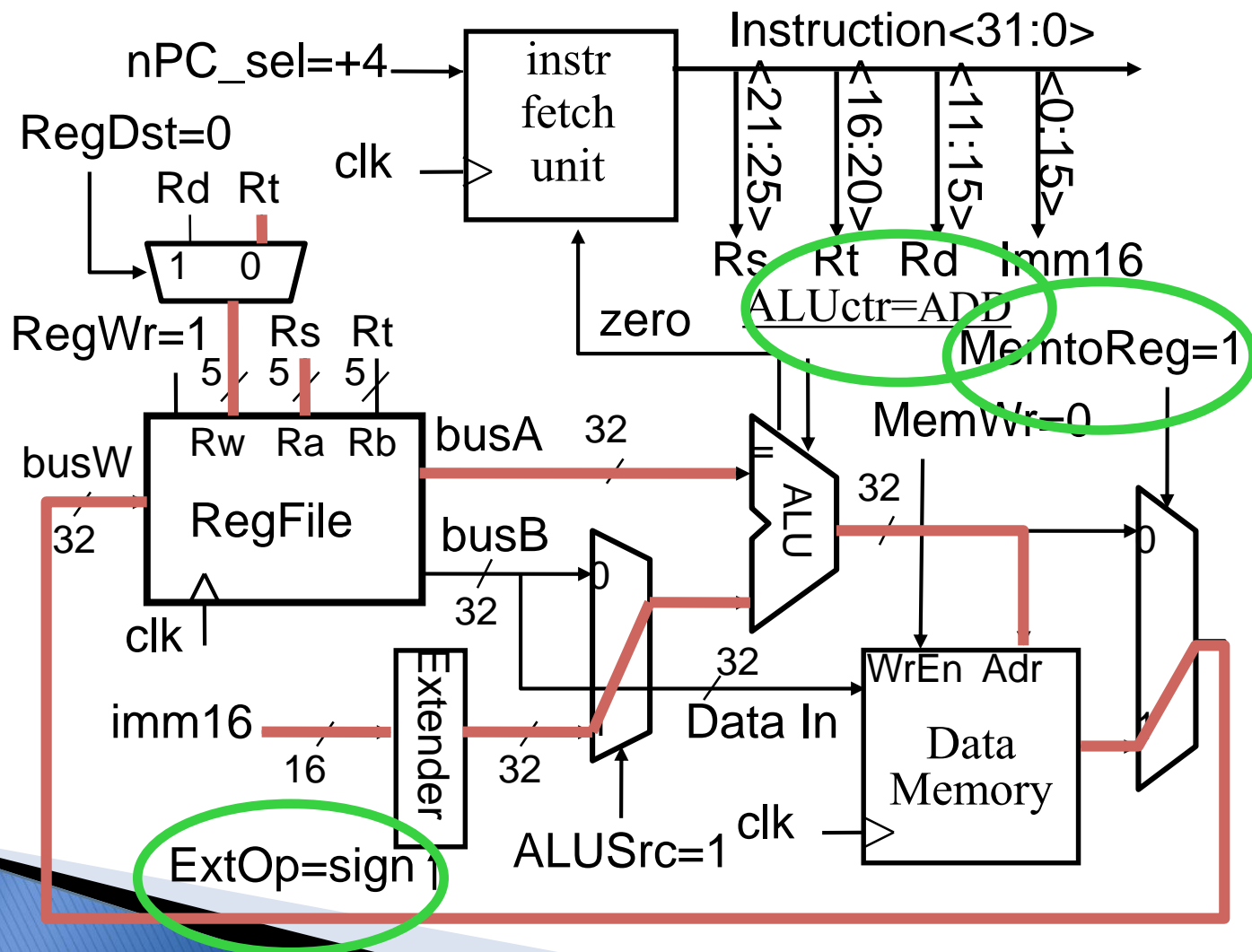
- ▶  $R[rt] = \text{Data Memory} \{R[rs] + \text{SignExt}[\text{imm16}]\}$




# Single Cycle Datapath for SW

 

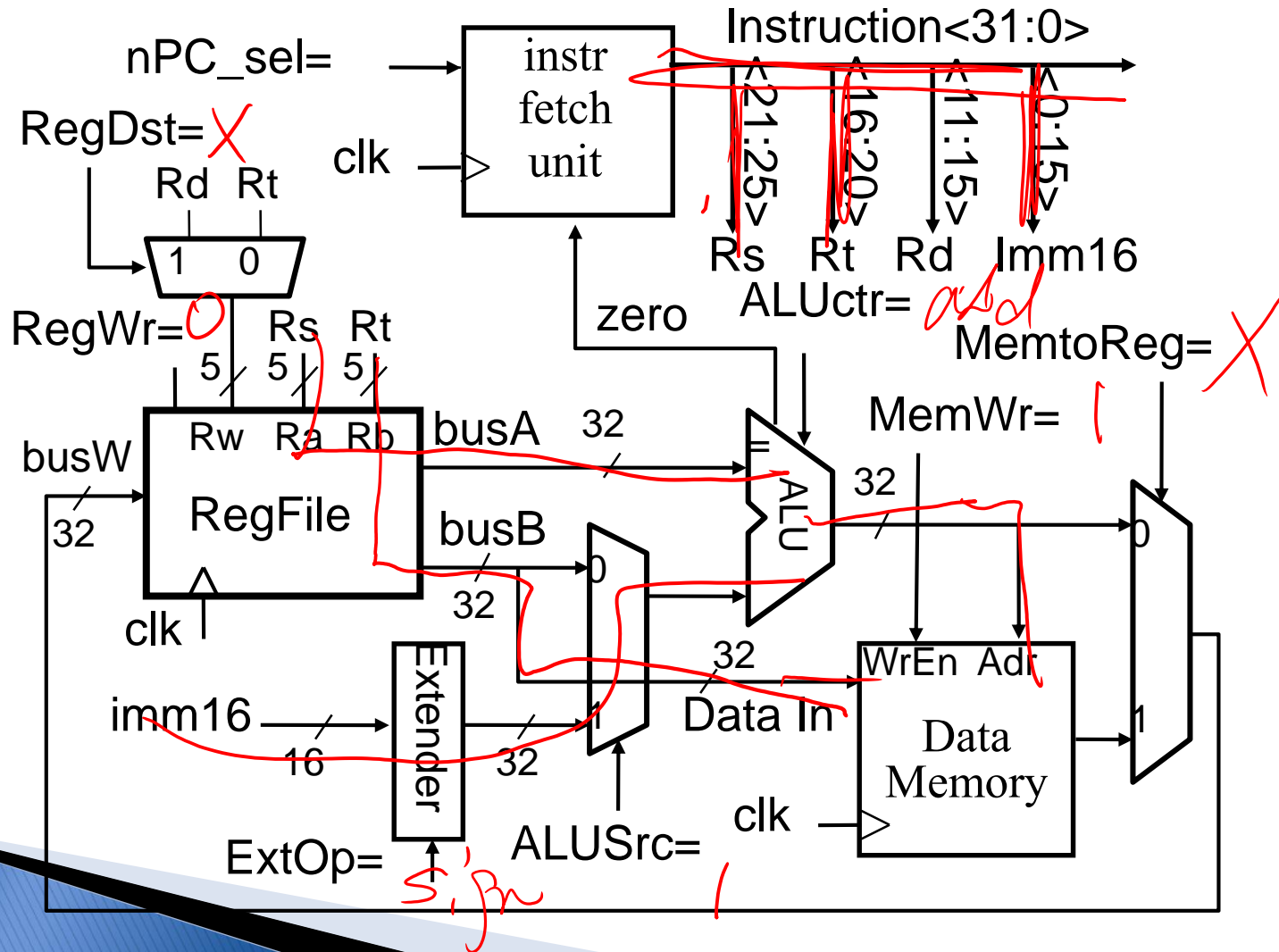
- ▶ Data Memory  $\{R[rs] + \text{SignExt}[imm16]\} = R[rt]$




# Single Cycle Datapath for SW

 

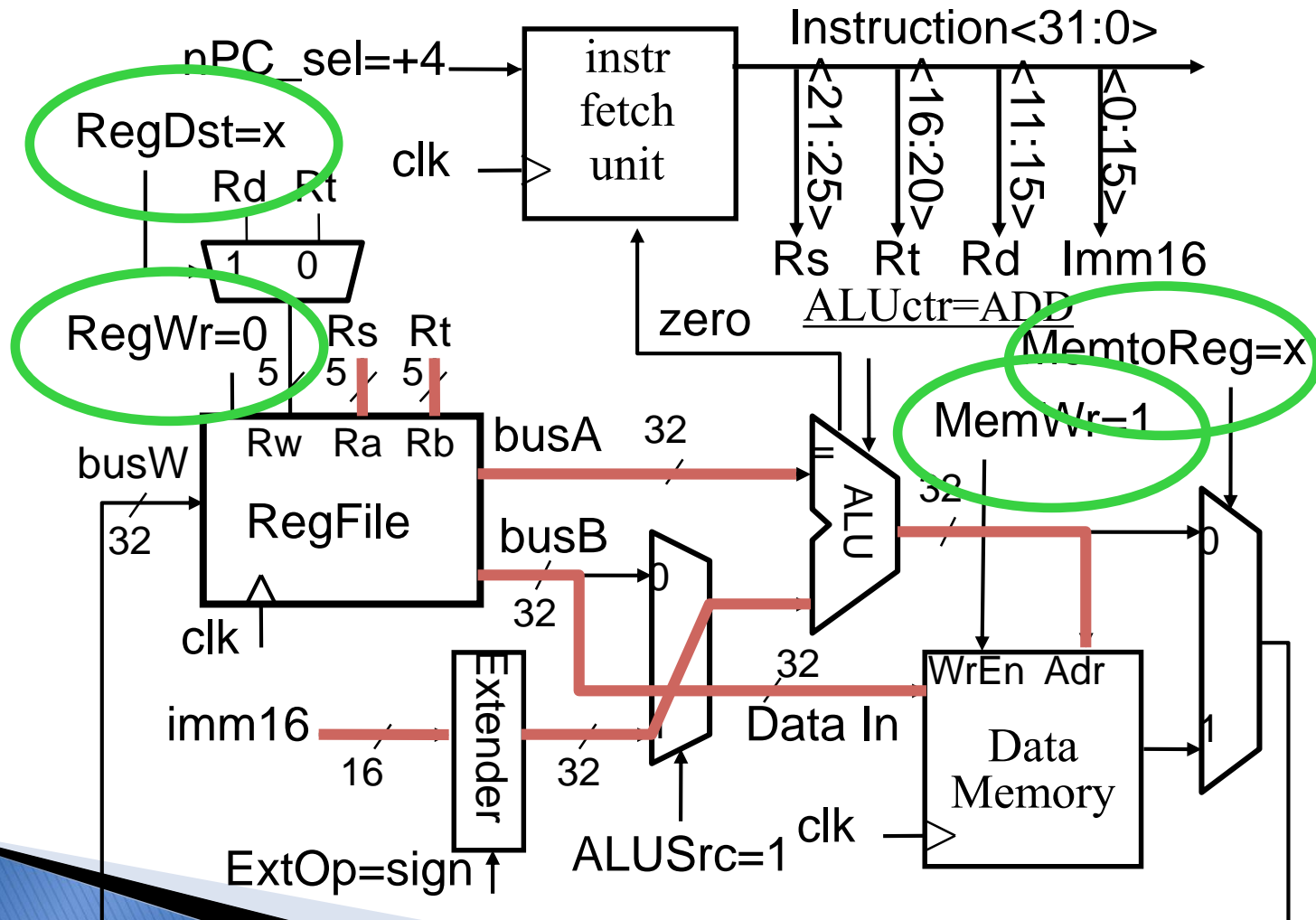
- ▶ Data Memory  $\{R[rs] + \text{SignExt}[imm16]\} = R[rt]$



# Single Cycle Datapath for Branch

 


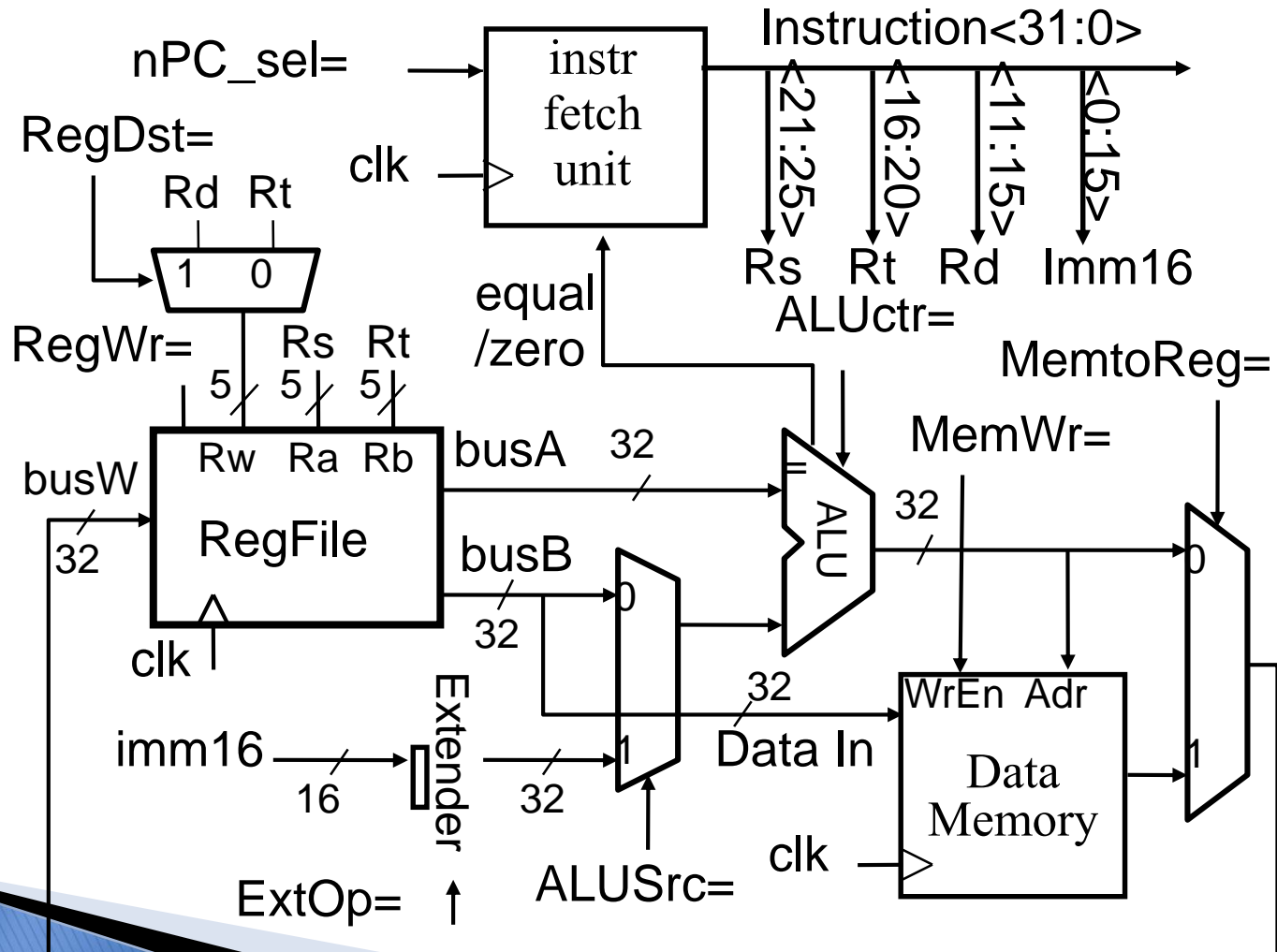- ▶ if  $(R[rs] - R[rt] == 0)$  then Zero = 1 ; else Zero = 0







# Single Cycle Datapath for Branch

 

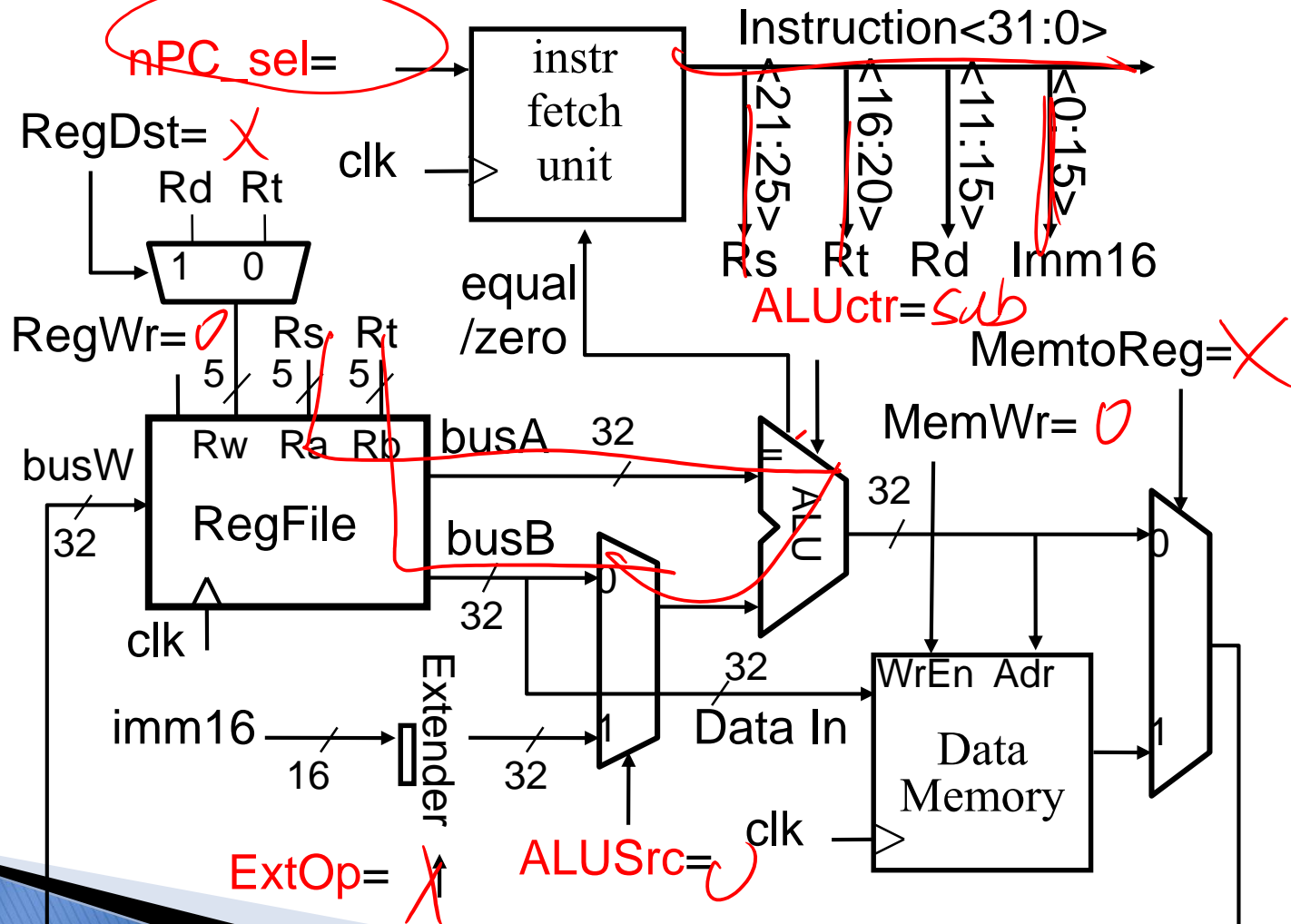
- if  $(R[rs] - R[rt] == 0)$  then Zero = 1 ; else Zero = 0



# Single Cycle Datapath for Branch

 

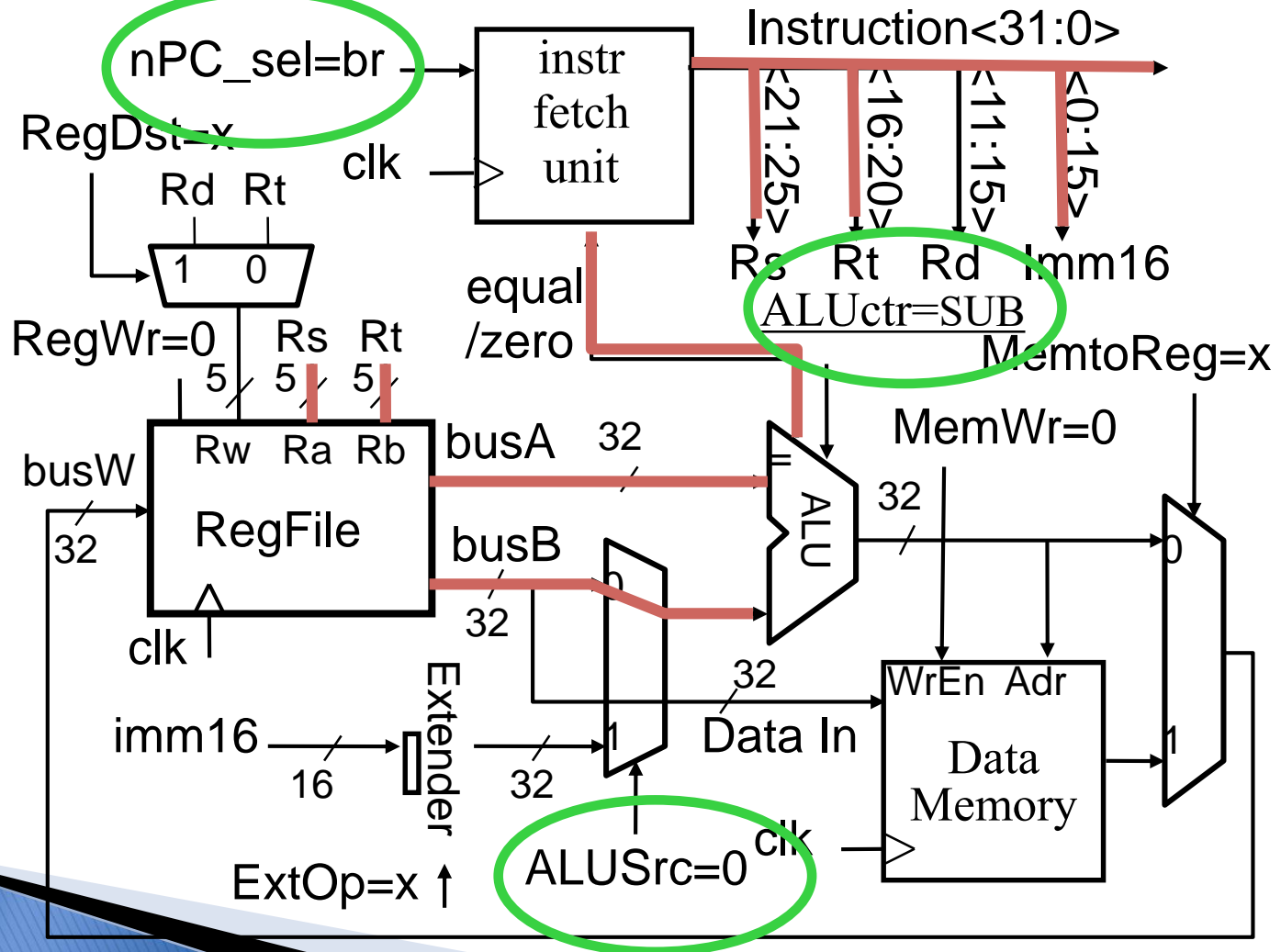
- if  $(R[rs] - R[rt] == 0)$  then Zero = 1 ; else Zero = 0



# Type of Circuits



- ▶ Synchronous Digital Systems are made up of two basic types of circuits:
- ▶ Combinational Logic (CL) circuits
  - Our previous adder circuit is an example.
  - Output is a function of the inputs only.
  - Similar to a pure function in mathematics,  $y = f(x)$ .  
(No way to store information from one invocation to the next. No side effects)
- ▶ State Elements: circuits that **store** information.

# General Synchronous Systems

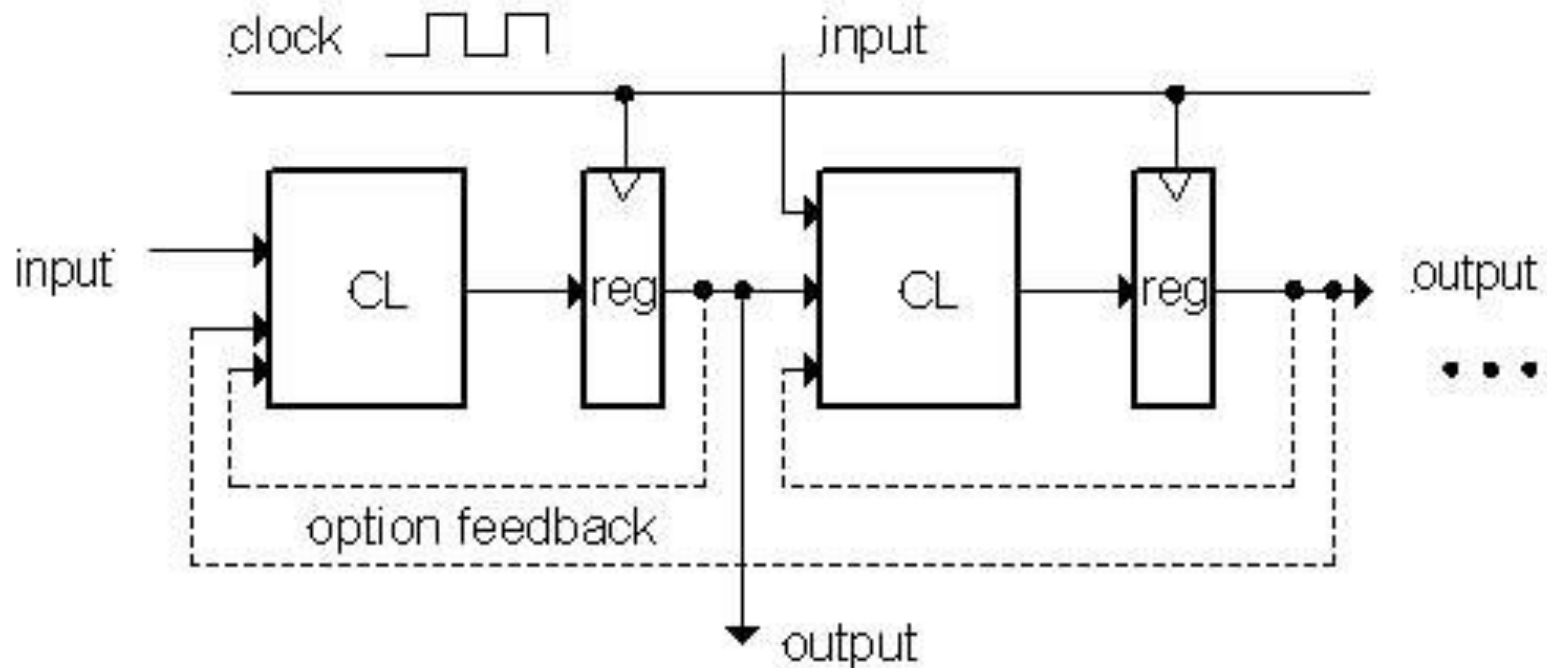

- ▶ Collection of CL blocks separated by registers.
- ▶ Registers may be back-to-back and CL blocks may be back-to-back.
- ▶ Feedback is optional.
- ▶ Clock signal(s) connects only to clock input of registers.


# Circuits with STATE (register)

  

# Uses for State Elements

- ▶ As a place to store values for some indeterminate amount of time:
  - Register files (like \$1-\$31 on the MIPS)
  - Memory (caches, and main memory)
- ▶ Help control the flow of information between combinational logic blocks.
  - State elements are used to hold up the movement of information at the inputs to combinational logic blocks and allow for orderly passage.

# Truth Tables

 


a	b	c	d	y
0	0	0	0	$F(0,0,0,0)$
0	0	0	1	$F(0,0,0,1)$
0	0	1	0	$F(0,0,1,0)$
0	0	1	1	$F(0,0,1,1)$
0	1	0	0	$F(0,1,0,0)$
0	1	0	1	$F(0,1,0,1)$
0	1	1	0	$F(0,1,1,0)$
0	1	1	1	$F(0,1,1,1)$
1	0	0	0	$F(1,0,0,0)$
1	0	0	1	$F(1,0,0,1)$
1	0	1	0	$F(1,0,1,0)$
1	0	1	1	$F(1,0,1,1)$
1	1	0	0	$F(1,1,0,0)$
1	1	0	1	$F(1,1,0,1)$
1	1	1	0	$F(1,1,1,0)$
1	1	1	1	$F(1,1,1,1)$

**TT #1: XOR, 1 iff  $a/b=1$  (not both)**

<b>a</b>	<b>b</b>	<b>y</b>
<b>0</b>	<b>0</b>	<b>0</b>
<b>0</b>	<b>1</b>	<b>1</b>
<b>1</b>	<b>0</b>	<b>1</b>
<b>1</b>	<b>1</b>	<b>0</b>



# TT #2: 2-bit adder

 

A	B	C
$a_1a_0$	$b_1b_0$	$c_2c_1c_0$
00	00	000
00	01	001
00	10	010
00	11	011
01	00	001
01	01	010
01	10	011
01	11	100
10	00	010
10	01	011
10	10	100
10	11	101
11	00	011
11	01	100
11	10	101
11	11	110

How  
Many  
Rows?

## TT #3: 32-bit unsigned adder

A		B		C
000 ... 0	000 ... 0	000 ... 00		
000 ... 0	000 ... 1	000 ... 01		
.	.	.	How Many Rows?	
.	.	.		
.	.	.		
111 ... 1	111 ... 1	111 ... 10		

How  
Many  
Rows?

## TT #4: 3-input majority circuit

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


# Logic Gates (1/2)

AND



ab	c
00	0
01	0
10	0
11	1

OR

 

ab	c
00	0
01	1
10	1
11	1

NOT



a	b
0	1
1	0

# Logic Gates (2/2)


XOR



NAND



NOR

 

ab	c
00	0
01	1
10	1
11	0

ab	c
00	1
01	1
10	1
11	0

ab	c
00	1
01	0
10	0
11	0


# 2-input gates extend to n-inputs

- N-input XOR is the only one which isn't so obvious
- It's simple: XOR is a 1 iff the # of 1s at its input is odd


a	b	c	y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

## TT $\Rightarrow$ Gates (e.g., majority circ.)

a	b	c	y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 
 
# Boolean Algebra (e.g., for majority fun.)



$$y = a \bullet b + a \bullet c + b \bullet c$$

$$y = ab + ac + bc$$



# Laws of Boolean Algebra

$$x \cdot \bar{x} = 0$$

$$x \cdot 0 = 0$$

$$x \cdot 1 = x$$

$$x \cdot x = x$$

$$x \cdot y = y \cdot x$$

$$(xy)z = x(yz)$$

$$x(y + z) = xy + xz$$

$$xy + x = x$$

$$\bar{x}y + x = x + y$$

$$\overline{x \cdot y} = \bar{x} + \bar{y}$$

$$x + \bar{x} = 1$$

$$x + 1 = 1$$

$$x + 0 = x$$

$$x + x = x$$

$$x + y = y + x$$

$$(x + y) + z = x + (y + z)$$

$$x + yz = (x + y)(x + z)$$

$$(x + y)x = x$$

$$(\bar{x} + y)x = xy$$

$$\overline{x + y} = \bar{x} \cdot \bar{y}$$

complementarity

laws of 0's and 1's

identities

idempotent law

commutativity

associativity

distribution

uniting theorem


uniting theorem v.2

DeMorgan's Law

# Boolean Algebraic Simplification

$$\begin{aligned}y &= ab + a + c \\&= a(b + 1) + c && \text{distribution, identity} \\&= a(1) + c && \text{law of 1's} \\&= a + c && \text{identity}\end{aligned}$$

# Circuit & Algebraic Simplification

 


original circuit

$$\downarrow$$
$$y = ((ab) + a) + c$$

$$\downarrow$$
$$\begin{aligned} &= ab + a + c \\ &= a(b + 1) + c \\ &= a(1) + c \\ &= a + c \end{aligned}$$

equation derived from original circuit

algebraic simplification

 


simplified circuit

BA also great for  
circuit verification  
Circ X = Circ Y?  
use BA to prove!

# Canonical forms (1/2)

	$abc$	$y$
$\bar{a} \cdot \bar{b} \cdot \bar{c}$	000	1
$\bar{a} \cdot \bar{b} \cdot c$	001	1
	010	0
	011	0
$a \cdot \bar{b} \cdot \bar{c}$	100	1
	101	0
$a \cdot b \cdot \bar{c}$	110	1
	111	0

Sum-of-products  
(ORs of ANDs)


$$y = \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + a\bar{b}\bar{c} + ab\bar{c}$$

## Canonical forms (2/2)

$$\begin{aligned}y &= \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + a\bar{b}\bar{c} + ab\bar{c} \\&= \bar{a}\bar{b}(\bar{c} + c) + a\bar{c}(\bar{b} + b) \\&= \bar{a}\bar{b}(1) + a\bar{c}(1) \\&= \bar{a}\bar{b} + a\bar{c}\end{aligned}$$

*distribution*  
*complementarity*  
*identity*

