

CSE 140

Computer Architecture

Lecture 3 – Single Cycle CPU


Announcement

- ▶ Lab #1 starts next week (9/9)
 - Due in one week
- ▶ Reading assignment #2
 - Chapter 2.5, 4.5 – 4.8
 - Do all **Participation Activities** in each section
 - Access through CatCourses
 - Due Thursday (9/12) at 11:59pm
 - Review CSE 31 materials (available at CatCourses)
 - Assembly language and machine code: Ch. 2.1-2.8, 2.9-2.10, 2.13
 - Quick review:
 - <https://classroom.udacity.com/courses/ud219>

Review


- ▶ CPU design involves Datapath, Control
 - Datapath in MIPS involves 5 CPU stages
 1. Instruction Fetch
 2. Instruction Decode & Register Read
 3. ALU (Execute)
 4. Memory
 5. Register Write

Generic Steps of Datapath

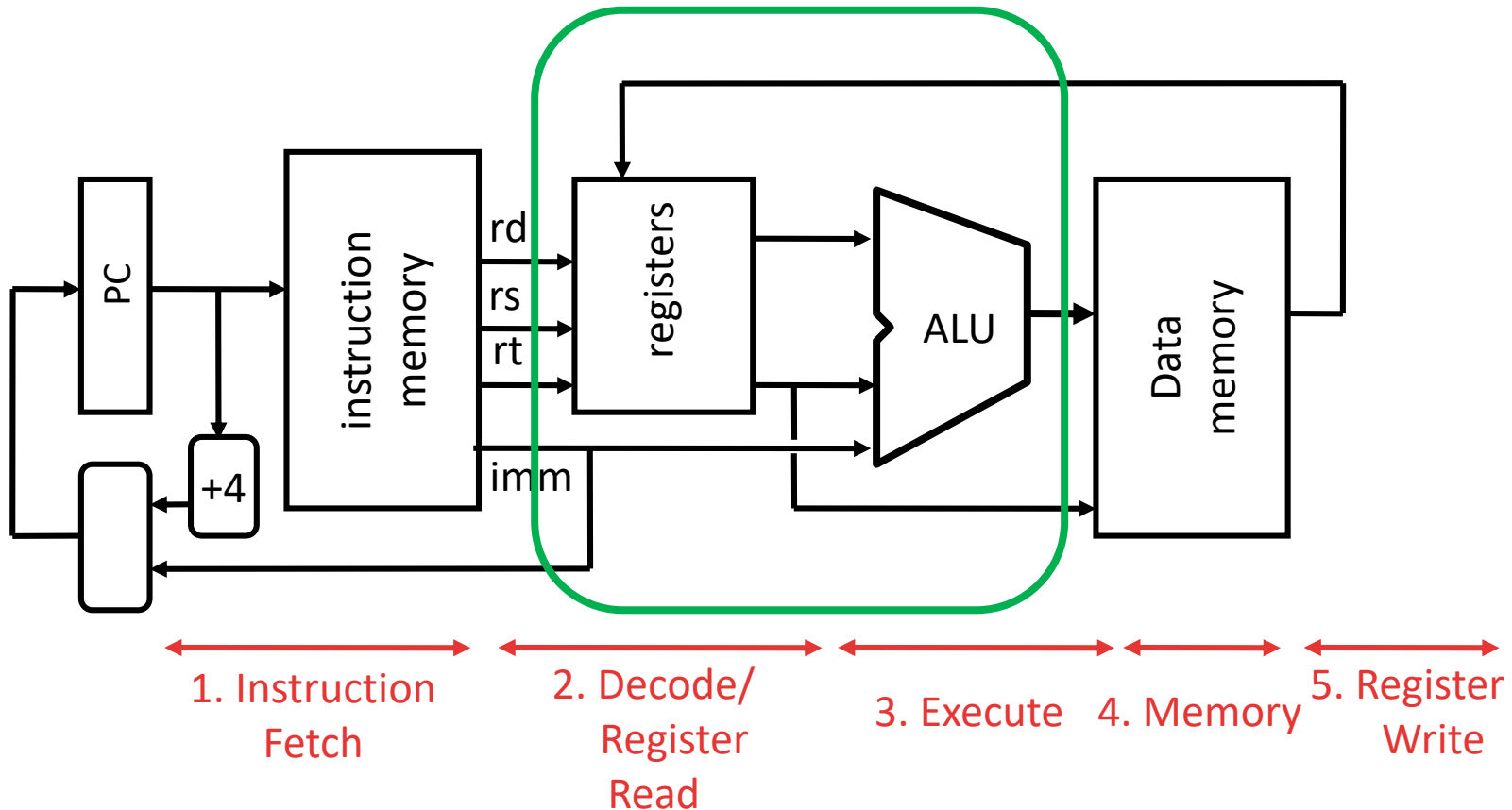


How do we handle the different register usage between r-type and i-type instructions?

A zoomed in version of RegFile and ALU

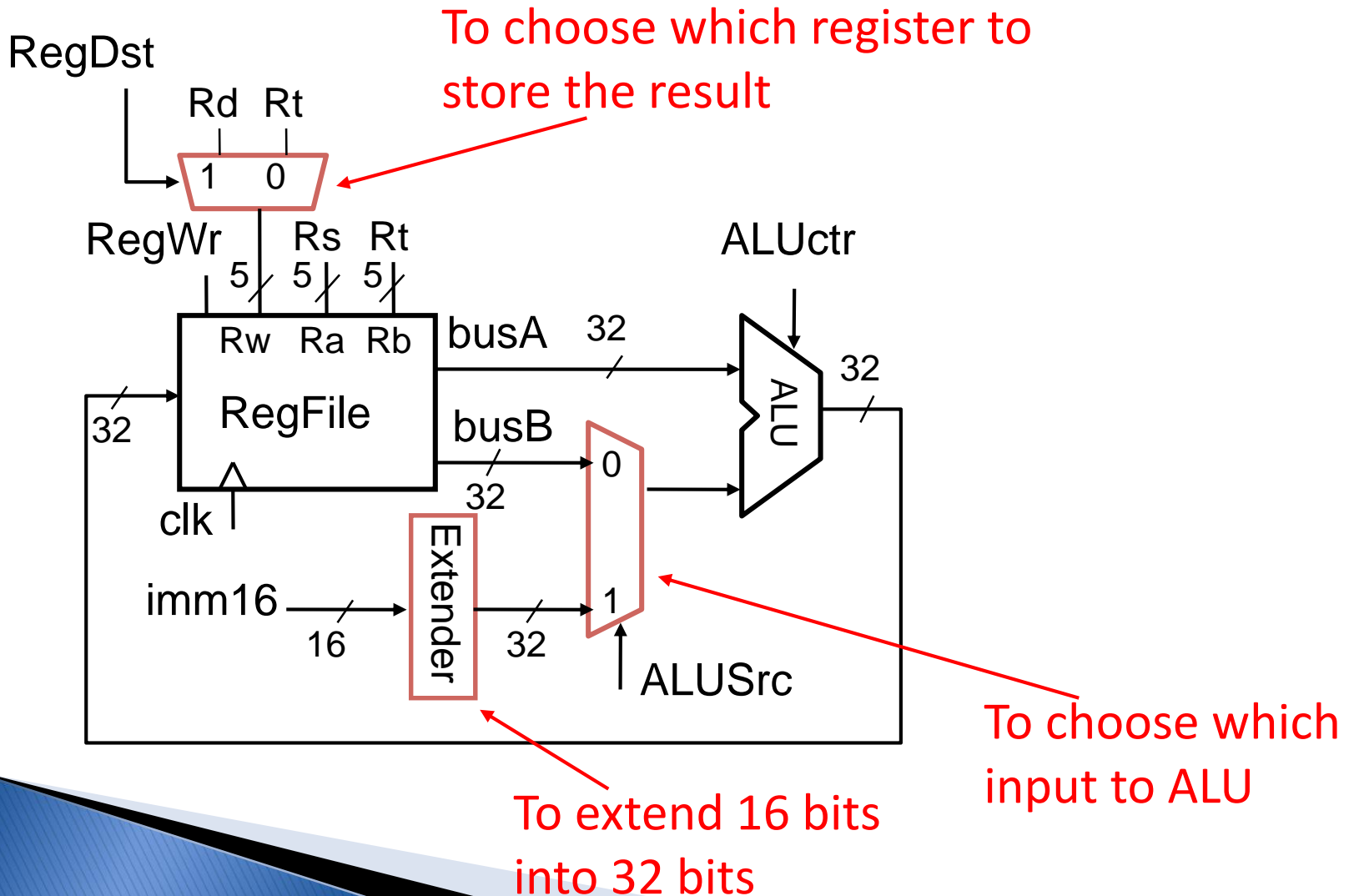

Load Memory

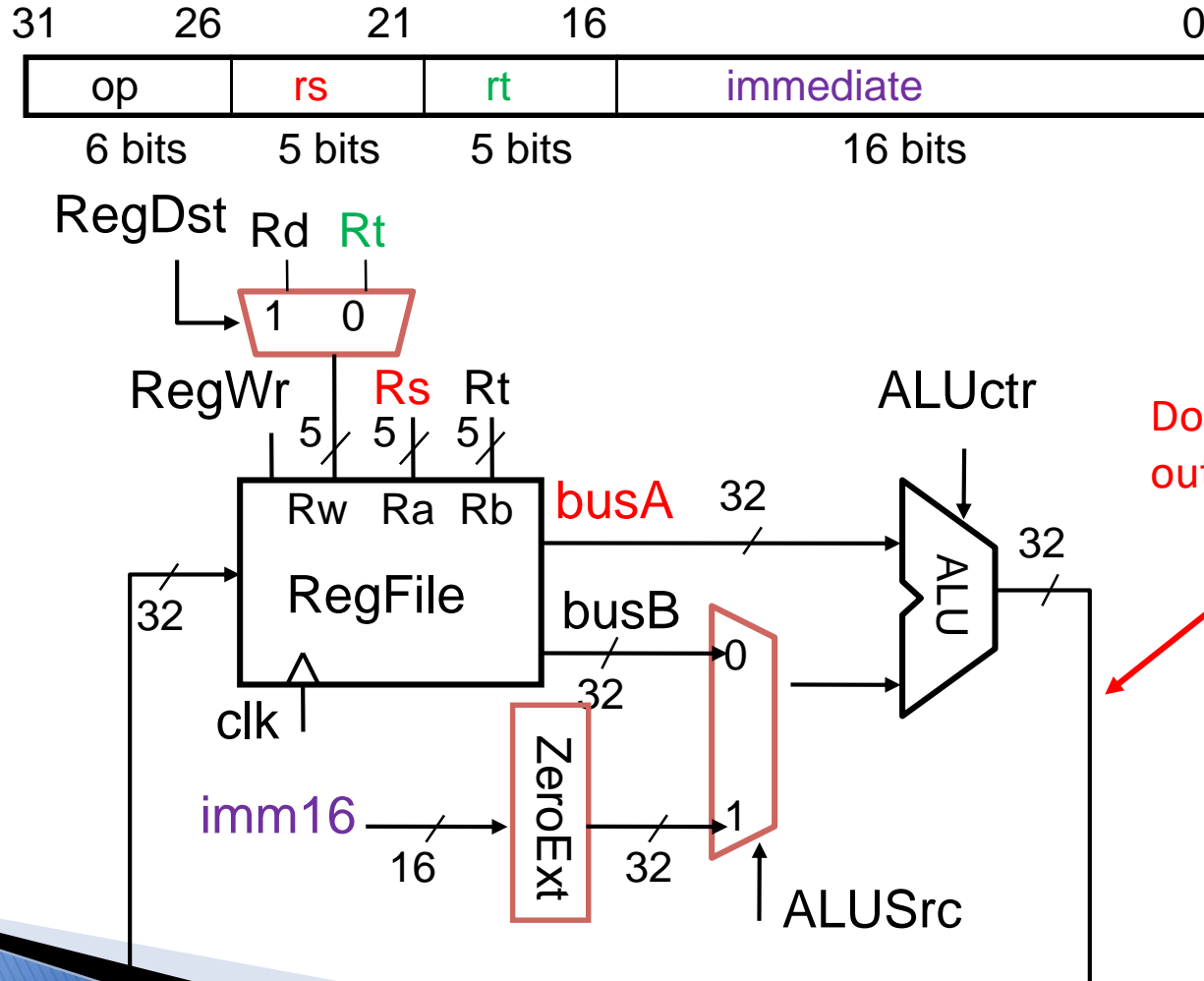
- ▶ $R[\underline{rt}] = \text{Mem}[R[\text{rs}] + \text{SignExt}[\text{imm16}]]$
- ▶ Example: `lw rt, rs, imm16`



Load Memory

► $R[\underline{rt}] = \text{Mem}[R[\underline{rs}] + \text{SignExt}[\text{imm16}]]$


► Example: `lw rt, rs, imm16`

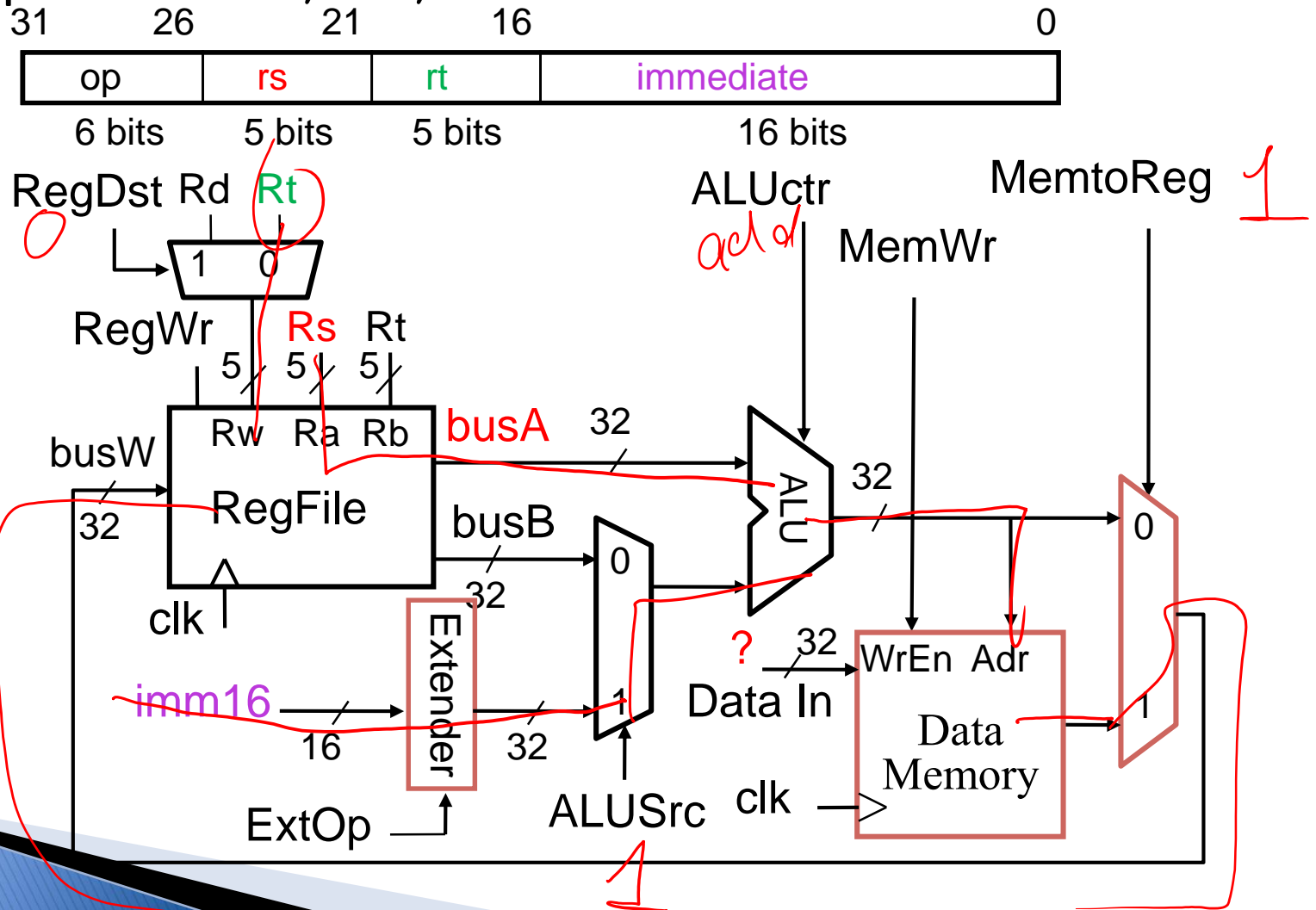

Store Memory

- ▶ $\text{Mem}[\text{R}[\text{rs}] + \text{SignExt}[\text{imm16}]] = \text{R}[\text{rt}]$



Ex.: `sw rt, rs, imm16`

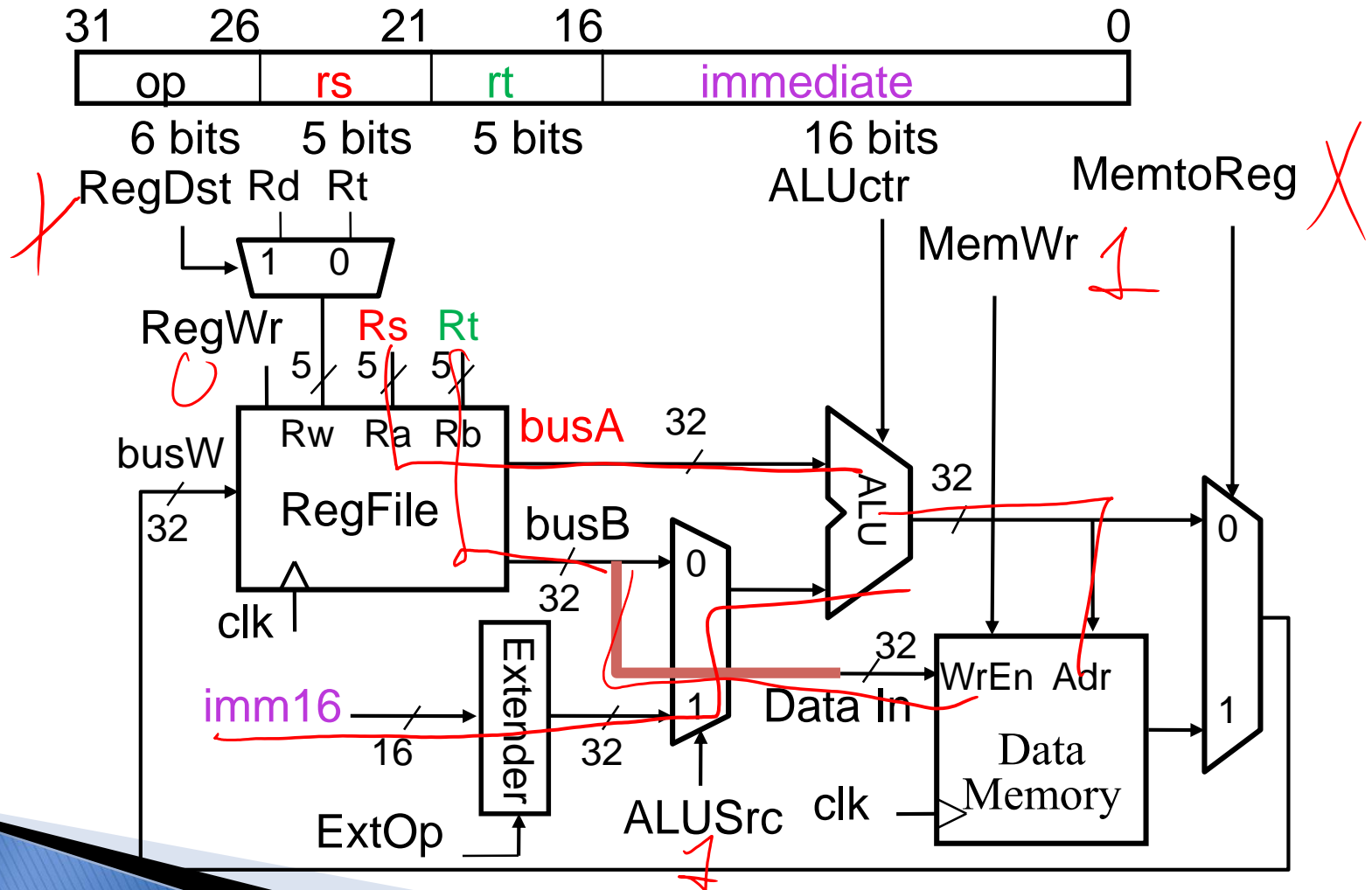

Datapath for Branch Operations

- ▶ beq rs, rt, imm16


Datapath generates condition (equal)

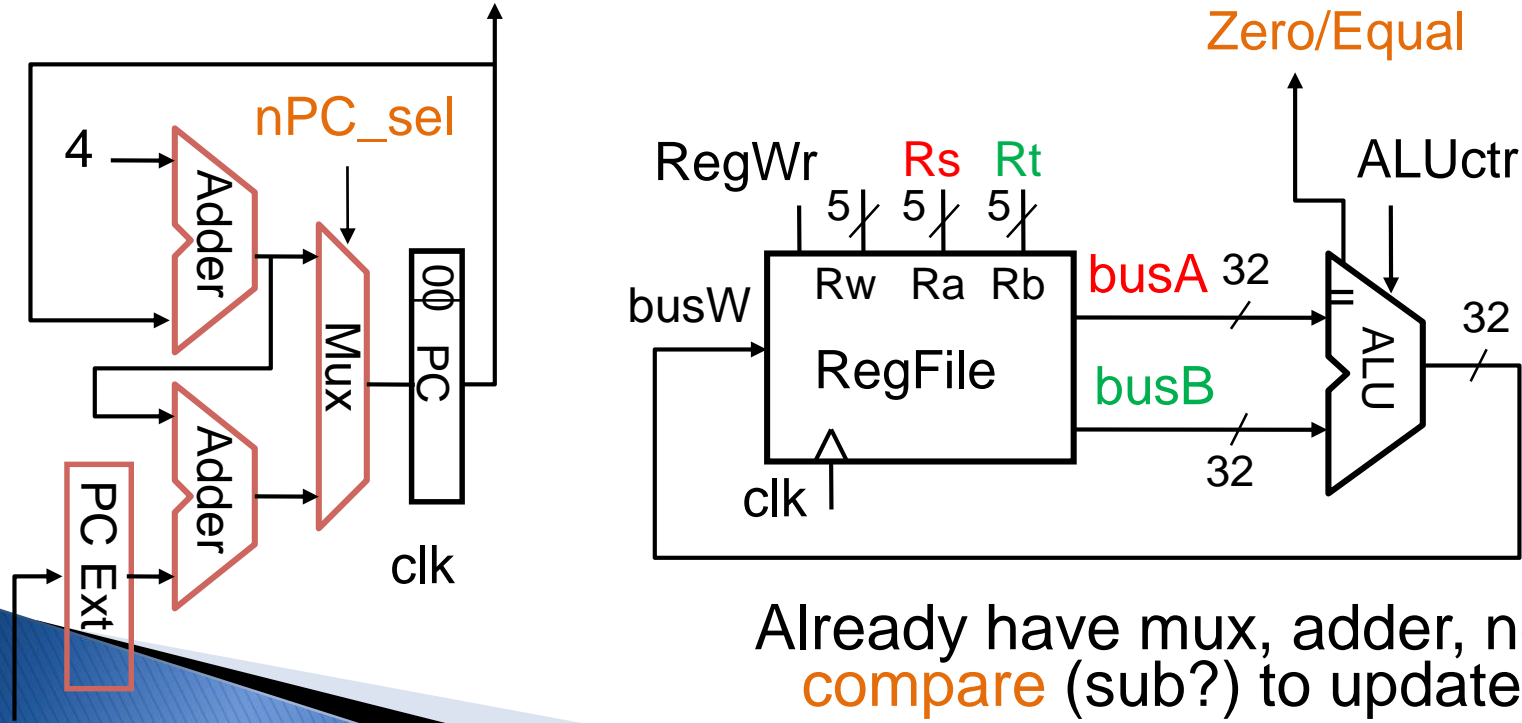 


Already have mux, adder, need **equal compare** (sub?) to update for PC

imm16

Single Cycle Datapath

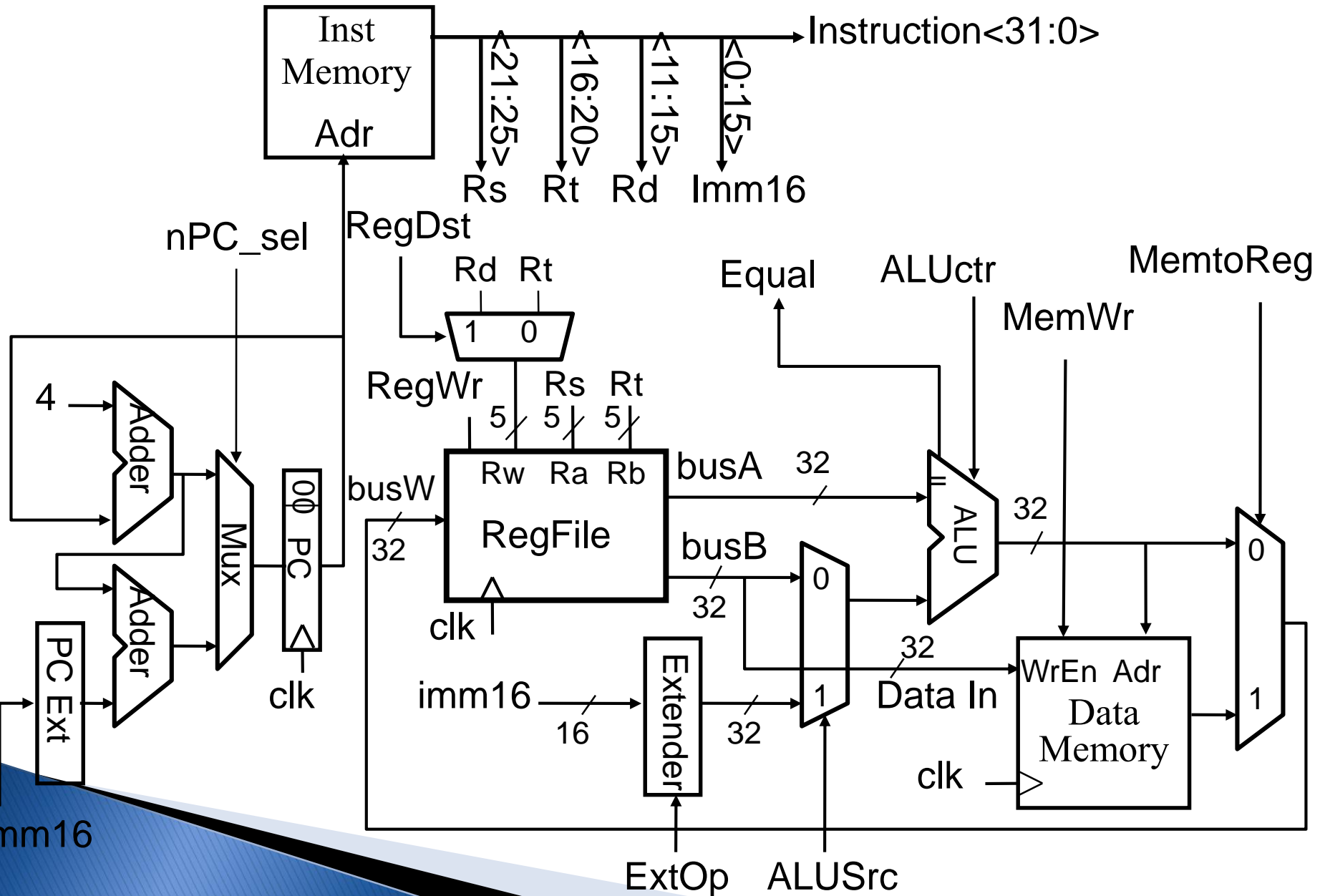


Abstract View of the Implementation

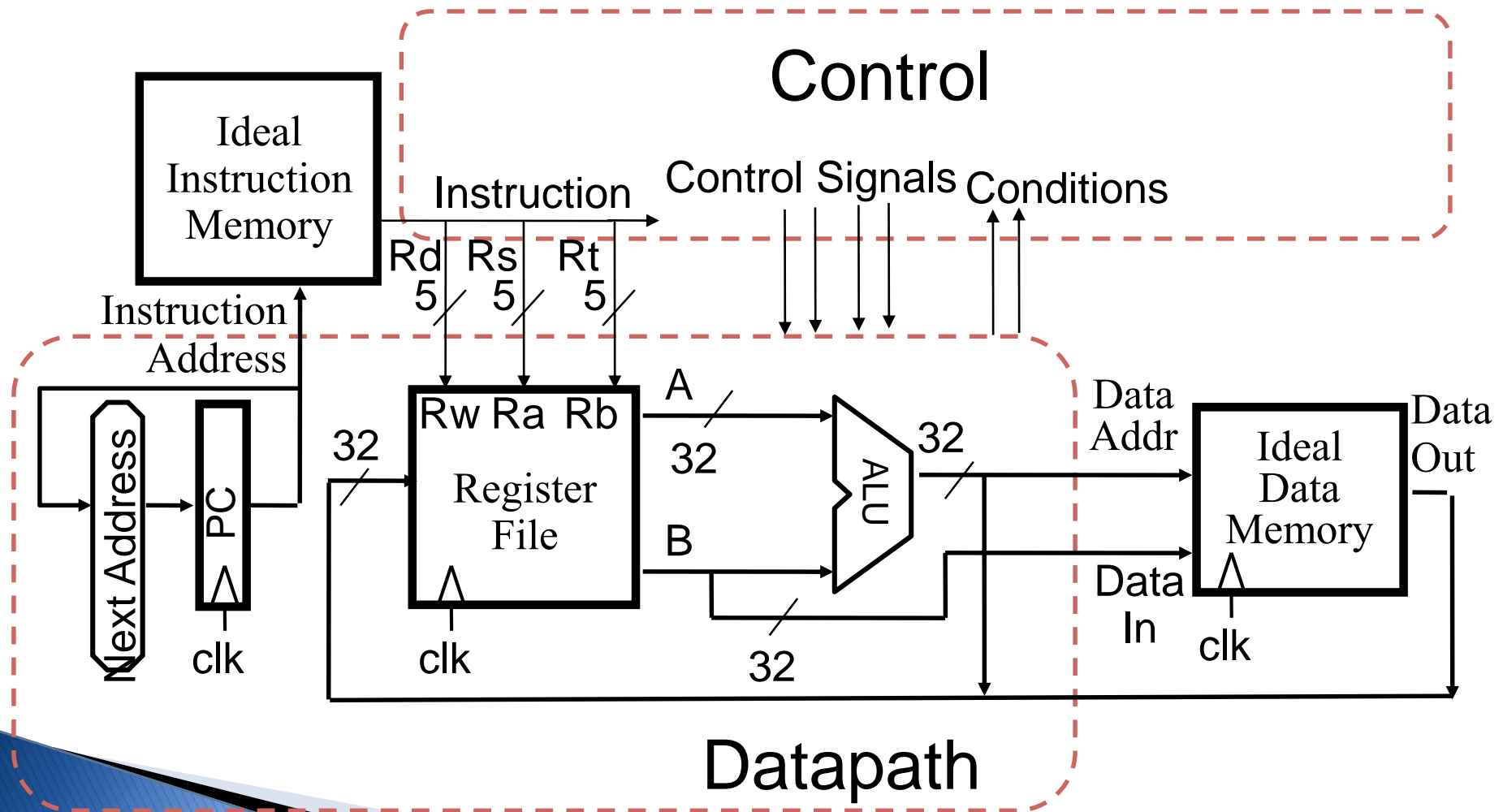


A Single Cycle Datapath

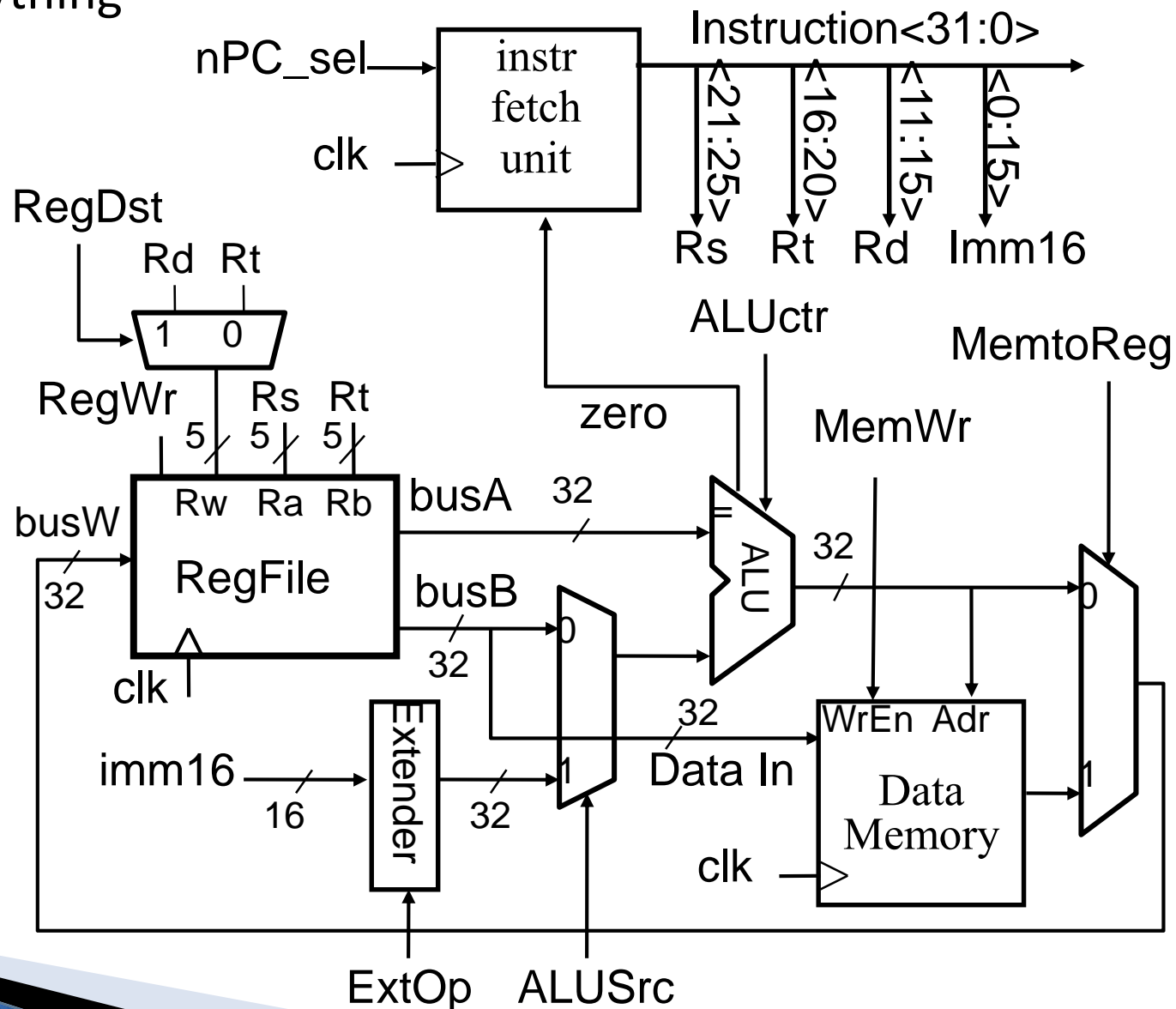- ▶ We have everything except control signals




Meaning of the Control Signals

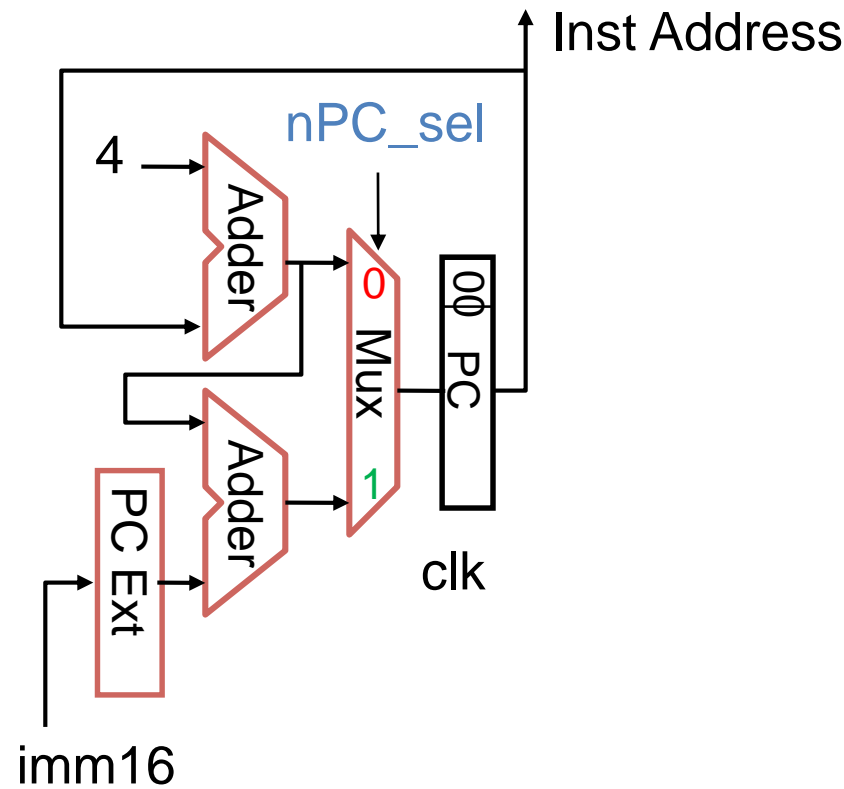- **nPC_sel**: “+4”: $0 \Rightarrow PC \leftarrow PC + 4$
“br”: $1 \Rightarrow PC \leftarrow PC + 4 + \{ \text{SignExt}(\text{Im16}), 00 \}$
“n”=next




Meaning of the Control Signals

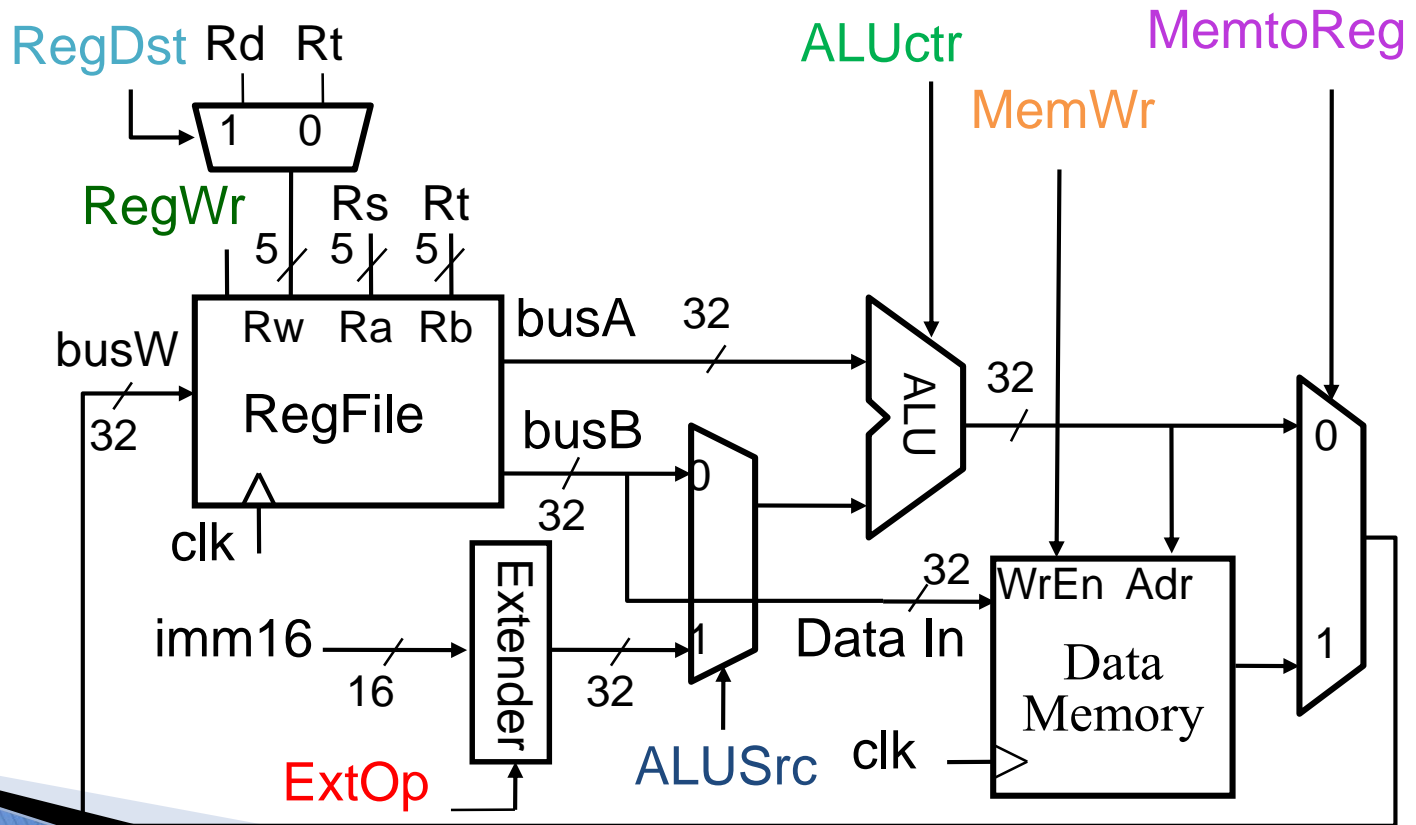- ▶ **ExtOp**: “zero”, “sign”
- ▶ **ALUsrc**: 0 \Rightarrow regB; 1 \Rightarrow immedi
- ▶ **ALUctr**: “ADD”, “SUB”, “OR”
- **MemWr**: 1 \Rightarrow write memory
- **MemtoReg**: 0 \Rightarrow ALU; 1 \Rightarrow Mem
- **RegDst**: 0 \Rightarrow “rt”; 1 \Rightarrow “rd”
- **RegWr**: 1 \Rightarrow write register



The Add Instruction

 

add rd, rs, rt


- MEM[PC] Fetch the instruction from memory
- $R[rd] = R[rs] + R[rt]$ The actual operation
- $PC = PC + 4$ Calculate the next instruction's address

Instruction Fetch Unit start of Add


- Fetch the instruction from Instruction memory:

Instruction = MEM[PC]


- same for all instructions

 

The Single Cycle Datapath during Add

 


$$R[rd] = R[rs] + R[rt]$$

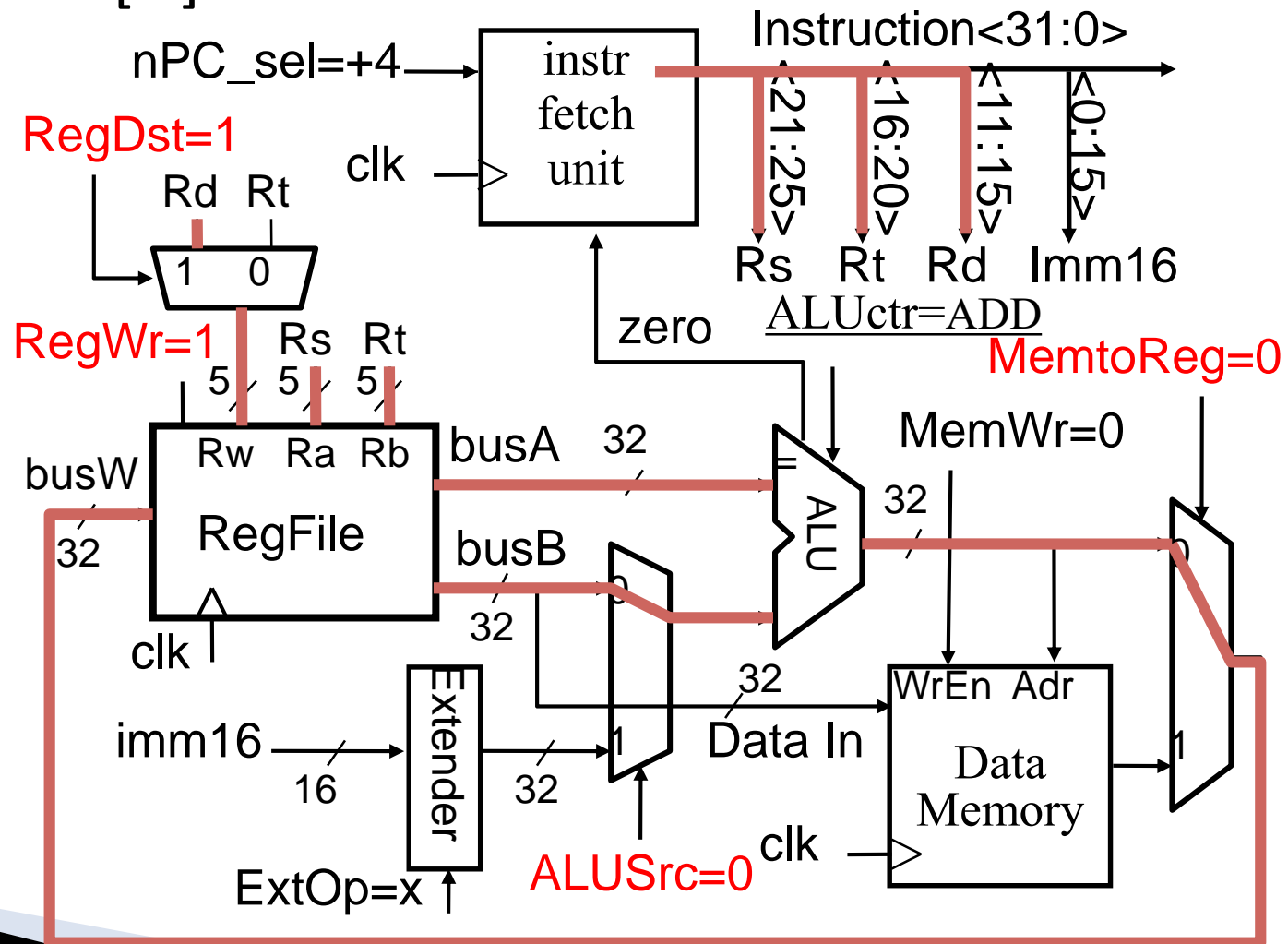


Instruction Fetch Unit end of Add

 
- ▶ $PC = PC + 4$
 - This is the same for all instructions except: Branch and Jump




Single Cycle Datapath for Ori

 

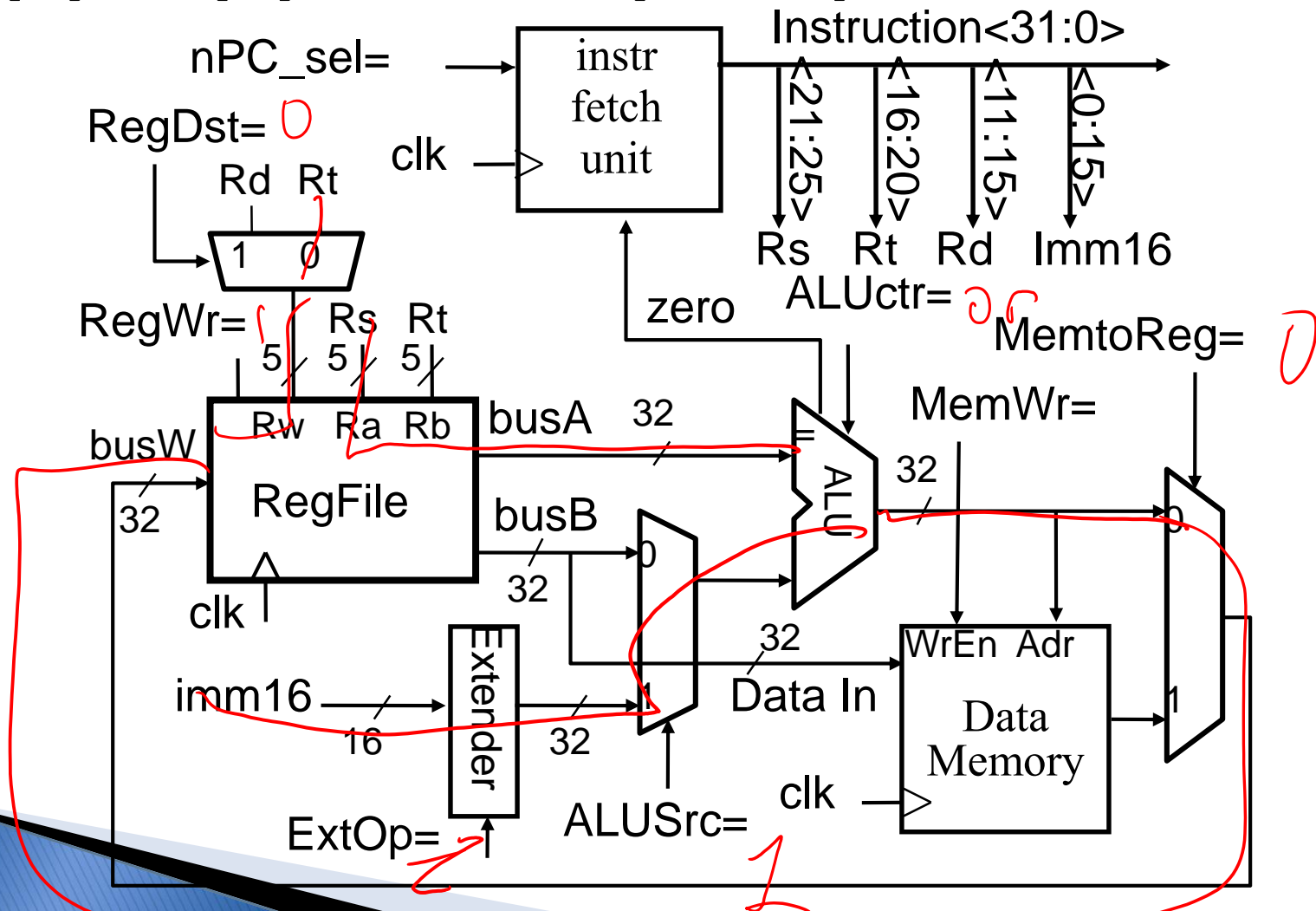
- ▶ $R[rt] = R[rs] \text{ OR } \text{ZeroExt}[\text{Imm16}]$




Single Cycle Datapath for Ori

 

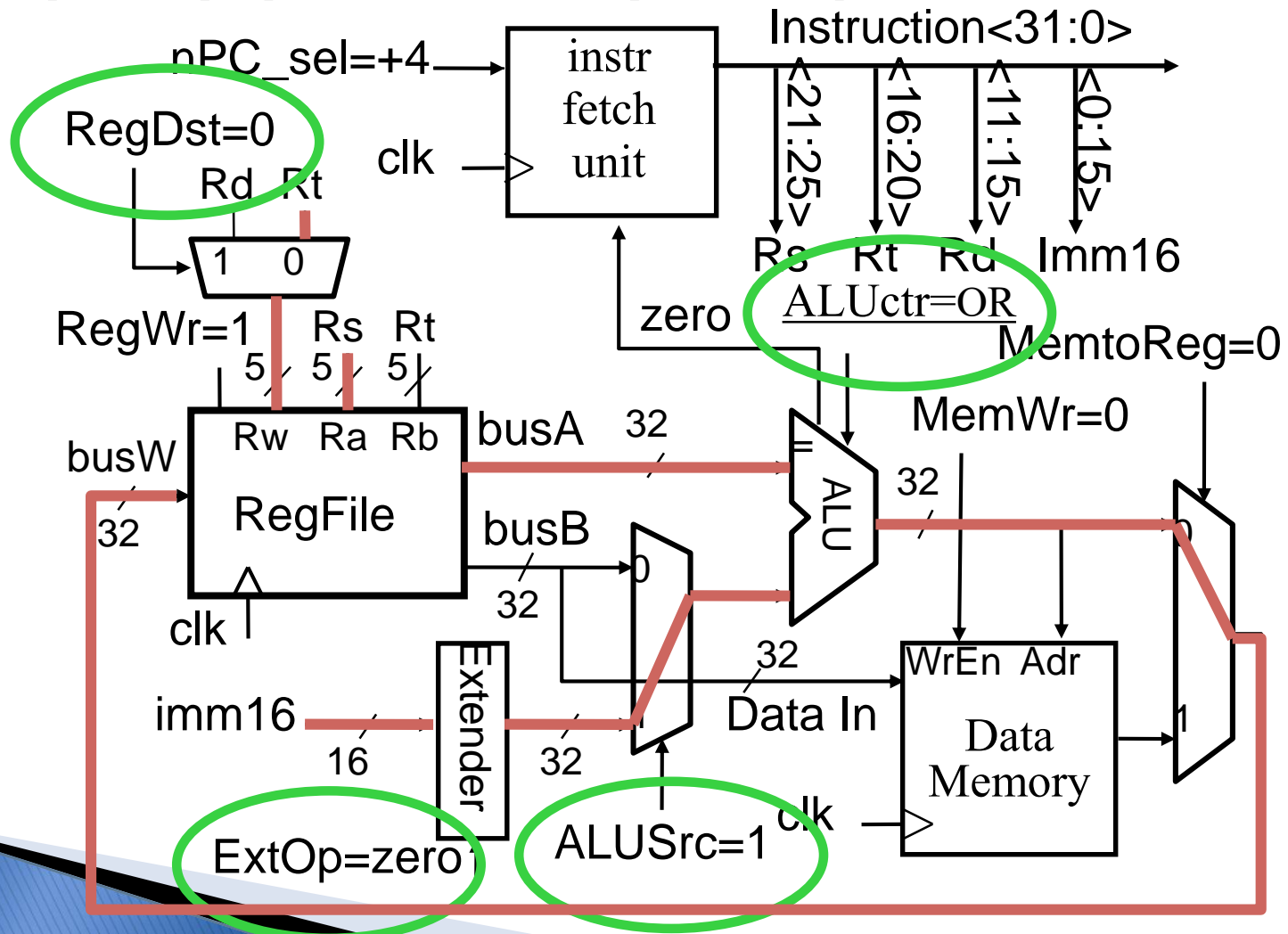
► $R[rt] = R[rs] \text{ OR } \text{ZeroExt}[\text{Imm16}]$




Single Cycle Datapath for LW

 

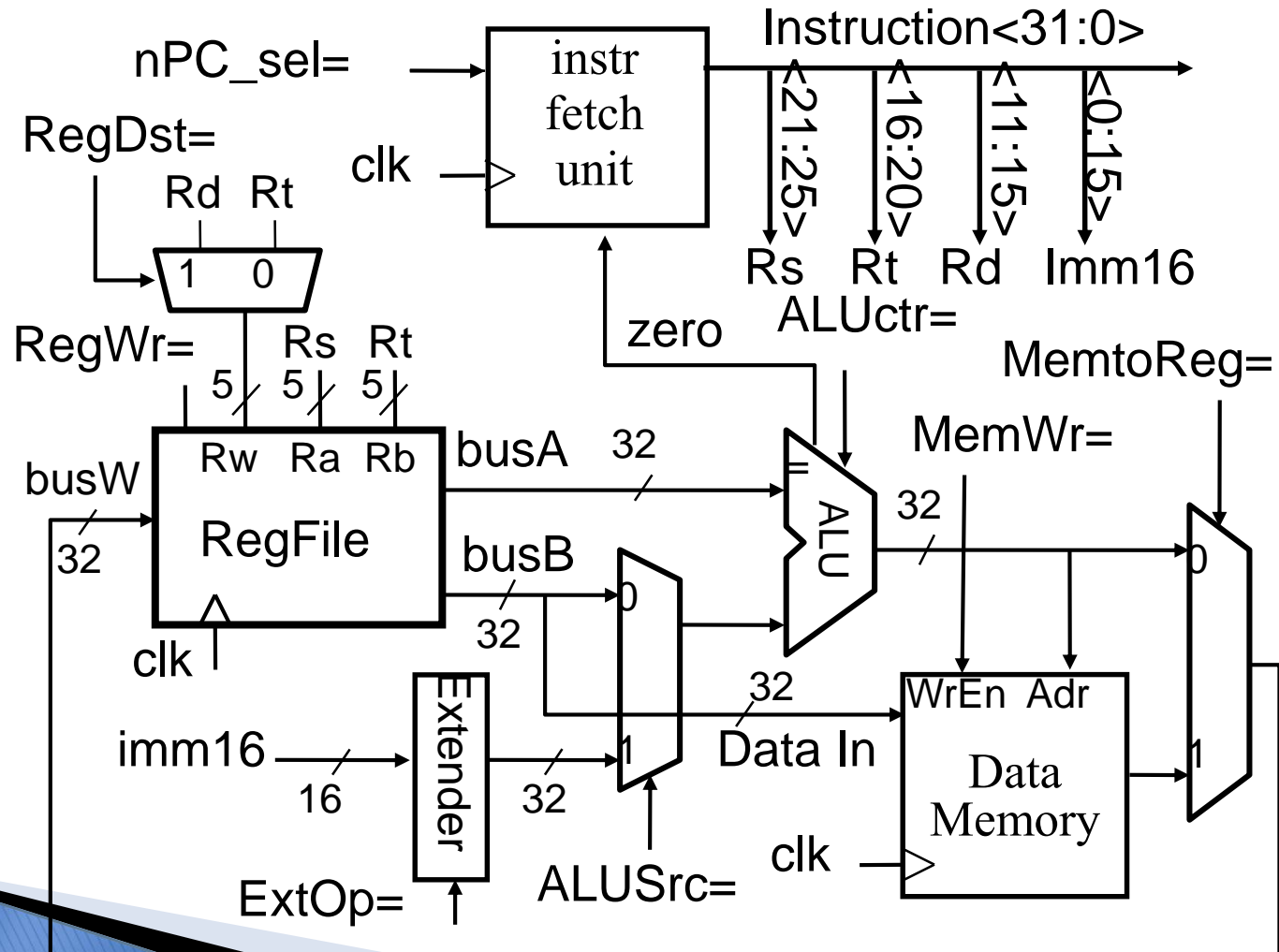
- ▶ $R[rt] = \text{Data Memory} \{R[rs] + \text{SignExt}[\text{imm16}]\}$




Single Cycle Datapath for LW

 

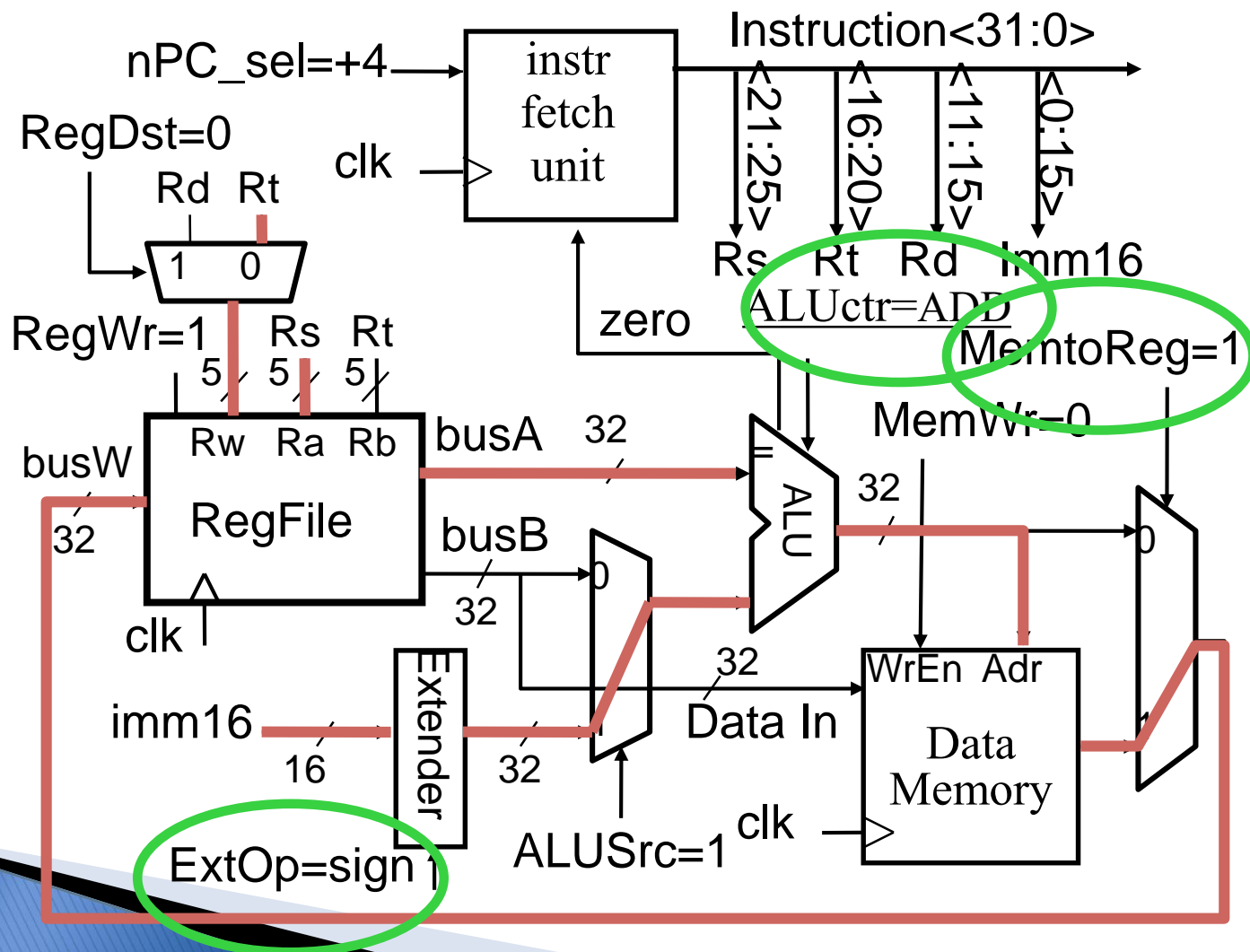
- ▶ $R[rt] = \text{Data Memory} \{R[rs] + \text{SignExt}[\text{imm16}]\}$




Single Cycle Datapath for SW

 

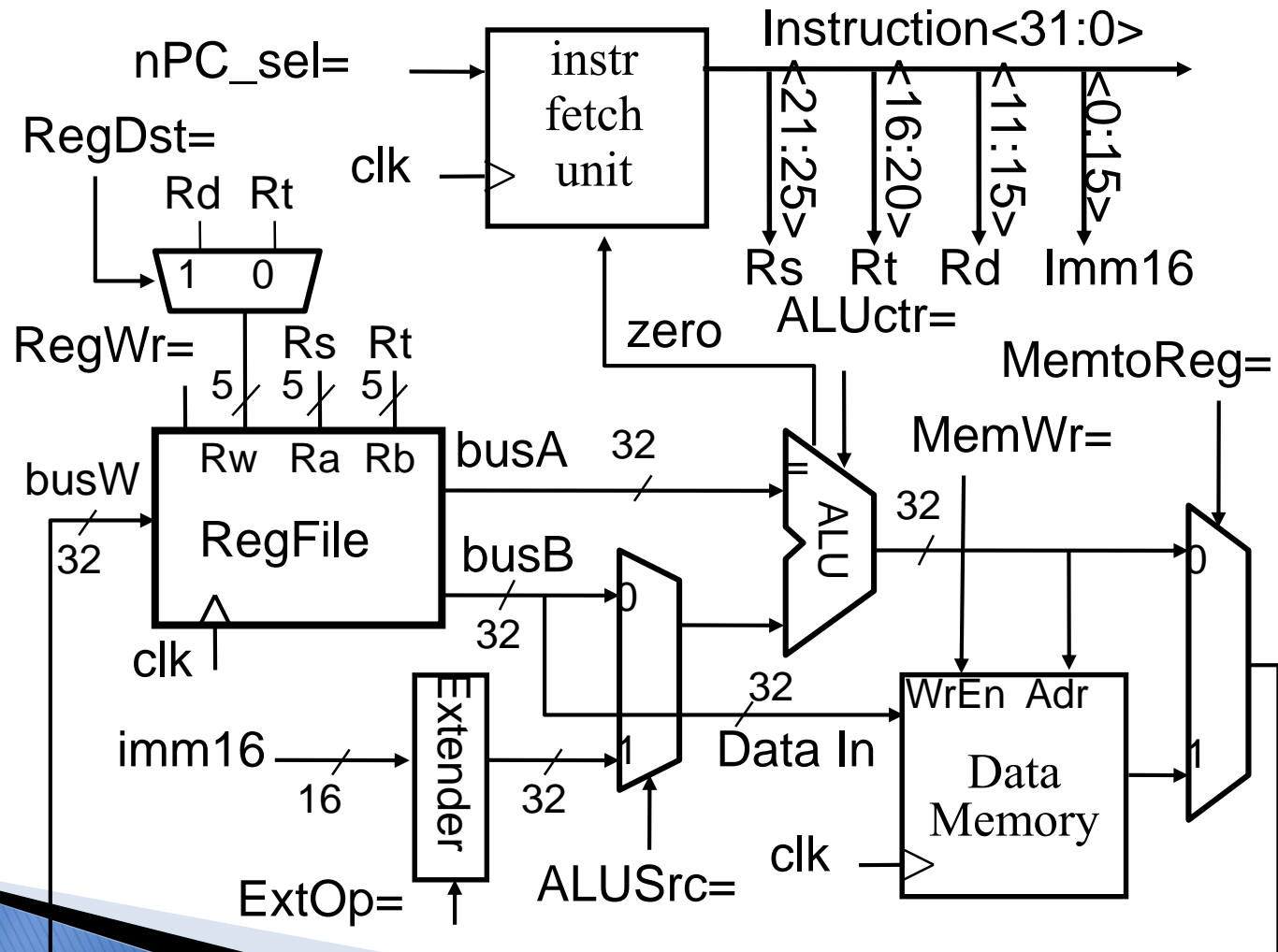
- ▶ Data Memory $\{R[rs] + \text{SignExt}[imm16]\} = R[rt]$




Single Cycle Datapath for SW

 

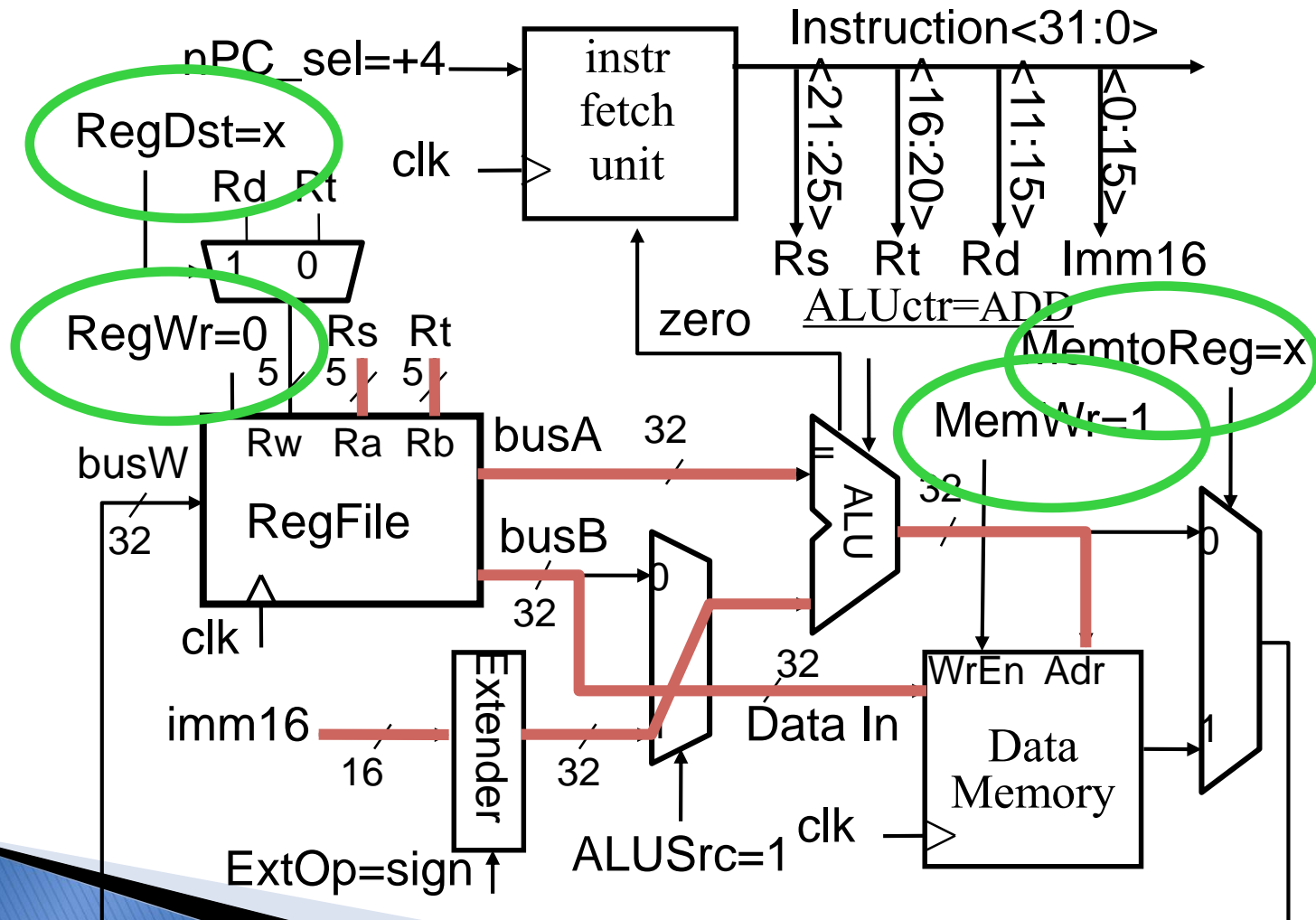- ▶ Data Memory $\{R[rs] + \text{SignExt}[imm16]\} = R[rt]$




Single Cycle Datapath for Branch

 


- ```

▶ if (R[rs] - R[rt] == 0) then Zero = 1 ; else Zero = 0


```

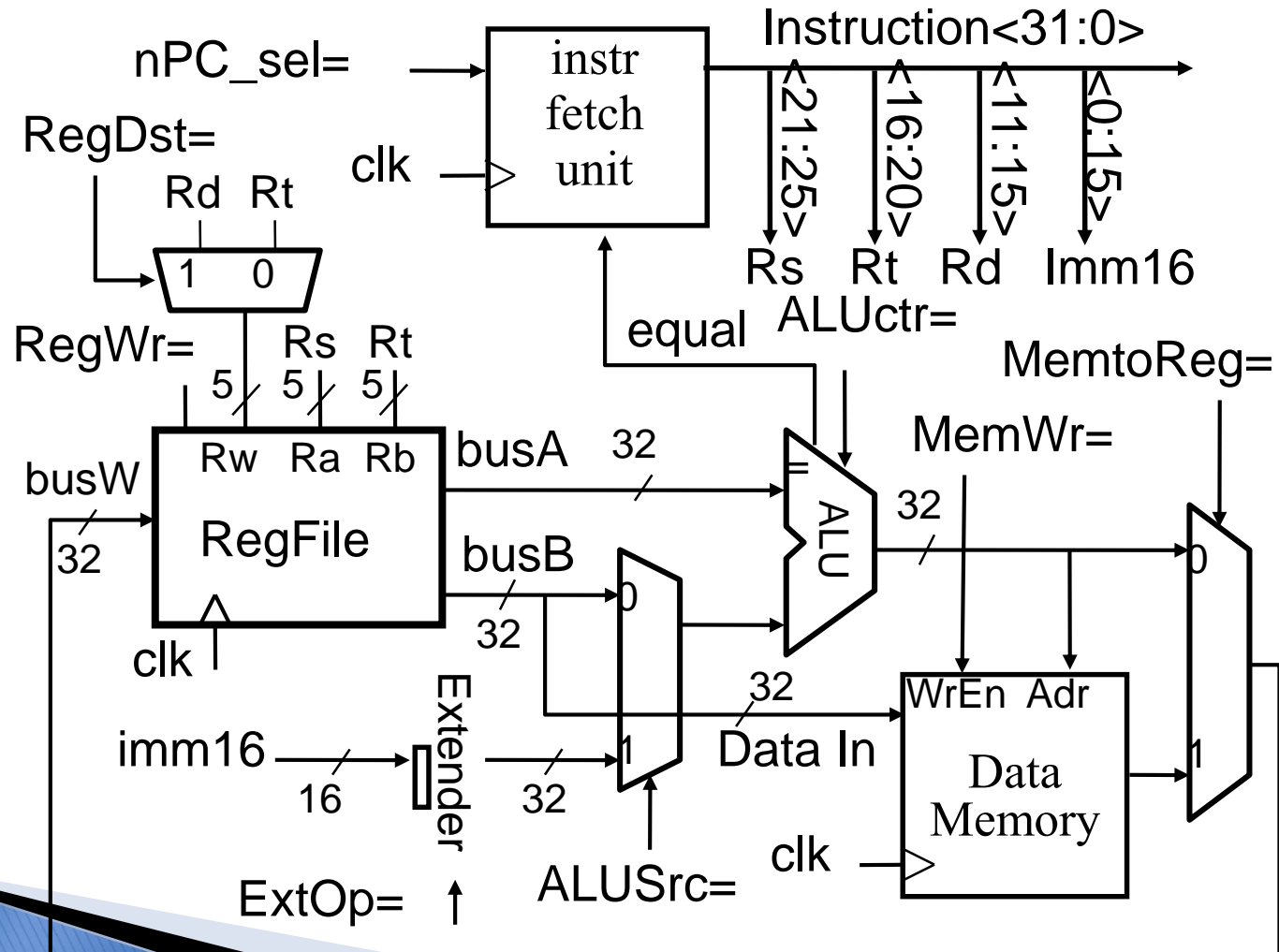


# Single Cycle Datapath for Branch

 

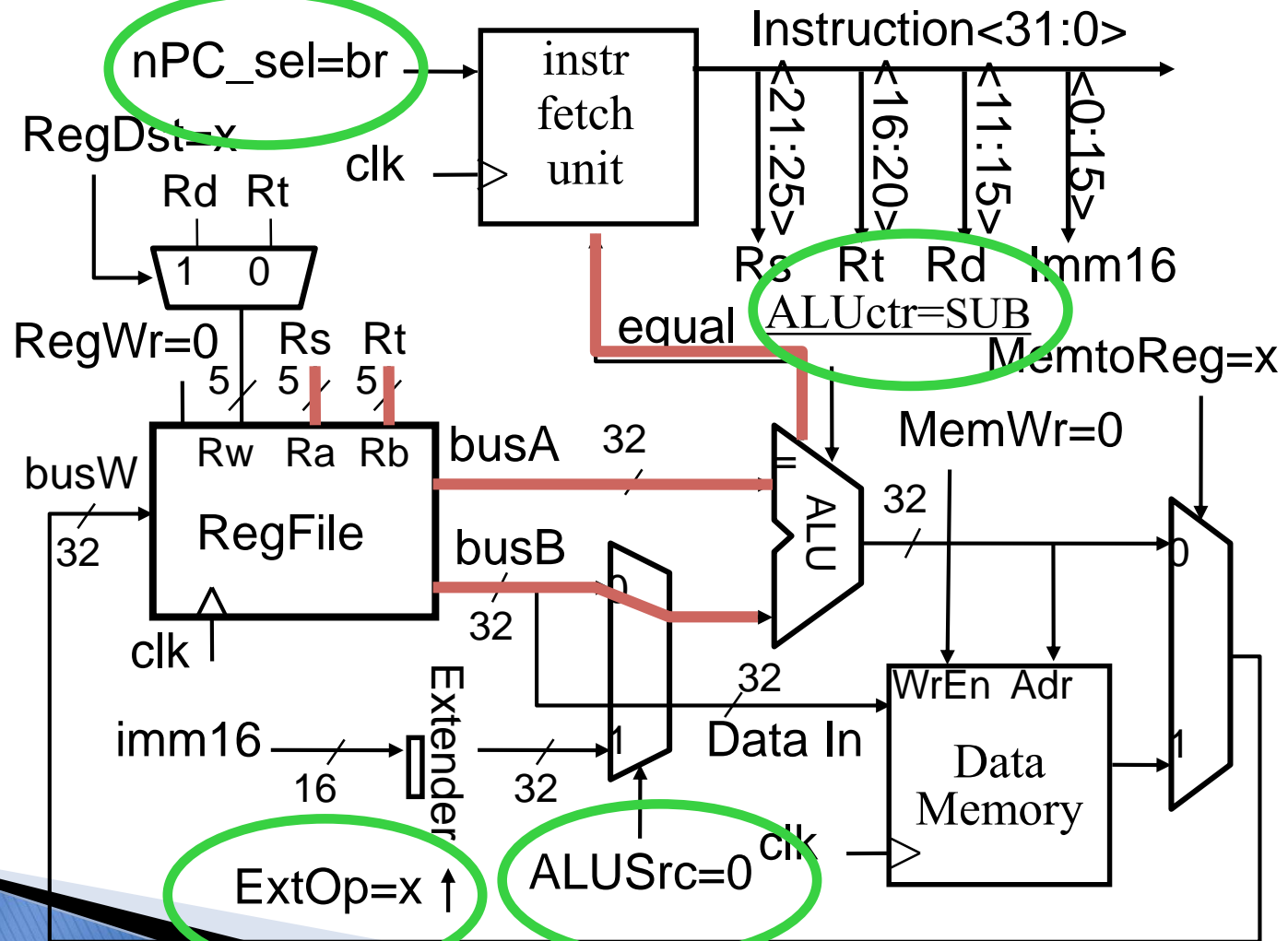- if  $(R[rs] - R[rt] == 0)$  then Zero = 1 ; else Zero = 0




# Instruction Fetch Unit end of Branch

 

- ▶ if (Zero == 1) then  $PC = PC + 4 + \text{SignExt}[\text{imm16}] * 4$  ; else  $PC = PC + 4$

*branch statement?*

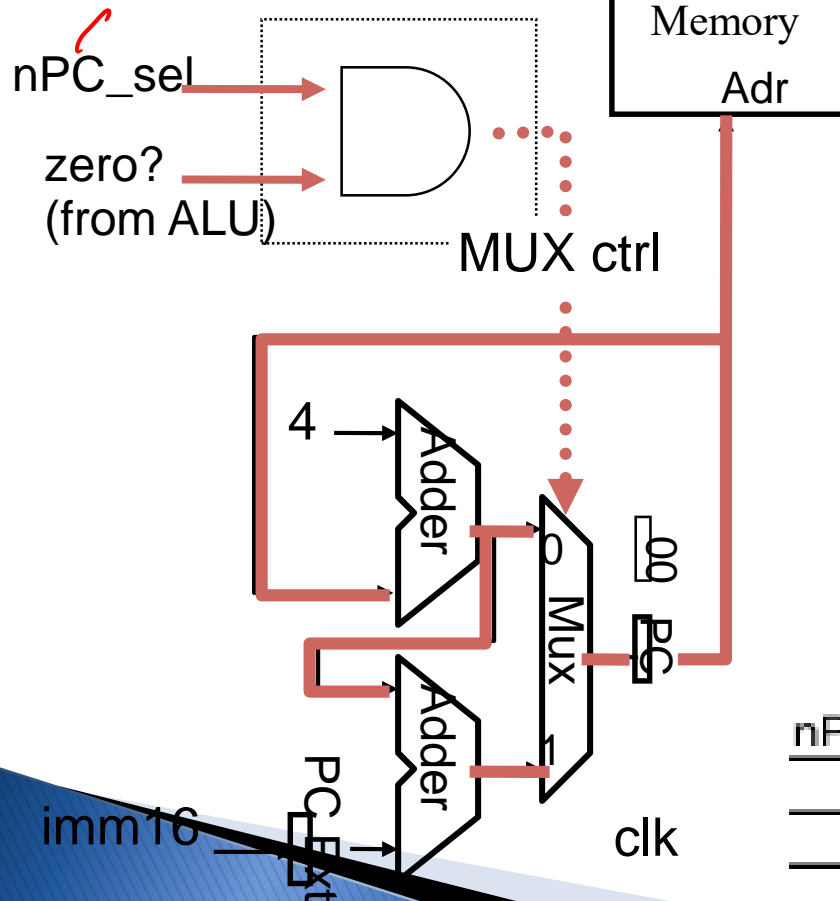


- What is encoding of nPC\_sel?
  - **Direct MUX select?**
  - **Branch inst. / not branch**
- Let's pick 2nd option

| nPC_sel | zero? | MUX |
|---------|-------|-----|
| 0       | x     | 0   |
| 1       | 0     | 0   |
| 1       | 1     | 1   |

Q: What logic gate?



# Control Logic

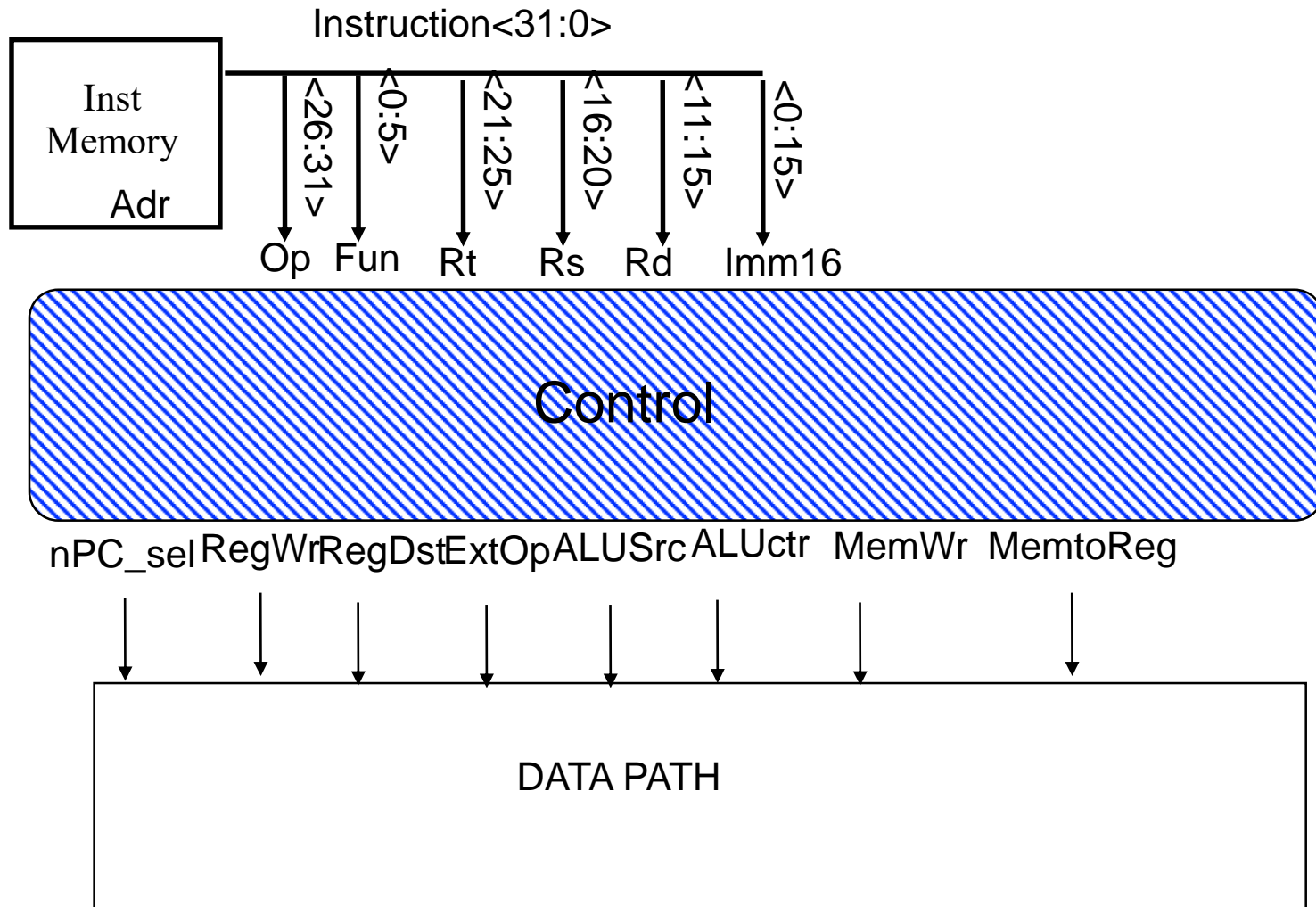

# Control Signals (1/2)

## inst      Register Transfer

|     |                                                                                                                                                          |                        |
|-----|----------------------------------------------------------------------------------------------------------------------------------------------------------|------------------------|
| add | $R[rd] \leftarrow R[rs] + R[rt];$                                                                                                                        | $PC \leftarrow PC + 4$ |
|     | $ALUsrc = \text{RegB}, ALUctr = \text{"ADD"}, \text{RegDst} = rd, \text{RegWr}, nPC\_sel = \text{"+4"}$                                                  |                        |
| sub | $R[rd] \leftarrow R[rs] - R[rt];$                                                                                                                        | $PC \leftarrow PC + 4$ |
|     | $ALUsrc = \text{RegB}, ALUctr = \text{"SUB"}, \text{RegDst} = rd, \text{RegWr}, nPC\_sel = \text{"+4"}$                                                  |                        |
| ori | $R[rt] \leftarrow R[rs] + \text{zero\_ext}(\text{Imm16});$                                                                                               | $PC \leftarrow PC + 4$ |
|     | $ALUsrc = \text{Im}, \text{Extop} = \text{"Z"}, ALUctr = \text{"OR"}, \text{RegDst} = rt, \text{RegWr}, nPC\_sel = \text{"+4"}$                          |                        |
| lw  | $R[rt] \leftarrow \text{MEM}[R[rs] + \text{sign\_ext}(\text{Imm16})];$                                                                                   | $PC \leftarrow PC + 4$ |
|     | $ALUsrc = \text{Im}, \text{Extop} = \text{"sn"}, ALUctr = \text{"ADD"}, \quad \text{MemtoReg}, \text{RegDst} = rt, \text{RegWr}, nPC\_sel = \text{"+4"}$ |                        |
| sw  | $\text{MEM}[R[rs] + \text{sign\_ext}(\text{Imm16})] \leftarrow R[rs];$                                                                                   | $PC \leftarrow PC + 4$ |
|     | $ALUsrc = \text{Im}, \text{Extop} = \text{"sn"}, ALUctr = \text{"ADD"}, \text{MemWr}, nPC\_sel = \text{"+4"}$                                            |                        |
| beq | $\text{if } (R[rs] == R[rt]) \text{ then } PC \leftarrow PC + \text{sign\_ext}(\text{Imm16}) \parallel 00 \text{ else } PC \leftarrow PC + 4$            |                        |
|     | $nPC\_sel = \text{"br"}, ALUctr = \text{"SUB"}$                                                                                                          |                        |

# Control Signals (2/2)

See Appendix A

func

op

|             |         |          |                   |         |         |          |         |
|-------------|---------|----------|-------------------|---------|---------|----------|---------|
|             | 10 0000 | 10 0010  | We Don't Care :-) |         |         |          |         |
|             | 00 0000 | 00 0000  | 00 1101           | 10 0011 | 10 1011 | 00 0100  | 00 0010 |
|             | add     | sub      | ori               | lw      | sw      | beq      | jump    |
| RegDst      | 1       | 1        | 0                 | 0       | x       | x        | x       |
| ALUSrc      | 0       | 0        | 1                 | 1       | 1       | 0        | x       |
| MemtoReg    | 0       | 0        | 0                 | 1       | x       | x        | x       |
| RegWrite    | 1       | 1        | 1                 | 1       | 0       | 0        | 0       |
| MemWrite    | 0       | 0        | 0                 | 0       | 1       | 0        | 0       |
| nPCsel      | 0       | 0        | 0                 | 0       | 0       | 1        | ?       |
| Jump        | 0       | 0        | 0                 | 0       | 0       | 0        | 1       |
| ExtOp       | x       | x        | 0                 | 1       | 1       | x        | x       |
| ALUctr<2:0> | Add     | Subtract | Or                | Add     | Add     | Subtract | x       |

|        |    |    |                |    |    |   |           |  |       |  |       |  |                  |
|--------|----|----|----------------|----|----|---|-----------|--|-------|--|-------|--|------------------|
|        | 31 | 26 | 21             | 16 | 11 | 6 | 0         |  |       |  |       |  |                  |
| R-type | op |    | rs             |    | rt |   | rd        |  | shamt |  | funct |  | add, sub         |
| I-type | op |    | rs             |    | rt |   | immediate |  |       |  |       |  | ori, lw, sw, beq |
| J-type | op |    | target address |    |    |   |           |  |       |  |       |  | jump             |

# Boolean Expressions for Controller

RegDst = add + sub

ALUSrc = ori + lw + sw

MemtoReg = lw

RegWrite = add + sub + ori + lw

MemWrite = sw

nPCsel = beq

Jump = jump

ExtOp = lw + sw

ALUctr[0] = sub + beq (assume ALUctr is 00 ADD, 01: SUB, 10: OR)

ALUctr[1] = or

*where,*

$rtype = \sim op_5 \cdot \sim op_4 \cdot \sim op_3 \cdot \sim op_2 \cdot \sim op_1 \cdot \sim op_0$ ,

$ori = \sim op_5 \cdot \sim op_4 \cdot op_3 \cdot op_2 \cdot \sim op_1 \cdot op_0$

$lw = op_5 \cdot \sim op_4 \cdot \sim op_3 \cdot \sim op_2 \cdot op_1 \cdot op_0$

$sw = op_5 \cdot \sim op_4 \cdot op_3 \cdot \sim op_2 \cdot op_1 \cdot op_0$

$beq = \sim op_5 \cdot \sim op_4 \cdot \sim op_3 \cdot op_2 \cdot \sim op_1 \cdot \sim op_0$


$jump = \sim op_5 \cdot \sim op_4 \cdot \sim op_3 \cdot \sim op_2 \cdot op_1 \cdot \sim op_0$

$add = rtype \cdot func_5 \cdot \sim func_4 \cdot \sim func_3 \cdot \sim func_2 \cdot \sim func_1 \cdot \sim func_0$

$sub = rtype \cdot func_5 \cdot \sim func_4 \cdot \sim func_3 \cdot \sim func_2 \cdot func_1 \cdot \sim func_0$


How do we  
implement this in  
gates?

# Controller Implementation

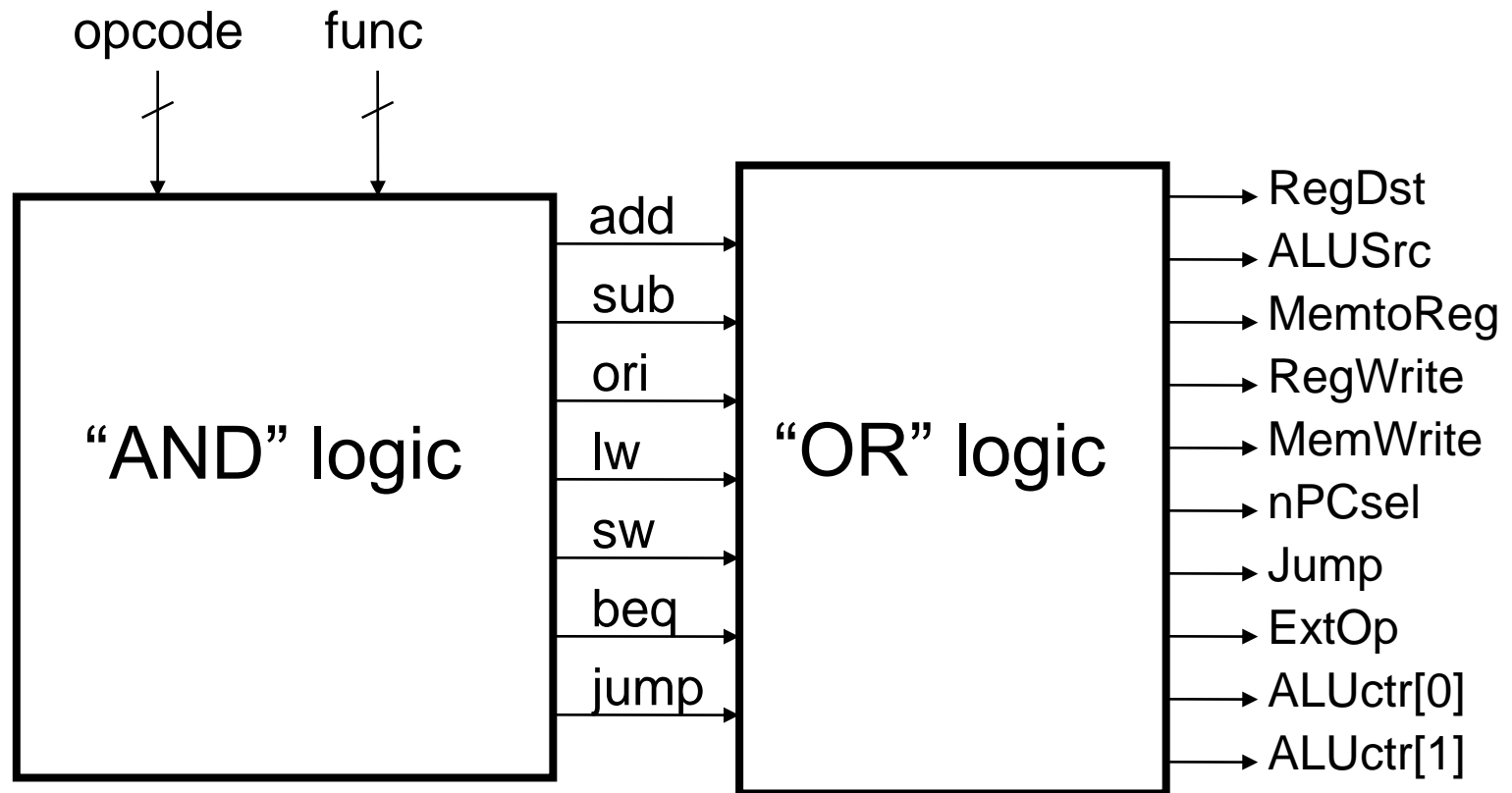



# Clocking Methodology

 


- ▶ Storage elements clocked by same edge
- ▶ Being physical devices, flip-flops (FF) and combinational logic have some delays
  - Gates: delay from input change to output change
  - Signals at FF D input must be stable before active clock edge to allow signal to travel within the FF (set-up time), and we have the usual clock-to-Q delay
- ▶ “Critical path” (longest path through logic) determines length of clock period


# An Abstract View of the Critical Path

Critical Path (Load Instruction) =  
Delay clock through PC (FFs) +  
Instruction Memory's Access Time +  
Register File's Access Time, +  
ALU to Perform a 32-bit Add +  
Data Memory Access Time +  
Stable Time for Register File Write

(Assumes a fast controller)

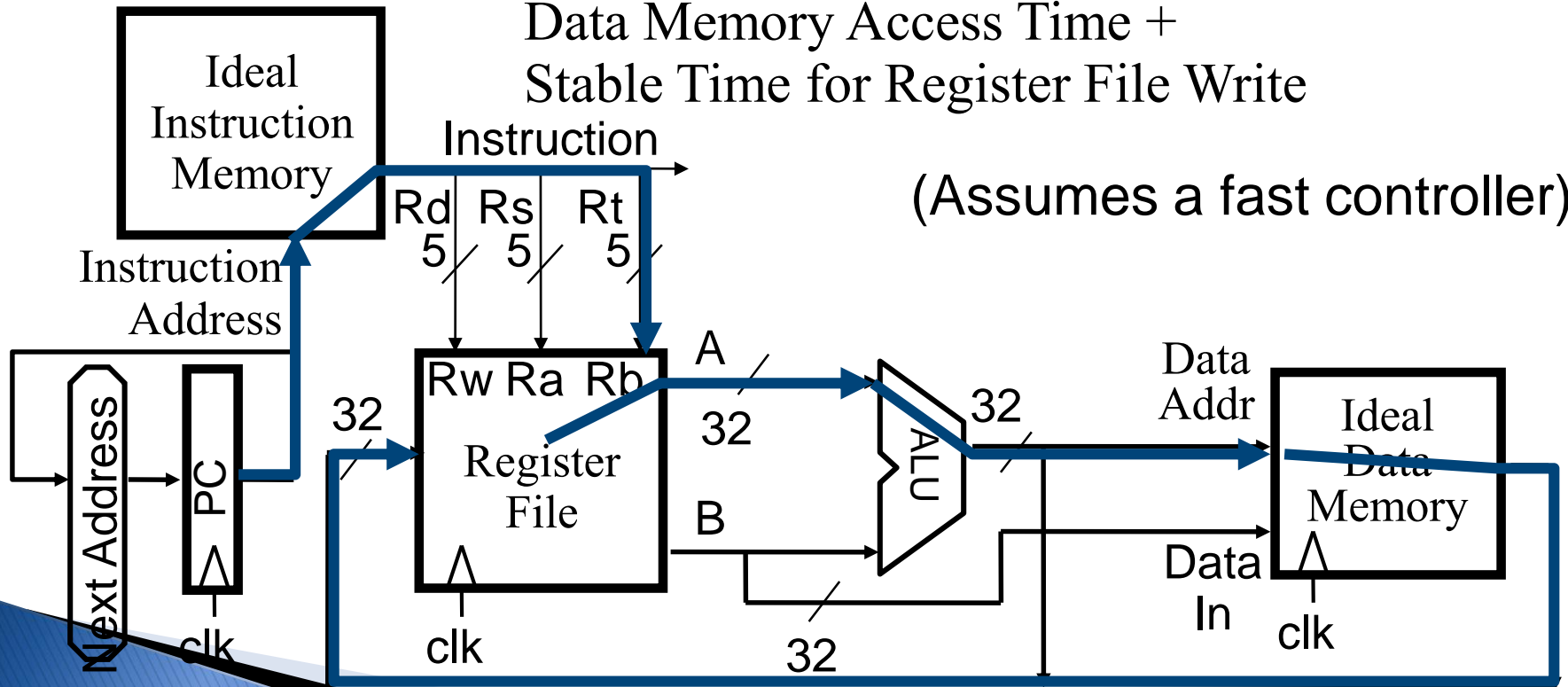

# Register-Register Timing: Cycle

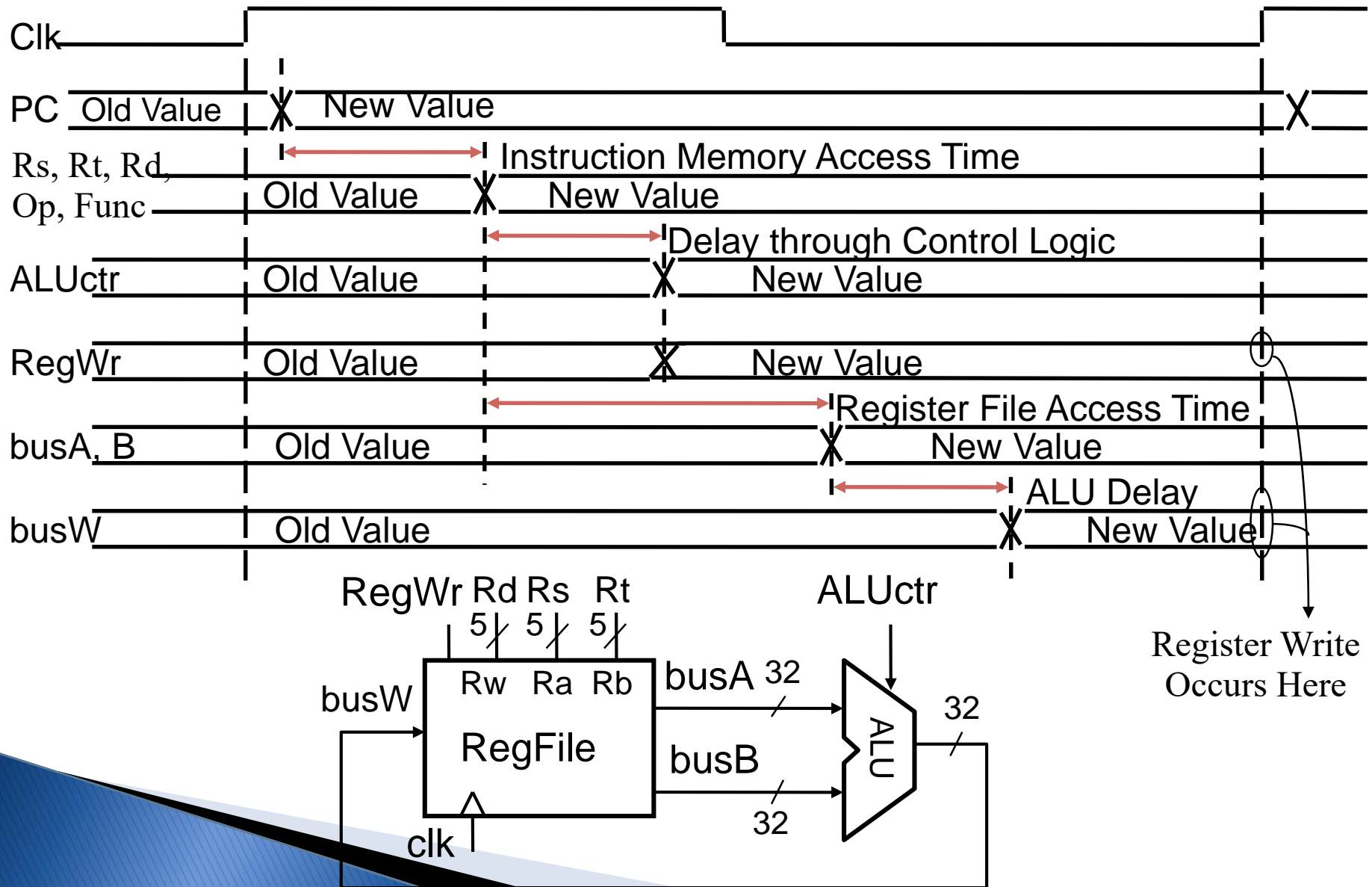

# Summary: Single-cycle Processor

- 5 steps to design a processor
  - 1. Analyze instruction set → datapath requirements
  - 2. Select set of datapath components & establish clock methodology
  - 3. Assemble datapath meeting the requirements
  - 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
  - 5. Assemble the control logic
    - Formulate Logic Equations
    - Design Circuits

